

188

188

: HAND WRITTEN NOTES:-

OF

①

Electrical ENGG

-: SUBJECT:-

MEASUREMENT

& INSTRUMENTATION

85


Electrical Engg
②

Electrical & Electronics Measurement And Instrumentation.

(only for IET PSU)

Electrical	Electronic	Instrumentation.
Measurement of R, L, C	Qmeter	Measurement of non electrical quantities like temp
Measurement of V, I, P, p.f, Energy.	Error Analysis CRO Digital Meter	pressure humidity flow. + acceleration
Potentiometer		
Instrumentation Xmen		

Text Book :- A K SHAWNEY

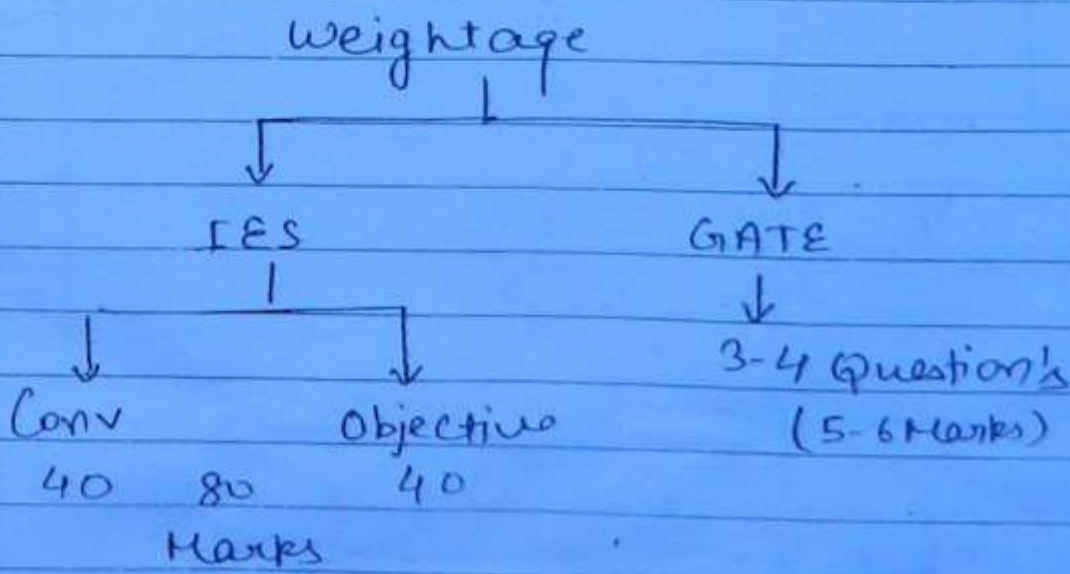

Analog Meter

Quantity of Measurement


principle

Representation


I	Electromagnetic	Indicating	Integrating	Rec
V	Electrostatic	↓	↓	
P	Induction	Ammeter	Energy meter	pot
P.f	Thermal (heating)	Voltmeter		Gro
Energy		Wattmeter		
f		pf meter		

order of Instruments:-

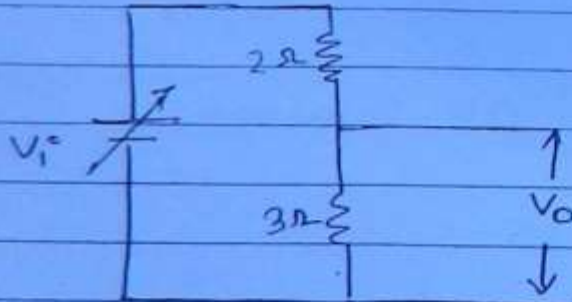Zeroth order:- system change instantaneously.



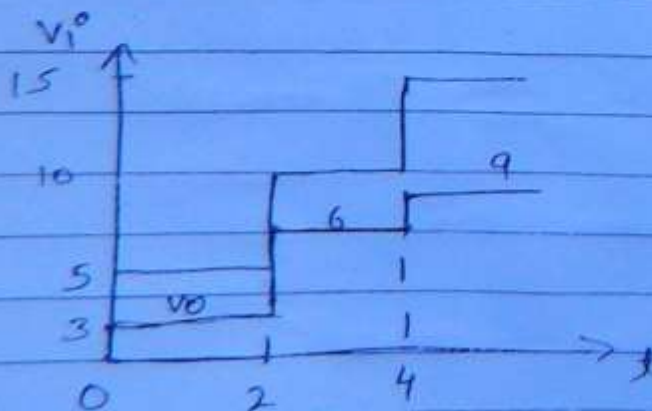
$$V_o = \frac{3V_i}{3+2} = \frac{3V_i}{5}$$



No Transient's.

First order :-

(5)

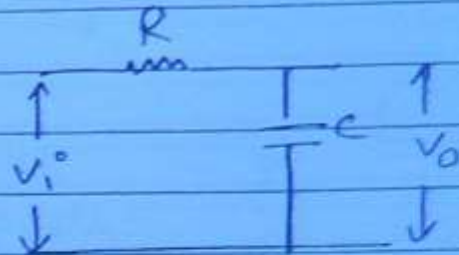


$$V_o = V_i [1 - e^{-t/RC}]$$

Recording



Null Detector

↓
potentiometric
Galvanometric

↓
potentiometer.

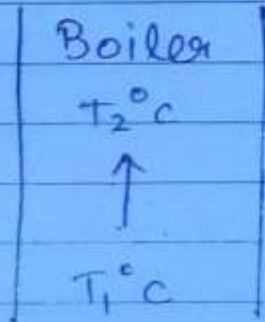

2V

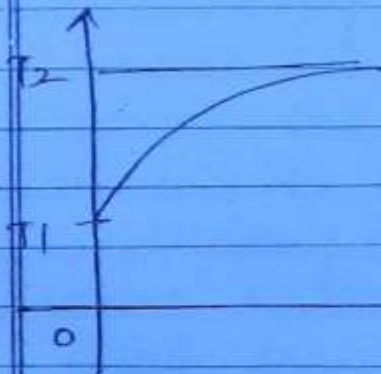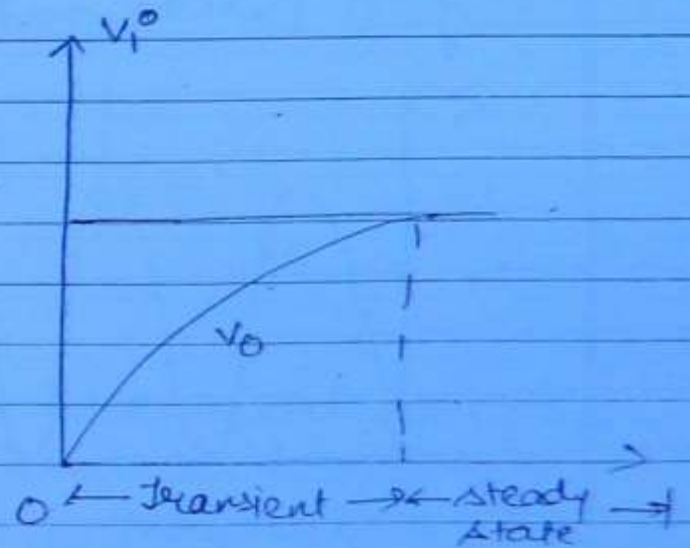

Eg:- RTD - Resistance Temp^t detector.

Thermocouple.

Second order :-





$$\frac{V_0}{V_i} = \frac{1/LC}{s^2 + \frac{R}{L}s + 1/LC}$$

(6)


$$T(s) = \frac{V_0}{V_i} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

ζ = Damping factor or (Ratio).



$\zeta = 0$ (undamped)

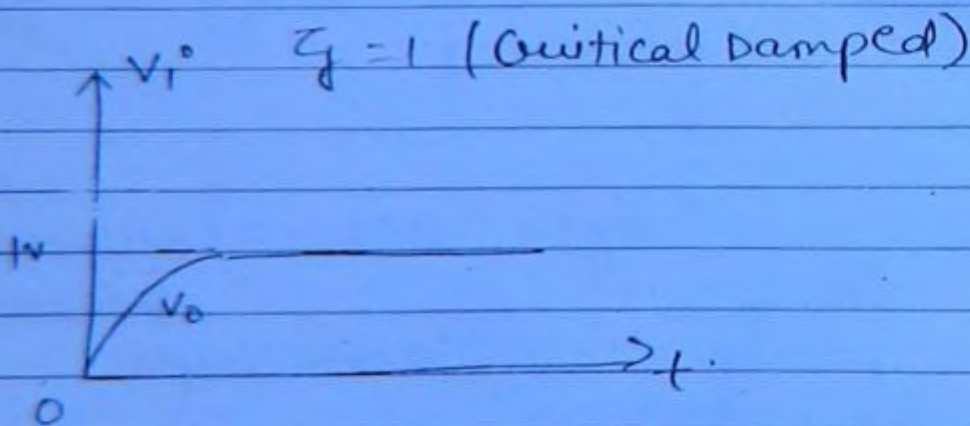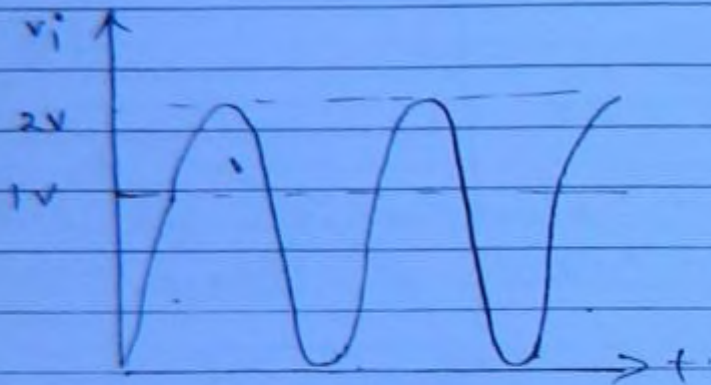

$0 < \zeta < 1$ (underdamped)

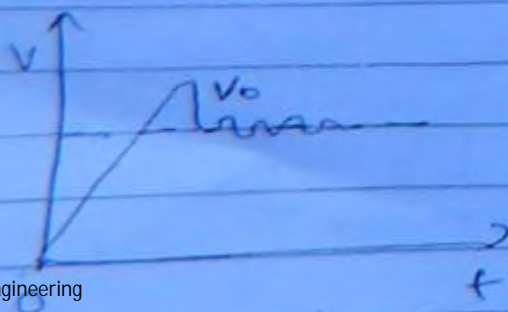


$\delta > 1$ (overdamped)

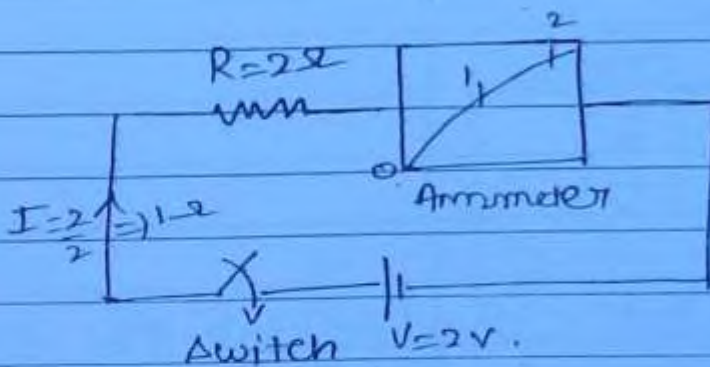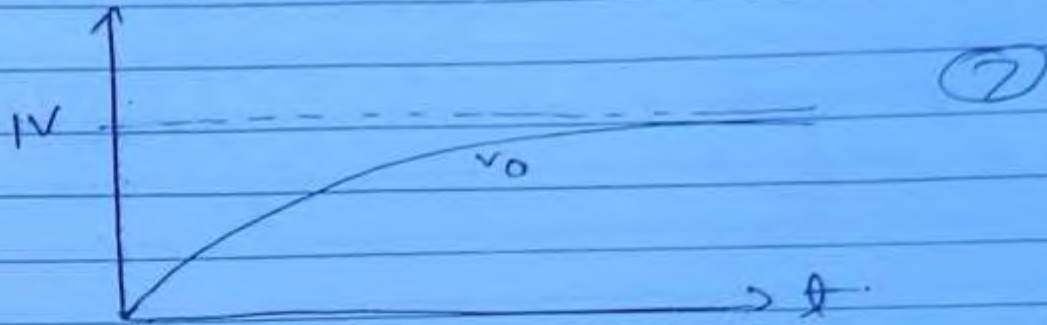

Indicating Meters! - Electrical system components (motor, generators, transmission line etc.) are containing R, L, C parameters and hence they are behaving like second order system to measure voltage, current and power the instrument should also behave similar to second order system. Hence the indicating meter are of second order type having a damping factor between 0.6 to 0.8. If the damping factor is nearer to the critical damped value then the output reaches to the steady state value at faster rate in minimum time.

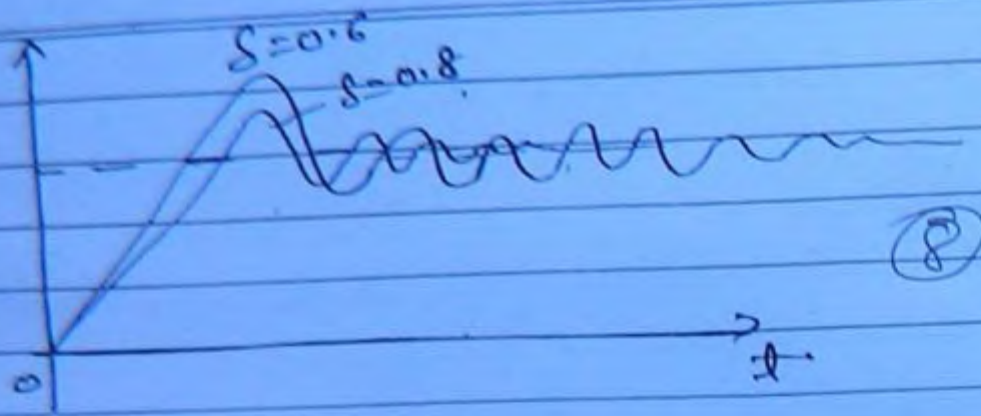The time response of indicating meter is depends on damping of the system.




Torques of Indicating Instrument →



- ① Damping Torque (T_D)
- ② Deflecting Torque (T_d)
- ③ Control Torque (T_c)

Damping Torque (T_D):- Used to stop the damping's produced at the final steady state of the instrument's.

(ii) Air Friction Damping:-

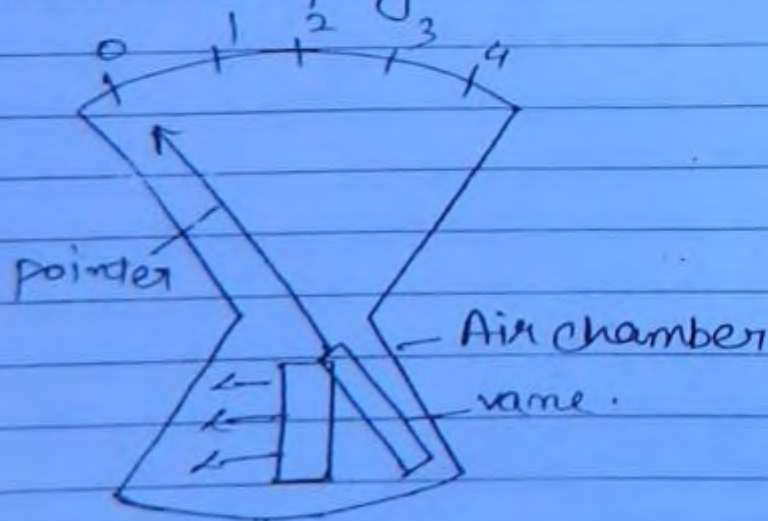


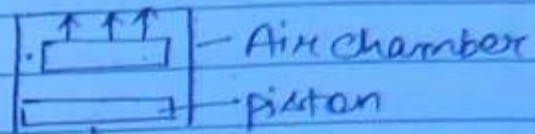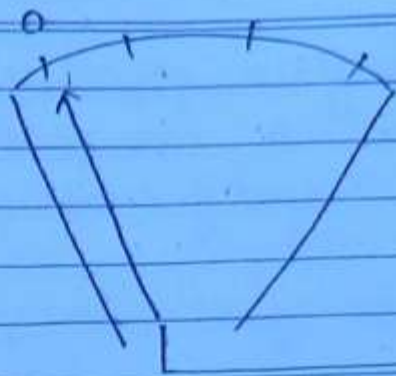Eg :- → Moving Iron instrument's
→ Electrodynamometer.



(9)

(ii) Fluid friction :-

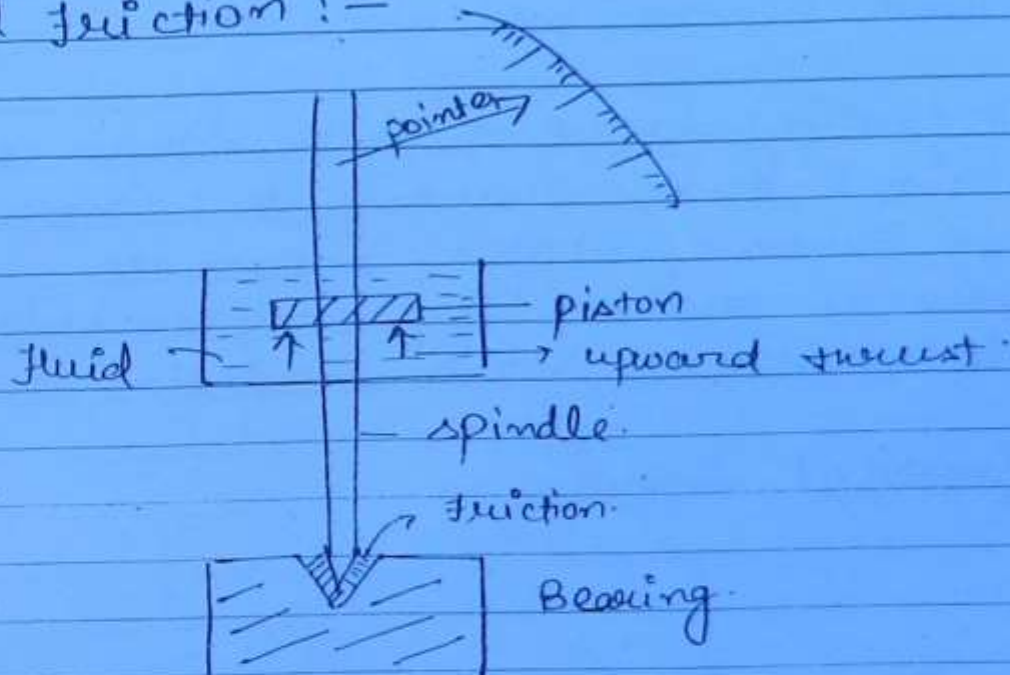

Example :- Electrostatic Meter.

Fluid friction is used where the deflecting torque is \min^m . to reduce the friction b/w bearing and spindle and also used to reduce damping at final steady state position.

(iii) Eddy Current / Electromagnetic Damping :-


Whenever a current carrying coil wound on a core and this core is moving in a magnetic field an EMF is induced. This will produce an eddy current. The interaction

of eddy current and flux produces damping torque which is used to damp out the oscillation at final steady state position.
 Eg:- Galvanometer, - Eddy (1/0)
 PMMC - Electromagnetic damping.

It is used where the permanent magnet is used in the instruments.

2) Deflecting Torque \rightarrow These torque are proportional to the quantity to be measured.
 i.e. Current, voltage, power etc.
 This is produced by using the principles of electromagnetic, static induction etc.

3) Control Torque \rightarrow (Tc)

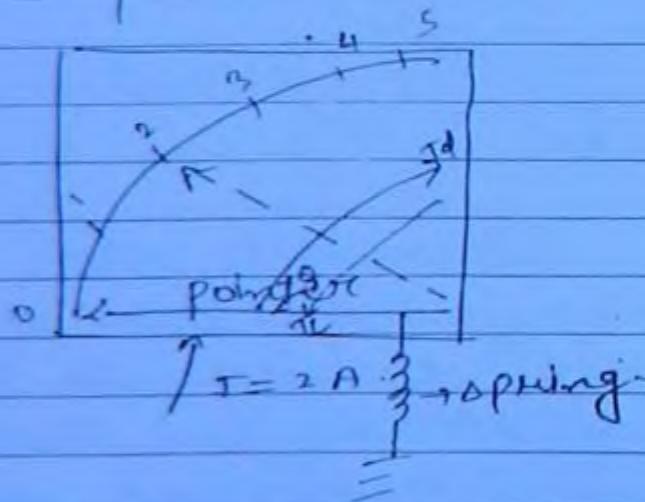

At balance $T_d = T_c$

$$T_d \propto \theta$$

$$T_c = K \theta$$

θ = deflecting angle in radians.

T_c = Control torque in N.m.


K = Spring constant in N.m/rad.

- Page _____
- (41)
- 2) Voltmeter
 - 3) watt-meter
 - 4) power factor meter
 - 5) Energymeter
 - 6) Megger \rightarrow high resistance measurement.
 - 7) power frequency meter.

AC Measurement :-

$$i_1 = I_{m1} \sin(\omega t - \phi)$$

$$i_2 = I_{m2} \sin \omega t$$

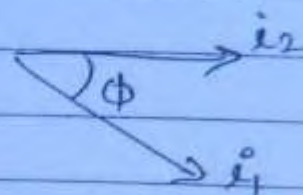

$$T_{d \text{ avg}} = \frac{1}{T} \int_0^T T_d \cdot dt = \frac{1}{T} \int_0^T (i_1 i_2 \frac{dH}{d\theta}) d\theta$$

for sinusoidal signal $T = 2\pi$

$$T_{d \text{ avg}} = \frac{1}{2\pi} \int_0^{2\pi} I_{m1} I_{m2} \sin \omega t \cdot \sin(\omega t - \phi) d(\omega t) \frac{dH}{d\theta}$$

$$T_{d \text{ avg}} = \frac{I_{m1} I_{m2} \cos \phi}{2} \frac{dH}{d\theta}$$

$$I_{RMS1} = \frac{I_{m1}}{\sqrt{2}} = I_1, \quad I_{RMS2} = \frac{I_{m2}}{\sqrt{2}} = I_2$$

$$T_{d \text{ avg}} = I_1 I_2 \cos \phi \frac{dH}{d\theta}$$

$$T_c = K\theta$$

At balance $T_c = T_d$

$$K\theta = I_1 I_2 \cos \phi \frac{dH}{d\theta}$$

$$\boxed{\theta \propto I_1 I_2 \cos \phi}$$

wear and tear can be avoided and its life span is more.

(12)

- (2) **Temperature Error:-** The internal resistance of the meter is proportional to surrounding temperature. If the temperature is changed then internal resistance will be changed so that the current flowing through the meter is affected and hence the meter reads wrong value.

It is compensated by low value of α material's like

Manganin — $\alpha = 0.00015/^\circ\text{C}$
or

Constantan.

Copper — $\alpha \Rightarrow 0.004/^\circ\text{C}$

- (3) **Frequency Error:-** The inductance of the coil is depends on frequency if the input frequency is changed then the inductive reactance will be changed which causes error in the meter reading.

% Relative Limiting Error = $E_r = \frac{\text{Measured value} - \text{True Value}}{\text{True Value}} \times 100$

$$\% E_r = \frac{A_m - A_t}{A_t} \times 100$$

True Value

$R_t = 100\Omega$, $R_m = 105\Omega$

$$\% E_r = \frac{105 - 100}{100} \times 100 \Rightarrow 5\%$$

$$R_m = 105 \Omega$$


$$R_t = 100 \Omega$$

$$Error = 5 \Omega$$


(13)

$$\text{Accuracy} = -\text{Error}$$

Electromagnetic Meters:-

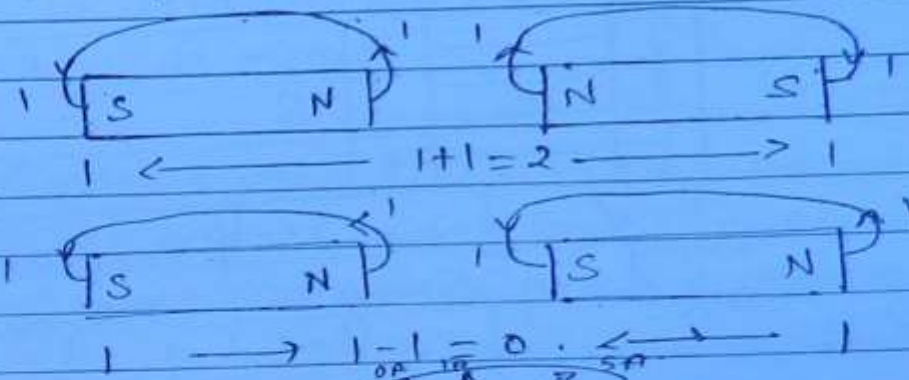

(1)

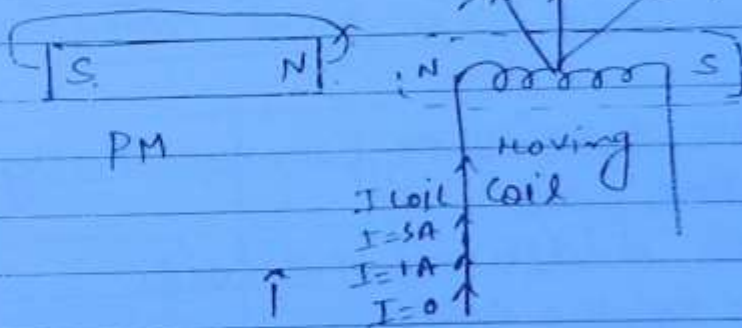


PMMC

Deflection is due to current.



(ii)

Moving Iron

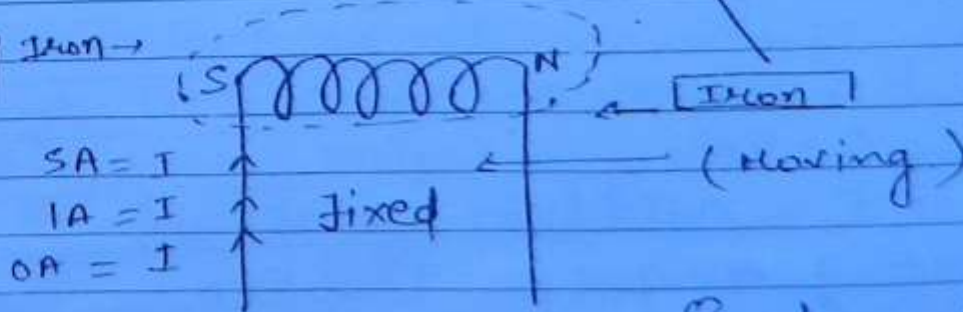

$$SA = I$$

$$IA = I$$


$$OA = I$$

Fixed


(Moving)

(3)

Electrodynamometer:-

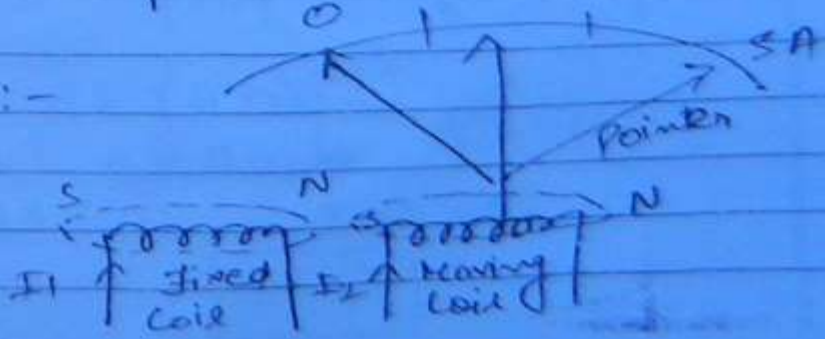

① PMMC [Permanent Magnet Moving Coil] :-

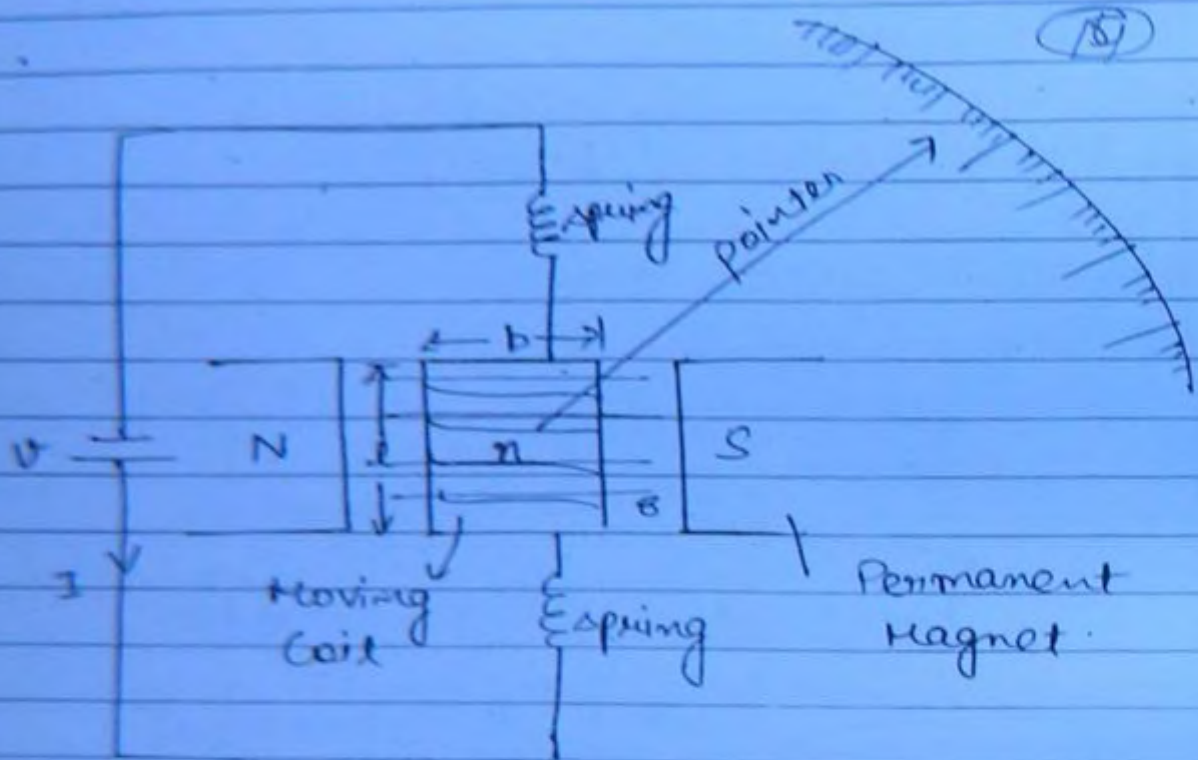

B = Magnetic flux density of permanent magnet.

l = length of the coil

b = breadth or width of the coil.

n = no of turns of the coil.

I = Current flowing through Meter [current to be measured]

A = Area of coil = lb

$$\text{Force } F = n B I l \sin \theta$$

$$\theta = 90^\circ$$

$$F = n B I l$$

$$\text{Deflecting torque, } T_d = F \times b$$

$$T_d = n B I l b$$

$$\Rightarrow n B I A$$


$$T_d = G I, \quad G = n B A$$

$$[T_d \propto I]$$

$T_c = K\theta$
At balance, $T_c = T_d$

$$K\theta = G I$$


$$\boxed{\theta \propto I}$$

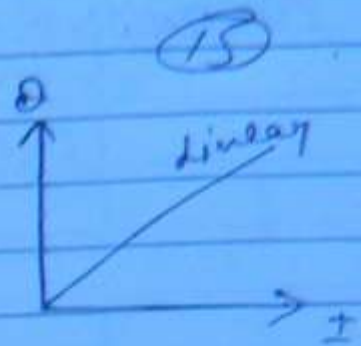



- ① Measures DC or Avg current or voltage.
- ② Scale is linear or uniform.
- ③ Accuracy is more.

Note (i) PMMC measures DC or avg quantity.

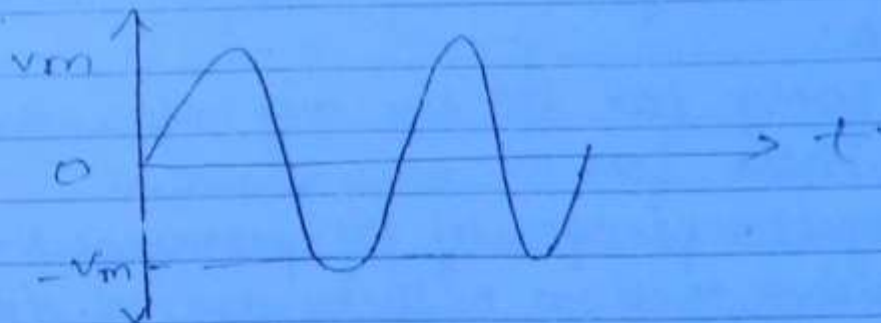- (ii) If a ac signal with equal value magnitude of +ve & negative is passing through PMMC then the pointer vibrates near to the zero position bcoz avg value is zero.



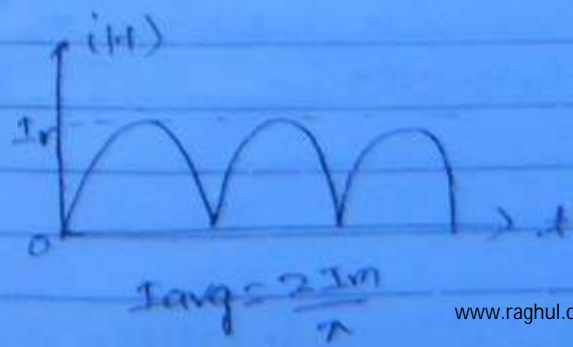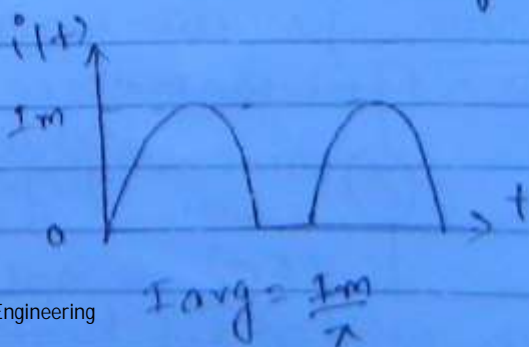
- (iii) If the output of half wave rectifier is passing through PMMC then it will read $I_{avg} = \frac{I_m}{\pi}$. Similarly, the output of full wave rectifier PMMC reads, $I_{avg} = \frac{2I_m}{\pi}$.



For any waveform find the I_{avg} by using

$$I_{avg} = \frac{1}{T} \int_0^T i(t) dt$$

(16)

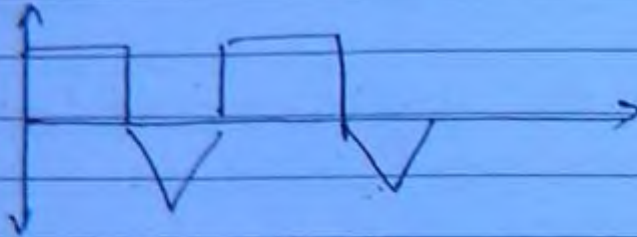

The current $i(t) = I_0 + I_1 \sin \omega t + I_2 \sin 2\omega t + \dots$ is passing through PMMC it reads.
 $I_{avg} = I_0$


Disadvantage.

- 1) Torque/weight ratio is higher in PMMC. So that accuracy is more compare to other meter's.
- 2) Used only for DC or avg measurement not suitable for AC measurement.
- 3) The magnetic property of permanent magnet and spring tension reduces due to surrounding temperature and aging.
- 4) For direct measurement it is suitable to measure current upto 50mA or 100mV.

Enhancement of Meters :-

① Ammeter :-


$I = 5A$

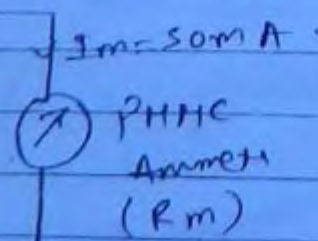

Device will get burnt.

Ammeter Shunt's :-

(17)

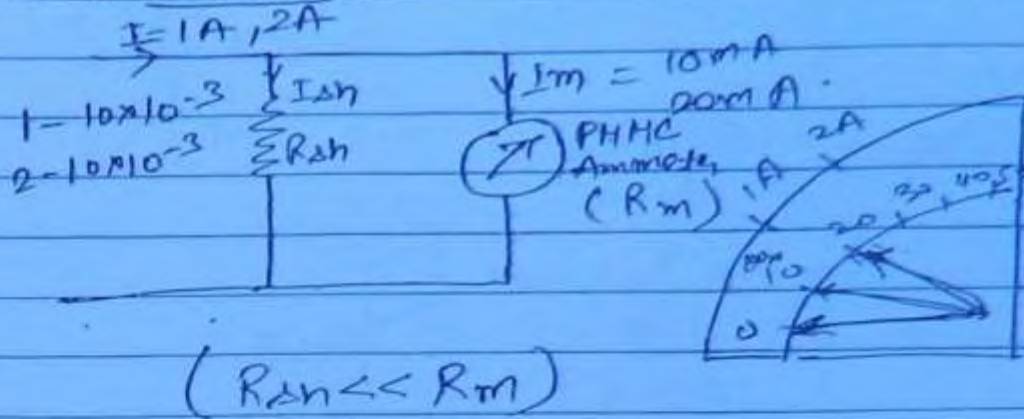

$$m = \text{multiplication factor} = \frac{I}{I_m} = \frac{5}{50 \times 10^{-3}} \rightarrow 100$$

$$I_m = \frac{I \cdot R_{sh}}{R_{sh} + R_m}$$

$$\frac{R_{sh} + R_m}{R_{sh}} = \frac{I}{I_m} = m$$

$$R_{sh} = \frac{R_m}{(m-1)}$$

For enhancement of ammeter, the shunt resistance (R_{sh}) is connected in parallel to the meter. R_{sh} is made of manganin which has low value of α .

$$[\text{Voltage drop} = V_m \cdot R_m]$$

A PMMC ammeter has a meter resistance of 100Ω and measures current of $10mA$ ^{with} direct measurement. Now much of shunt resistance is required to measure current's of

(i) $100mA$

(ii) $1A$

(iii) $10A$

Find the voltage drop across the meter at full

scale in each case?

(18)

IV

~~100 A.~~

~~$m = \frac{10 \times 10^{-3}}{100}$~~

~~$\Rightarrow 10^{-4}$~~

~~$m = \frac{100}{10 \times 10^{-3}} \Rightarrow 10,000$~~

~~$R_{sh} = \frac{R_m}{(m-1)}$~~

(I)

$I_m = 10 \text{ mA}$

$R_m = 100 \Omega$

(II)

$m = I_{fs} / I_m = 100 / 10 = 10$

$R_{sh} = R_m / (m-1) = 100 / (10-1) = 11.1 \Omega$

$V_m = I_m \cdot R_m = 10 \times 10^{-3} \times 100 = 1 \text{ V}$

(III)

$I = 1 \text{ A}$

$m = \frac{1}{10 \times 10^{-3}} = 100$

$R_{sh} = \frac{100}{100-1} = 1.01 \Omega$

$V = I_m \cdot R_m = 1 \text{ V}$

(IV)


$I = 10 \text{ A}$

$m = \frac{10}{10 \times 10^{-3}} = 1000$

$R_{sh} = \frac{100}{1000-1} = 0.1001 \Omega$


$V = I_m \cdot R_m = 1 \text{ V}$

$$I = 100 \text{ mA}$$

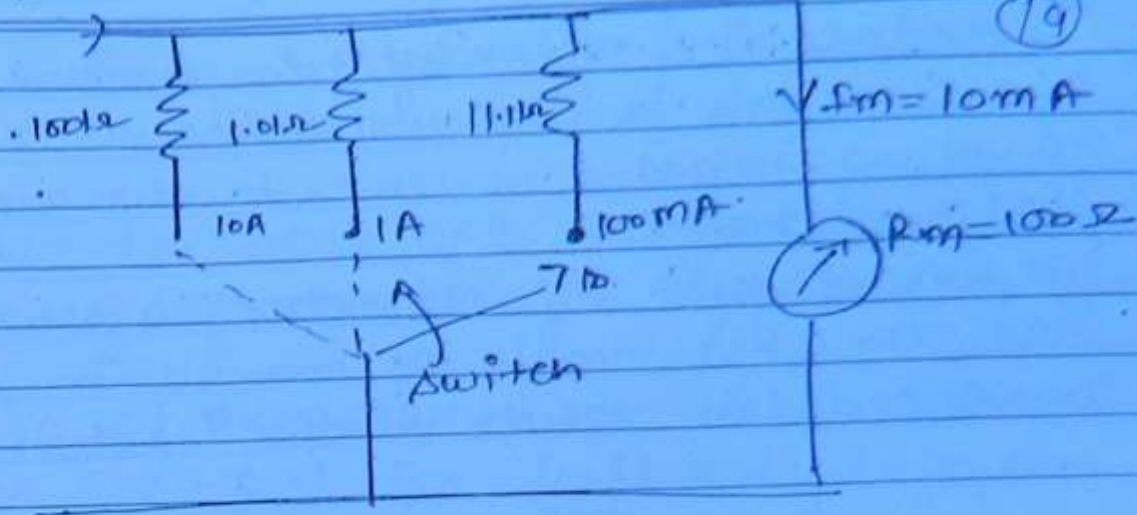


Multi Ammeter.

Effect Of Temperature On Ammeter →

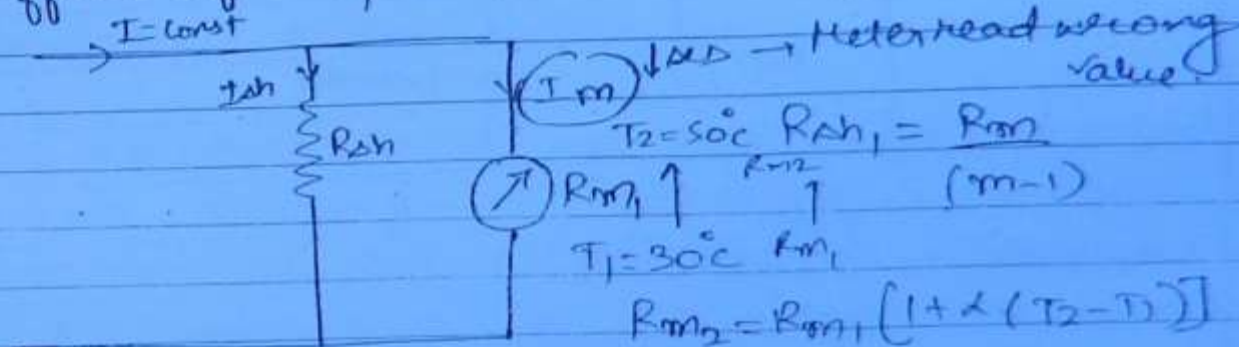

For compensating this we use →

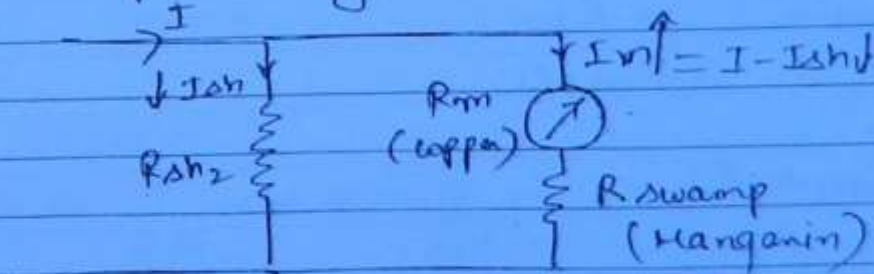

$$I_m = I \cdot \frac{R_{sh2}}{R_{sh2} + R_{m1} + R_{swamp}} \quad , \quad m = \frac{I}{I_m}$$


$$R_{sh2} = \frac{R_{m1} + R_{swamp}}{(m-1)} = \frac{R_{m1}}{(m-1)} + \frac{R_{swamp}}{(m-1)}$$

$$R_{sh2} = R_{sh1} + R_{swamp} \quad , \quad R_{sh2} > R_{sh1}$$

To reduce the effect of temperature in case of ammeter's swanp resistance made of manganin is added in series to the meter.

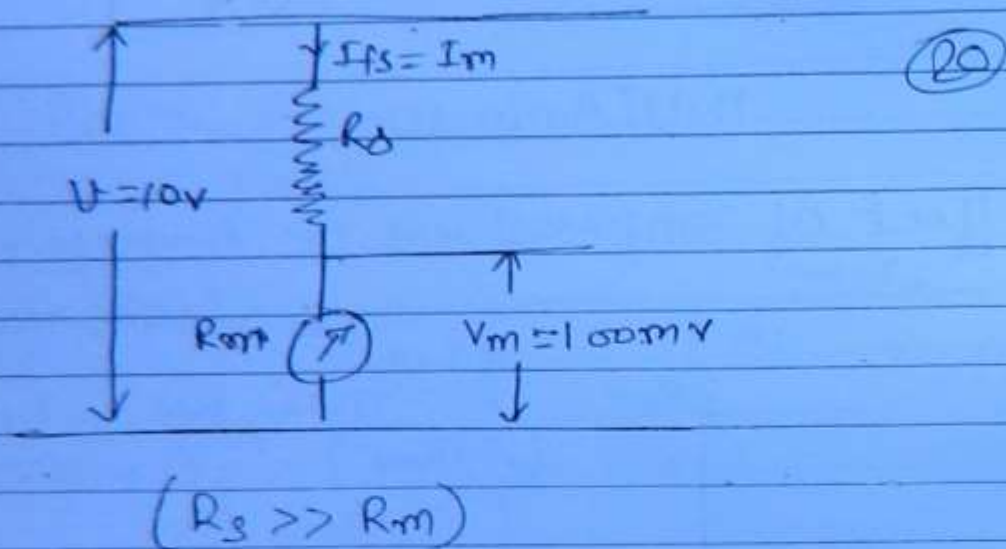(ii) Voltmeter:-

For Enhancement of voltmeter's a series multiple resistor (R_s) made of manganin is connected in series to the meter.



$$m = \frac{V}{V_m} = \text{Multiplication factor.}$$

$$V_m = \frac{V \cdot R_m}{(R_m + R_s)}$$

$$\frac{R_m + R_s}{R_m} = \frac{V}{V_m} = m$$

$$[R_s = R_m(m-1)]$$

$$\text{full scale current} = I_{fs} = \frac{V}{(R_s + R_m)}$$

voltmeter sensitivity (or) figure of merit (FOM):-

$$S_v = \frac{1}{I_{fs}} = \frac{R_s + R_m}{V} \quad \Omega/V \quad (21)$$

Note:- Higher the value of S_v , higher the sensitivity accuracy of meter. Lower the loading effect.

→ In Case of Ammeter which takes low value of the current for full scale deflection than its sensitivity is maximum.

Eg:- Two meter's A & B having a full scale current of 1mA & 5mA than meter A is more sensitive than meter B.

Q The voltmeter having an internal resistance of 100Ω measures the voltage upto 10mV without R_s . How much of R_s is required to measure a voltage of (i) 100mV, (ii) 1V (iii) 10V. In each case find full scale current and

Ans $R_m = 100\Omega$ voltmeter sensitivity
 $V_m = 10\text{mV}$.

(i) $V = 100\text{mV}$
 $m = \frac{V}{V_m} = 10$
 $R_s = R_m (m - 1)$
 $= 100 (10 - 1)$
 $= 900\Omega$

$$I_{fs} = \frac{V}{R_s + R_m} = \frac{100 \times 10^{-3}}{900 + 100} = 0.1\text{mA}$$

$$S_v = \frac{1}{I_{fs}} = \frac{1}{0.1} = 10\text{K}\Omega/V$$

②

$$V_s = 1V$$

$$m = \frac{1}{10 \times 10^{-3}} = 100$$

(22)

$$R_s = 100 (100 - 1) = 9900 \Omega$$

$$I_{fs} = \frac{1}{9900 + 100} = 0.1 \text{ mA}$$

$$S_V = 10 \text{ K}\Omega/\text{V}$$

③


$$V_s = 10V$$

$$m = \frac{10}{10 \times 10^{-3}} = 1000$$

$$R_s = 100 (1000 - 1) = 99900 \Omega$$

$$I_{fs} = \frac{10}{99900 + 100} = 0.1 \text{ mA}$$

$$S_V = 10 \text{ K}\Omega/\text{V}$$

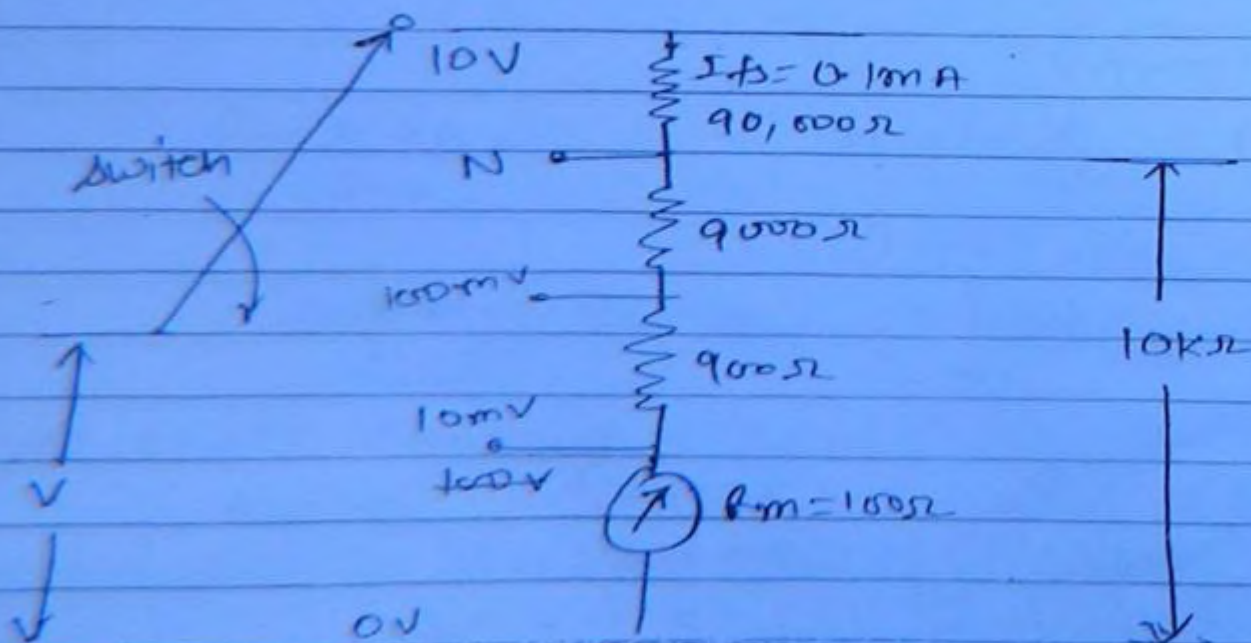

Voltmeter Sensitivity indicates the change in the resistance for unit change in the voltage.

(23)


Loading Effect:- If a low sensitivity voltmeter's are used for measurement of voltage across equipment the meter will work's as a load and the current is passing through the meter so that instrument read wrong value. This is called loading effect.

To reduce the loading effect high sensitivity voltmeter's are to be used.

Q

Two voltmeter's A & B are used to measure voltage across $15\text{K}\Omega$ resistance for the circuit shown in the figure. Meter A has sensitivity of $1\text{K}\Omega/\text{V}$ and Meter B has sensitivity of $1\text{M}\Omega/\text{V}$. Find the error in the measurement of voltage across the $50\text{K}\Omega$.

As

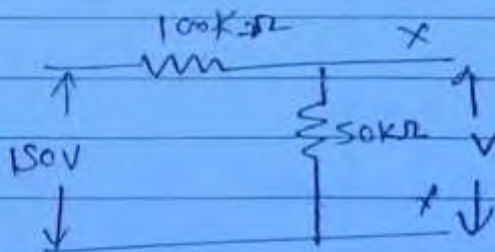

$$V_{\text{True}} = V_T = \frac{50}{100 + 50} \times 150$$

$$\Rightarrow 50\text{V}$$

meter A

$$S_V = 1\text{K}\Omega/\text{V}$$


$$V = (0 - 50)\text{V}$$

$$R_S + R_{m1} = V S_V$$

$$\Rightarrow 50 \times 1 = 50\text{K}\Omega$$

$$\text{Measured} = V_A = \frac{25 \times 150}{100 + 25}$$

$$\Rightarrow 30\text{V}$$

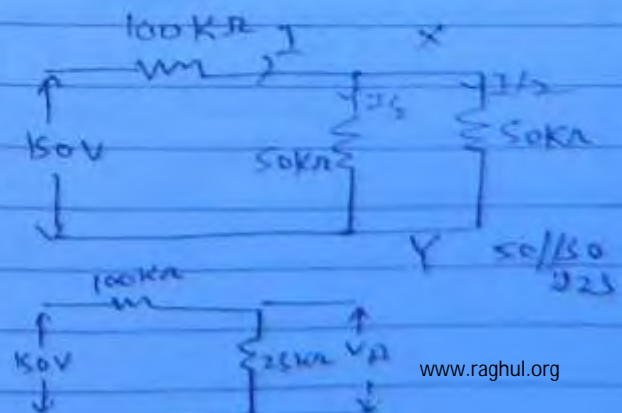

$$\% E_a = \frac{V_m - V_T}{V_T} \times 100$$

$$\Rightarrow \frac{30 - 50}{50} \times 100$$


(24)

$$E_a = -40\%$$


$$S_V = 1 \text{ M}\Omega/\text{V}$$

$$V = 0.50 \text{ V}$$
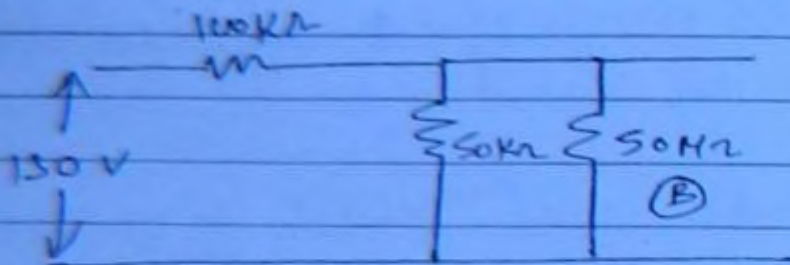
$$R_s + R_m = V S_V = 50 \text{ M}\Omega$$


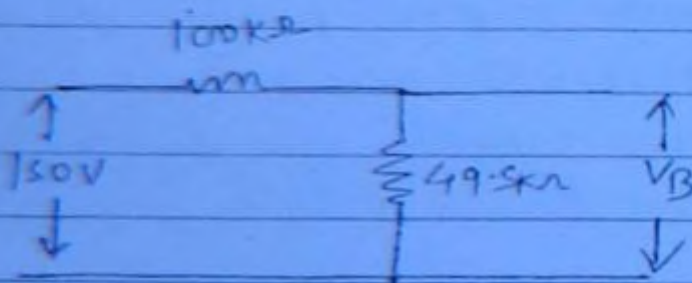
$$50\text{k}\Omega \parallel 50\text{M}\Omega \Rightarrow 49.5\text{k}\Omega$$




$$V_B = \frac{150 \times 49.5}{100 + 49.5} = 49.7 \text{ V}$$

$$E_a = \frac{49.7 - 50}{50} \times 100$$


$$E_a = -0.6\%$$

Voltmeter with different Ratings:-

25

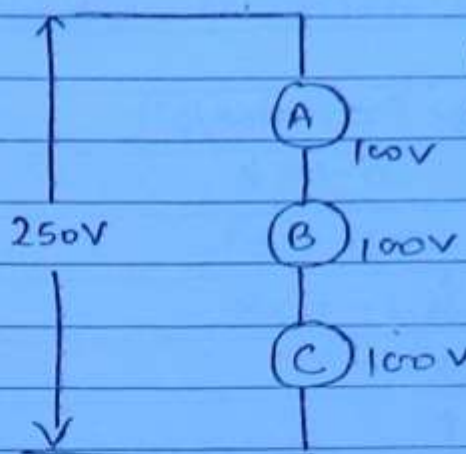

Given Rating	A	B	C
	V, S_v	I_{fs}, V	$I_{fs}, (R_s + R_m)$
	$S_v = \frac{R_s + R_m}{V}$	$I_{fs} = \frac{V}{R_s + R_m}$	$R_c = (R_s + R_m)$
	$R_A = R_s + R_m = V S_v$	$(R_s + R_m) = \frac{V}{I_{fs}} = R_B$	

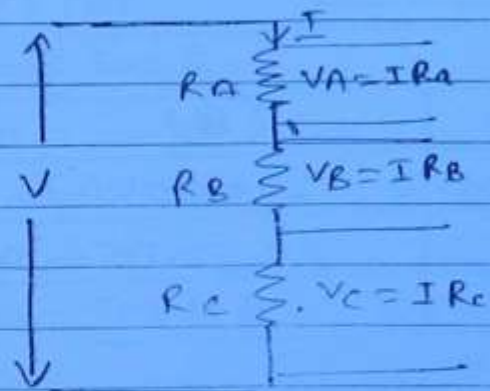

$$I = \frac{V}{(R_A + R_B + R_C)}$$

32
817


A	B	C	
100V, 5mA	100V, 250Ω/V	10mA, 15KΩ	$100 \times 5 \times 10^{-3}$
$R_A = \frac{100}{5 \times 10^{-3}} = 20K\Omega$	$R_B = 100 \times 250 \Rightarrow 25K\Omega$	$R_C = 15K\Omega$	0.5 250 150 400



$$I = \frac{120}{20 + 25 + 15} \Rightarrow 2 \text{ mA}$$

$$V_A = 2 \times 20 = 40V$$

$$V_B = 2 \times 25 = 50V$$

$$V_C = 2 \times 15 = 30V$$

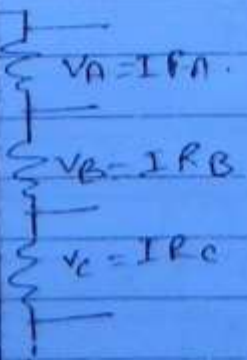

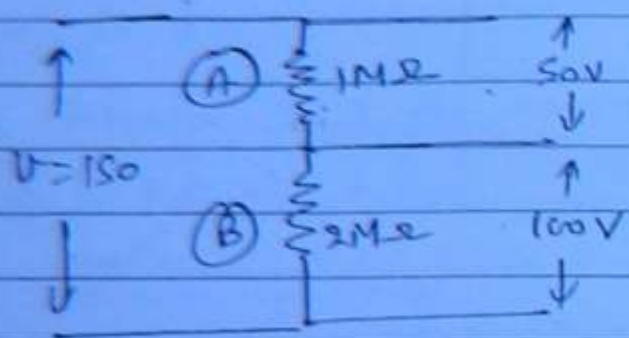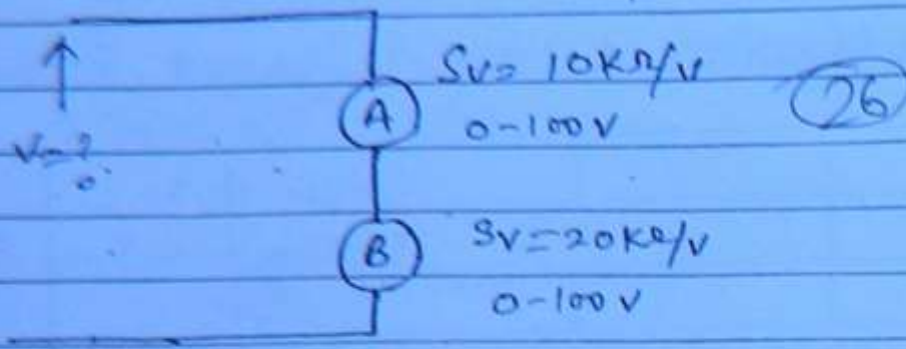

OR

(A)




$$S_V = 10 \text{ k}\Omega/\text{V}$$

$$I_B = \frac{1}{S_V} = 0.1 \text{ mA}$$

(B)

$$S_V = 20 \text{ k}\Omega/\text{V}$$

$$I_B = 0.05 \text{ mA}$$

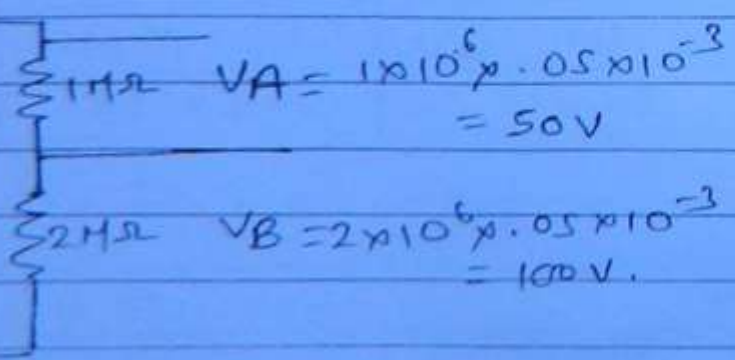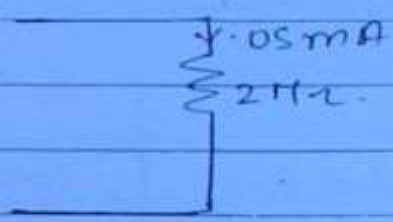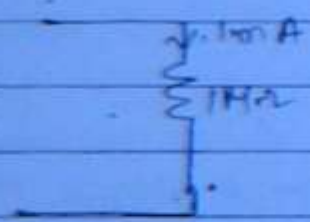

Q32

$$V = 50V.$$

$$S_V = 5K\Omega/V, I_{fs} = 200\mu A$$

$$R_m = 100\Omega$$

(27)

$$R_A + R_m = V S_V \Rightarrow 50 \times 5 = 250K\Omega$$

$$R_S + 100 = 250 \times 10^3$$

$$R_S + 0.1K\Omega = 250K\Omega$$

$$R_S = 249.9K\Omega$$

Q33

$$I_{fs} = 50\mu A$$

$$V = 10V$$

$$R_m = 500\Omega$$

$$R_A + R_m = \frac{V}{I_{fs}} = \frac{10}{50 \times 10^{-6}} \Rightarrow 199.5K\Omega$$

Q34

$$I_{fs} = 200\mu A$$

$$S_V = \frac{1}{200 \times 10^{-6}} \Rightarrow 5K\Omega/V$$

$$\Rightarrow 5\Omega/mV$$

Q37

$$I_m = 1mA$$

$$R_m = 100\Omega$$

$$I = 100mA$$

$$m = \frac{I}{I_m} = 100$$

$$R_{oh} = \frac{R_m}{m-1} = \frac{100}{99} = 1.01\Omega$$

Q31

Q10

$$T_C = 10^\circ C$$

$$K \downarrow = 0.04\% / ^\circ C \rightarrow 10^\circ C \Rightarrow K \downarrow = 0.4\% \quad T_C \downarrow = 0.4\%$$

$$I_d = 0.8mA$$

$$B \downarrow = 0.02\% / ^\circ C \Rightarrow 10^\circ C \Rightarrow B \downarrow = 0.2\% \quad I_d \downarrow = 0.2\%$$


0.2% max

Application of PNMC:-

(28)

Rectifier - Meters:-

① Half wave Rectifier Meter:-

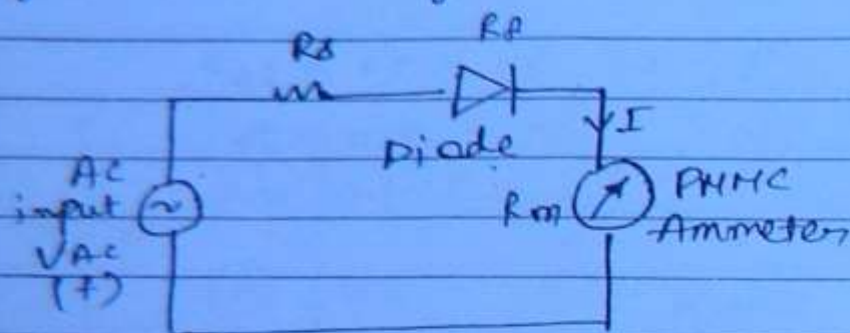

$$V_{AC} = V_m \sin \omega t$$

$$= \sqrt{2} V_{RMS} \sin \omega t$$

$$I = I_{avg} = \frac{V_{avg}}{(R_s + R_f + R_m)}$$


$$\Rightarrow \frac{V_m}{\pi (R_s + R_f + R_m)}$$

$$\Rightarrow \frac{\sqrt{2} V_{RMS}}{\pi (R_s + R_f + R_m)}$$

$$\left[I_1 = I_{avg} = \frac{0.45 V_{RMS}}{(R_s + R_f + R_m)} \right] \text{--- (1)}$$

With DC input :-

Ideal Diode
 $R_f = 0$

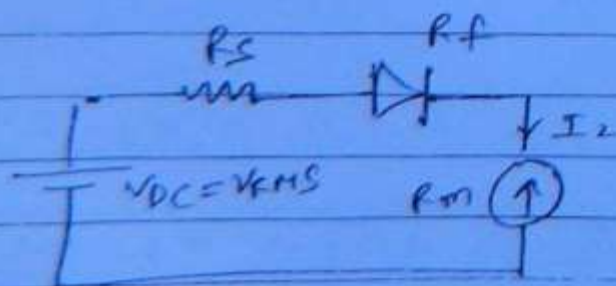


$$I_2 = \frac{V_{RMS}}{(R_s + R_f + R_m)} \quad \text{--- (2)}$$

f from (1) & (2)


$$I_1 = 0.45 I_2$$

$$S_{i ac} = 0.45 S_{i dc}$$

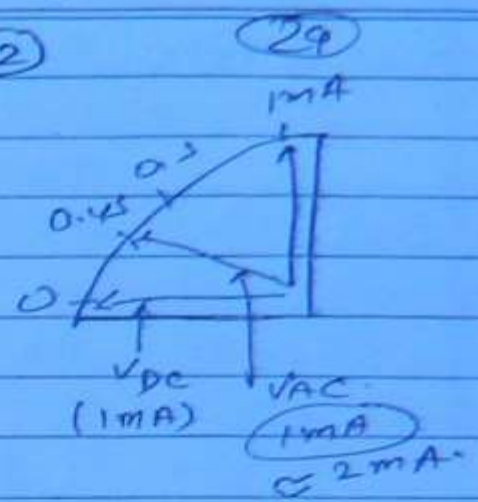

$\Rightarrow S_i =$ current sensitivity.

② Full wave Rectifier Meter:—

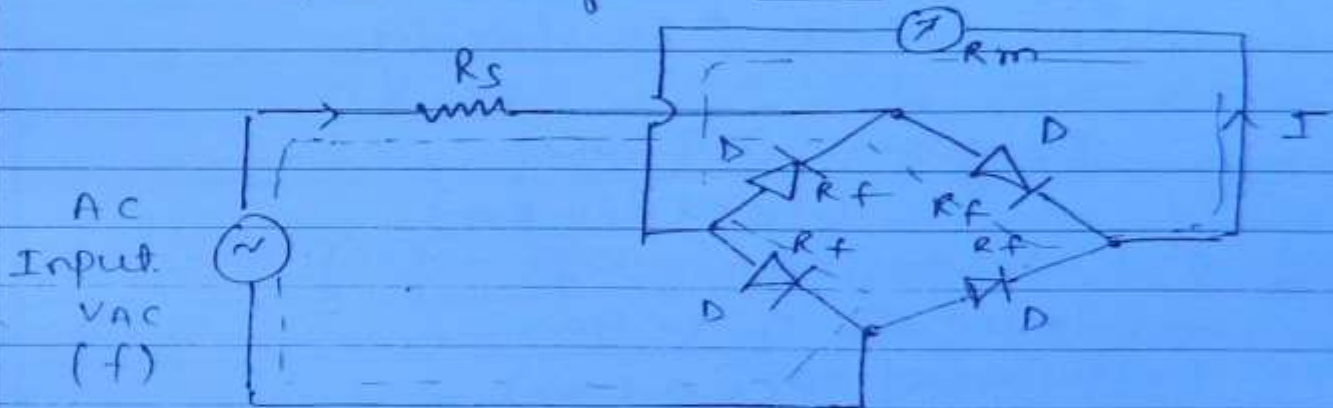

$$V_{ac} = V_m \sin \omega t.$$

$$= \sqrt{2} V_{RMS} \sin \omega t.$$

$$I_1, I_{avg} = \frac{V_{avg}}{(R_s + 2R_f + R_m)}$$

$$\Rightarrow \frac{2 V_m}{\pi (R_s + 2R_f + R_m)}$$

$$\Rightarrow \frac{2\sqrt{2} V_{RMS}}{\pi (R_s + 2R_f + R_m)}$$

$$I_1 = I_{avg} = \frac{0.9 V_{RMS}}{(R_s + 2R_f + R_m)} \quad \text{--- (1)}$$

with DC input \rightarrow

(30)

$$I_2 = \frac{V_{RMS}}{(R_s + 2R_f + R_m)} \quad (2)$$

from (1) and (2)

$$I_1 = 0.9 I_2$$

$$S_i^{ac} = 0.9 S_i^{dc}$$

$\rightarrow S_i = \text{Current Sensitivity}$

$$I_{avg} = \frac{0.9 V_{RMS}}{(R_s + 2R_f + R_m)}$$

$$1 \times 10^{-3} \Rightarrow \frac{0.9 \times 100}{(R_s + 0 + 100)}$$

$$R_s + 100 = 90 \times 10^3$$

$$R_s = 90 \times 10^3 - 100$$

$$\Rightarrow 89.9 \text{ K}\Omega$$

$$I_{avg} = \frac{0.9 V_{RMS}}{(R_s + 2R_f + R_m)}$$

Ignoring R_f & R_m .

$$45 \times 10^{-3} = \frac{0.9 \times 100 \times 10^{-3}}{R_s}$$

$$R_s = 2 \times 10^6 \Omega$$

$$X_C = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi f X_C}$$

Error due to Calibration \rightarrow If a meter is calibrated for a particular waveform eg:- (3)

Sinusoidal. RMS & Avg measurement.

If the same meter is applied with other than sinusoidal waveforms. A meter produces error. This is called error due to calibration. For calculation of these type of error form factor of original waveform (sinusoidal). And the form factor of other than sinusoidal waveform are calculated from these values error is calculated.


$$\% \text{ Error} = E_x = \frac{\text{Measured} - \text{True}}{\text{True}} \times 100$$

$$\Rightarrow \frac{\text{Form factor of original (sinusoidal)} - \text{form factor of other signal}}{\text{form factor of other signal}} \times 100$$

Q


A full wave rectifier meter is calibrated to measure the RMS quantity of the sinusoidal input. For this meter a sawtooth waveform having a peak value of V_m & a time period of T is applied. Find the error in the measurement of RMS value of sawtooth signal.

As

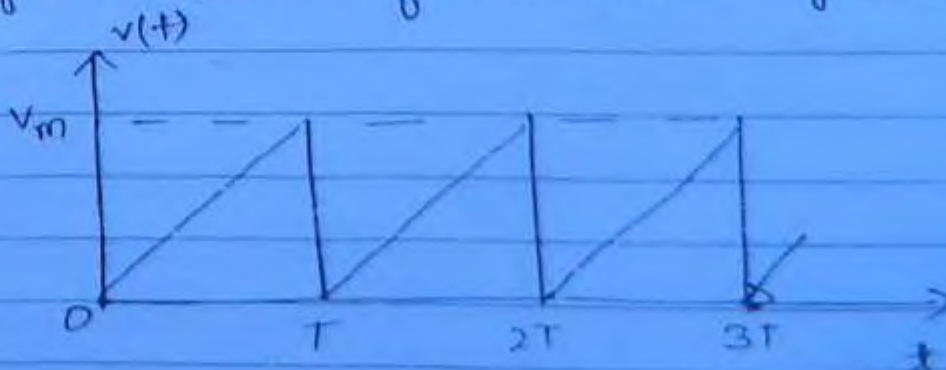

Sinusoidal signal
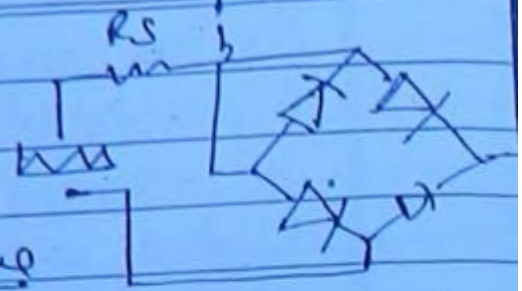
$$\frac{I_{RMS}}{I_{avg}} = 1.11 = \text{form factor} = \text{Measured value}$$



Saw tooth :-

(32)

$$V_{RMS} = \left[\frac{1}{T} \int_0^T v^2(t) dt \right]^{1/2}$$

$$v(t) = \frac{V_m}{T} t$$

$$V_{RMS} = \left[\frac{1}{T} \int_0^T \frac{V_m^2 t^2}{T^2} dt \right]^{1/2}$$

$$\Rightarrow V_m / \sqrt{3}$$

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \int_0^T \frac{V_m t}{T} dt$$

$$\Rightarrow V_m / 2$$

$$\text{form factor} = \frac{V_{RMS}}{V_{avg}} = \frac{V_m / \sqrt{3}}{V_m / 2} \Rightarrow 1.154 = \text{True}$$


$$\% \text{ Error} = \frac{1.11 - 1.154}{1.154} \times 100$$

$$\Rightarrow -3.89\%$$


Moving Im Meter:- [MI]

33

① Attractive MI :-

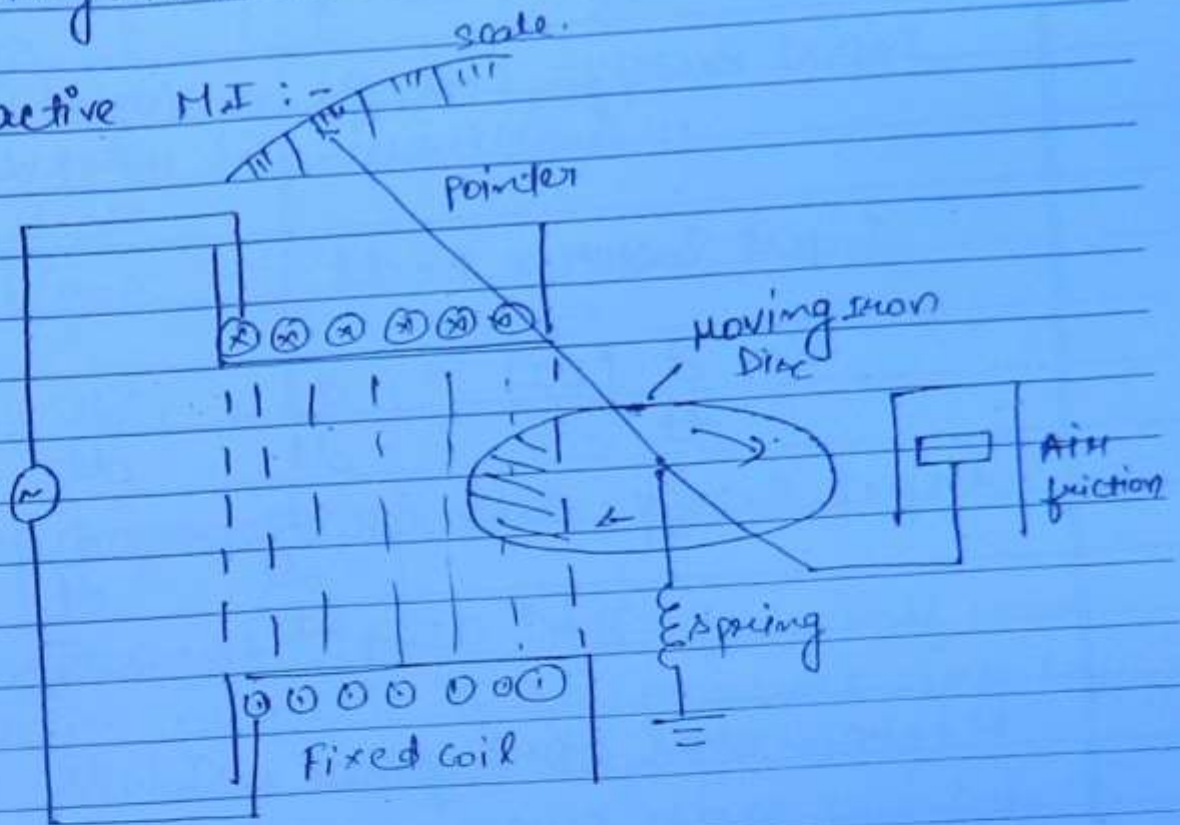

② Repulsive MI :-

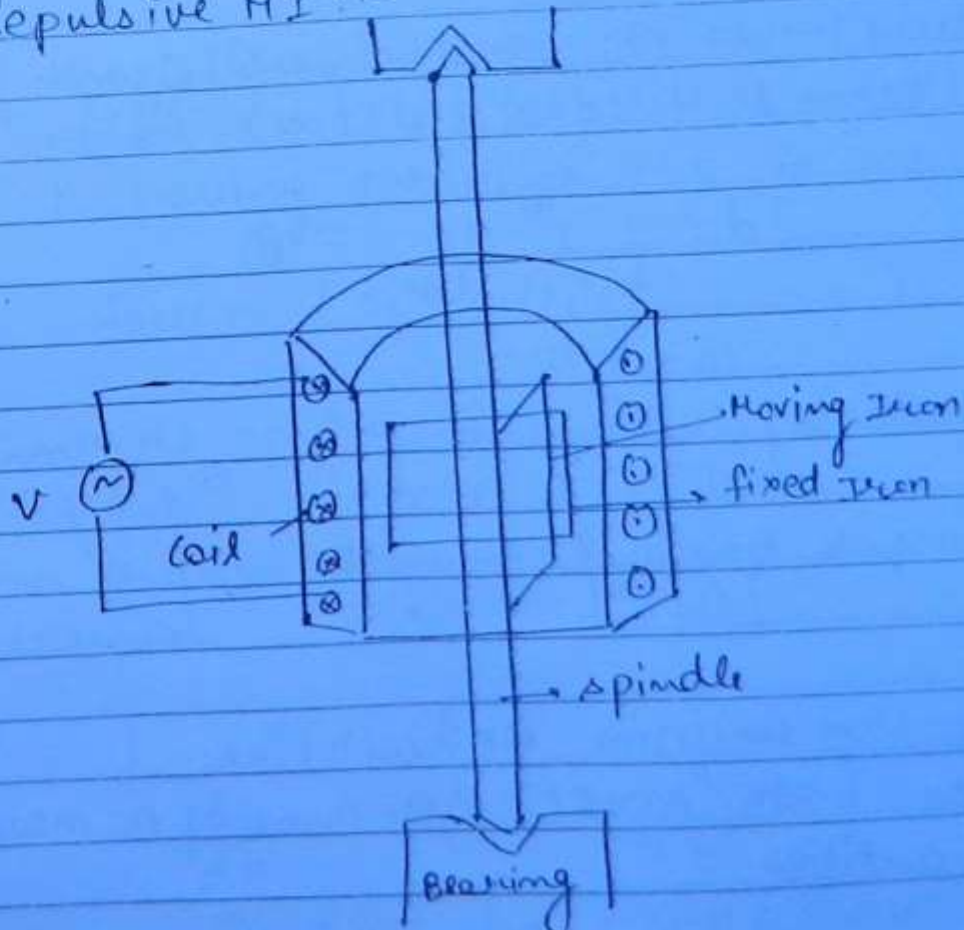

Deflecting Torque (T_d)

(34)

Input Energy = change in stored Energy
+ Mechanical work done.

\rightarrow (1)

$$\text{Input Energy} = \int I dt$$

$$V = \frac{d}{dt} [LI] = L \frac{dI}{dt} + I \frac{dL}{dt}$$

$$\text{Input Energy} = \int I dt \left[L \frac{dI}{dt} + I \frac{dL}{dt} \right]$$

$$\Rightarrow LI dI + I^2 dL \quad - (2)$$

$$\text{Mechanical work done} = T_d \cdot d\theta \quad - (3)$$

$$\text{change in stored Energy} = \frac{1}{2} [I + dI]^2 (L + dL) - \frac{1}{2} I^2 L$$

Substitute (2), (3) & (4) in (1) ignore terms $dL(dI)^2$, $dI(dL)$ terms.


$$T_d = \frac{1}{2} I^2 \frac{dL}{d\theta} \quad - (4)$$

$$T_a = K\theta$$

At balance, $T_c = T_d$


$$K\theta = \frac{1}{2} I^2 \frac{dL}{d\theta}$$

$$\boxed{\theta \propto I^2}$$

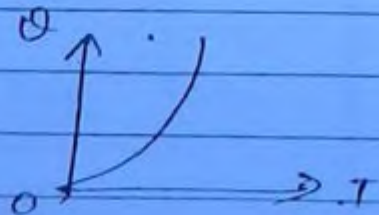

Scale is Non uniform or non linear.

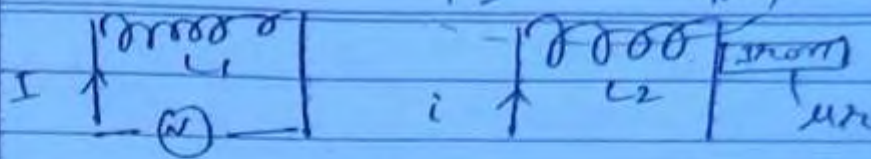Measures both AC & DC. In case of AC measures RMS quantities.



35

$$\begin{array}{l|l} \int \frac{V_2 L \cdot dI}{dt} & L_2 = \frac{N_2^2 \mu_0 \mu_1 A}{l} \\ L_1 = \frac{N_1^2 \mu_0 \mu_1 A}{l} & \Rightarrow L_1 \mu_2 \\ \frac{1}{2} L_1 I_1^2 & \frac{1}{2} L_2 I_2^2 \end{array}$$

Some Important points →

- (i) MI measures $I_{RMS} = I_m / \sqrt{2}$ for a half wave rectifier output. And it measures $I_{RMS} = I_m / \sqrt{2}$ for full wave rectifier output.

For any other waveform shape calculate

$$I_{RMS} = \left[\frac{1}{T} \int_0^T i^2(t) dt \right]^{1/2}$$

If the current $i(t)$

$$i(t) = I_0 + I_1 \sin \omega t + I_2 \sin 2\omega t + \dots$$

is passing through MI it measures

$$I_{RMS} = \sqrt{I_0^2 + \frac{1}{2} (I_1^2 + I_2^2 + \dots)}$$

- (ii) Control spring is used to produce controlling torque.

- (iii) Air friction damping is used to produce damping torque.

$$K = 25 \times 10^{-6}$$

$$\frac{dI}{d\theta} = \left(3 - \frac{20}{42} \right) \times 10^{-6}$$

$$K\theta = \frac{1}{2} I^2 \left(3 - \frac{20}{42} \right) \times 10^{-6}$$

$$W = \frac{1}{2} I^2 \frac{dL}{d\theta}$$

(36)


$$2.5 \times 10^{-6} = \frac{1}{2} \times (I)^2 \times \left(\frac{3-20}{4} \right) \times 10^{-6}$$

$$\boxed{I = 1.2}$$

$$I_{RMS} = \sqrt{I_0^2 + \frac{1}{2} (I_1^2 + I_2^2 + \dots)}$$

$$\Rightarrow \sqrt{(-8)^2 + \frac{1}{2} (6\sqrt{2})^2}$$

$$\Rightarrow 10$$

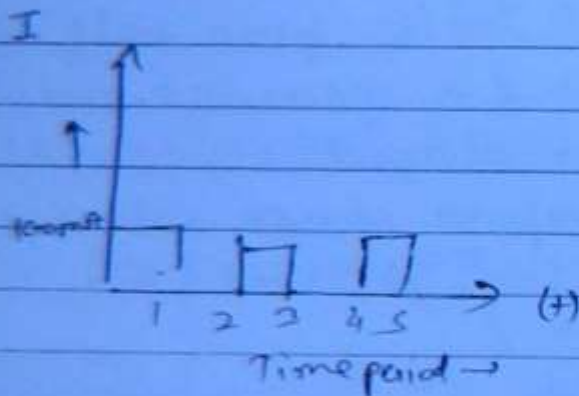

$$I(t) = 100 \text{ mA}, \quad 0 < t < 1$$


$$= 0, \quad 1 < t < 2$$

$$T = 2 \text{ ms}$$

$$I_{RMS} = \left[\frac{1}{T} \int_0^T I^2(t) dt \right]^{1/2}$$

$$\Rightarrow \left[\frac{1}{2} \int_0^1 (100)^2 dt + \int_1^2 0 \cdot dt \right]^{1/2}$$
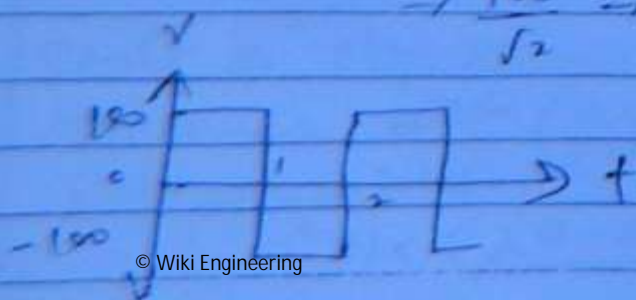
$$\Rightarrow \frac{100}{\sqrt{2}} \Rightarrow 70.7 \text{ mA}$$




$$I_{RMS} = 100 \text{ mA}$$

Errors of M.I

(32)

Frequency Error:-

① Ammeter:-

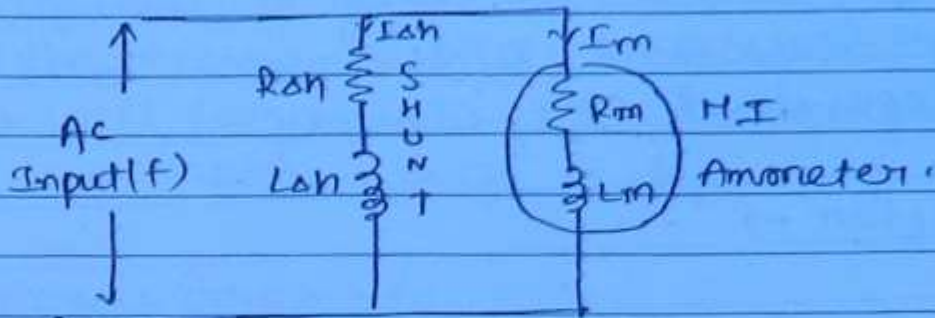

$$I_m = \frac{I \cdot (R_{sh} + j\omega L_{sh})}{R_m + R_{sh} + j\omega(L_m + L_{sh})}$$

$$|I_m| = \frac{I \sqrt{R_{sh}^2 + \omega^2 L_{sh}^2}}{\sqrt{(R_m + R_{sh})^2 + \omega^2 (L_m + L_{sh})^2}} \quad \text{--- (1)}$$

frequency dependent.

$$I_{sh} = \frac{I \cdot \sqrt{R_m^2 + \omega^2 L_m^2}}{\sqrt{(R_m + R_{sh})^2 + \omega^2 (L_m + L_{sh})^2}} \quad \text{--- (2)}$$

$$\frac{(1)}{(2)} = \frac{I_m}{I_{sh}} = \frac{\sqrt{R_{sh}^2 + \omega^2 L_{sh}^2}}{\sqrt{R_m^2 + \omega^2 L_m^2}}$$

$$\Rightarrow \frac{R_{sh}}{R_m} \sqrt{\frac{1 + \omega^2 \left(\frac{L_{sh}}{R_{sh}}\right)^2}{1 + \omega^2 \left(\frac{L_m}{R_m}\right)^2}}$$

$$\text{If } \left[\frac{L_{sh}}{R_{sh}} = \frac{L_m}{R_m} \right] ; \left[\frac{I_m}{I_{sh}} = \frac{R_{sh}}{R_m} \right]$$


↑
Independent of frequency.

(38) $i_1 = 30 \sin 2\pi \times 50 t$, $I_{RMS1} = \frac{30}{\sqrt{2}}$, $f_1 = 50$.

$i_2 = 30 \sin 2\pi \times 100 t$, $I_{RMS2} = \frac{30}{\sqrt{2}}$, $f_2 = 100$


→ If the time constant of the shunt is equal to time constant of the meter. Then an meter is independent of frequency.

2) Voltmeter →

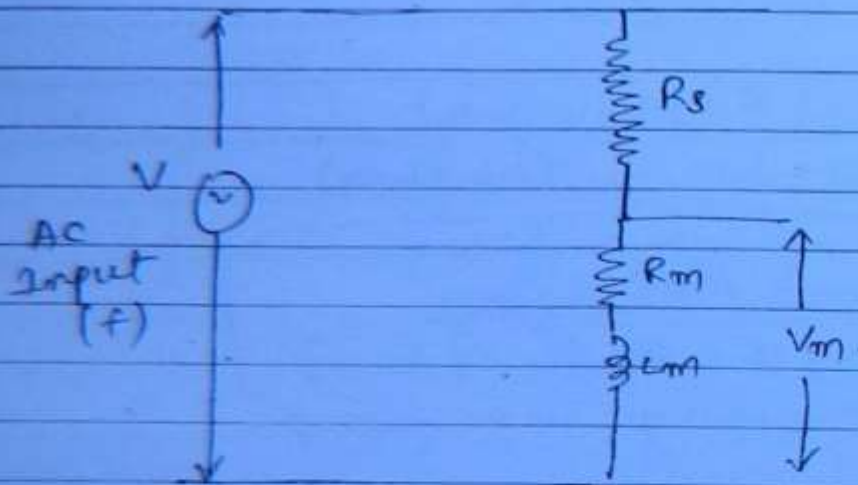

R_s is very high, so its internal inductance neglected.
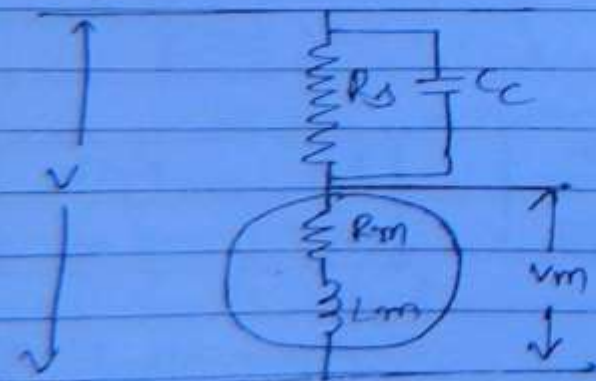
$$V_m = \frac{V \sqrt{R_m^2 + \omega^2 L_m^2}}{\sqrt{(R_s + R_m)^2 + \omega^2 L_m^2}} \rightarrow \text{depends on frequency.}$$




C_c = Compensating Capacitor.

$$C_c = \frac{0.41 L_m}{R_s^2} ; C_c R_s = \frac{0.41 L_m}{R_s} \quad (39)$$

To make voltmeter independent of frequency a compensating capacitor is connected in parallel to the series multiply resistance R_s . This will compensate the inductive reactance of the meter which is depending on frequency.


Hysteresis Error →

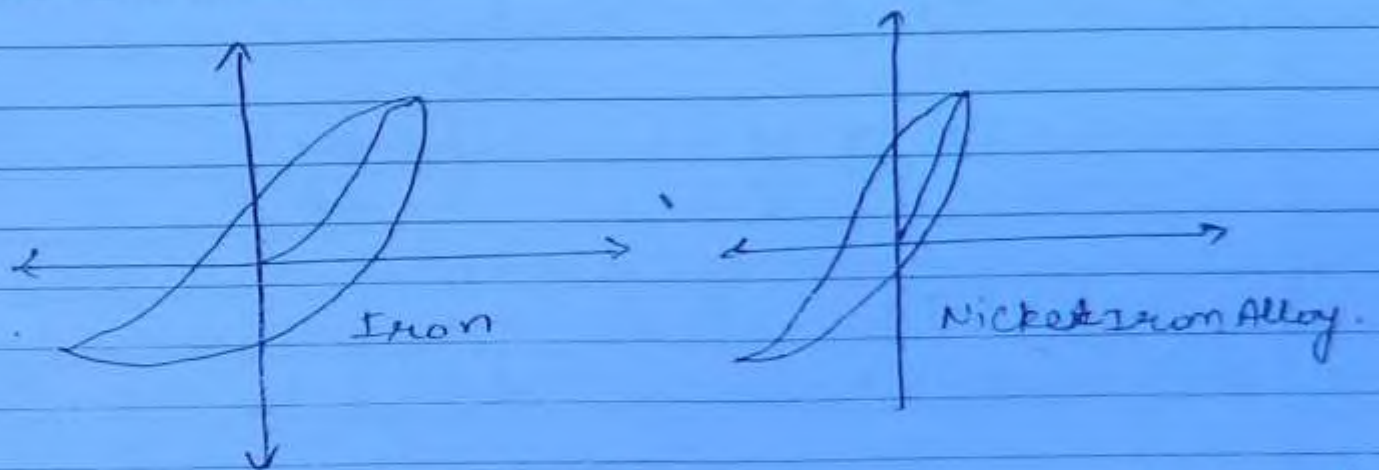

Nickel Iron alloy has low hysteresis area and hence it is used as a rotating iron disc.

Eddy Current Error → At higher frequency it produces constant value of eddy current loss hence M.I. instrument are not used at higher frequency more than 125 Hz.

Electro dynamometer →

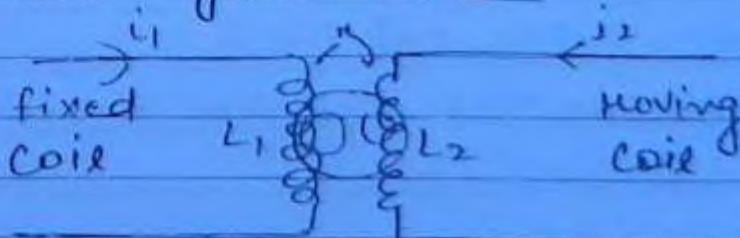

M = Mutual inductance

$$K\theta = \frac{1}{2} I^2 \frac{dL}{d\theta} \quad dM/d\theta$$

Series Aiding: $L = L_1 + L_2 + 2M$
 $L_1, L_2 \Rightarrow$ constants, $M \Rightarrow$ variable

$$\left[\frac{dL}{d\theta} = \frac{2dM}{d\theta} \right]$$

(40)

MI meter:-

$$T_d = \frac{1}{2} I^2 \frac{dL}{d\theta}$$

$$T_d \Rightarrow \frac{1}{2} I \cdot I \cdot \frac{dL}{d\theta}$$

$$T_d \Rightarrow \frac{1}{2} i_1 i_2 \left(\frac{2dM}{d\theta} \right)$$

$$\left[T_d = i_1 i_2 \frac{dM}{d\theta} \right] \rightarrow \text{Electrodynamometer}$$

$$\left[T_c = K\theta \right]$$

At balance,

$$T_c = T_d$$

$$K\theta = i_1 i_2 \cdot \frac{dM}{d\theta}$$

$$\left[\theta \propto i_1 i_2 \right]$$

- ① It measures both AC and DC.
- ② In case of AC measures the RMS Quantity.

Applications \rightarrow


- ① Ammeter

- 2) Voltmeter
- 3) watt-meter
- 4) power factor meter
- 5) Energymeter
- 6) Megger \rightarrow high resistance measurement.
- 7) Power frequency meter.

AC Measurement :-

$$i_1 = I_{m1} \sin(\omega t - \phi)$$

$$i_2 = I_{m2} \sin \omega t$$

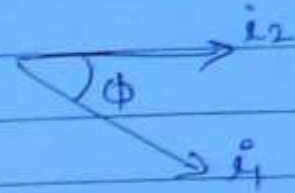

$$T_{d \text{ avg}} = \frac{1}{T} \int_0^T T_d \cdot dt = \frac{1}{T} \int_0^T (i_1 i_2 \frac{dH}{d\theta}) dt$$

for sinusoidal signal $T = 2\pi$

$$T_{d \text{ avg}} = \frac{1}{2\pi} \int_0^{2\pi} I_{m1} I_{m2} \sin \omega t \cdot \sin(\omega t - \phi) d(\omega t + \frac{dH}{d\theta})$$

$$T_{d \text{ avg}} = \frac{I_{m1} I_{m2} \cos \phi}{2} \frac{dH}{d\theta}$$

$$I_{RHS1} = \frac{I_{m1}}{\sqrt{2}} = I_1, \quad I_{RHS2} = \frac{I_{m2}}{\sqrt{2}} = I_2$$

$$T_{d \text{ avg}} = I_1 I_2 \cos \phi \frac{dH}{d\theta}$$

$$T_c = K\theta$$

At balance $T_c = T_d$


$$K\theta = I_1 I_2 \cos \phi \cdot \frac{dH}{d\theta}$$

$$\boxed{\theta \propto I_1 I_2 \cos \phi}$$

Applications →

(42)

① Ammeter:-

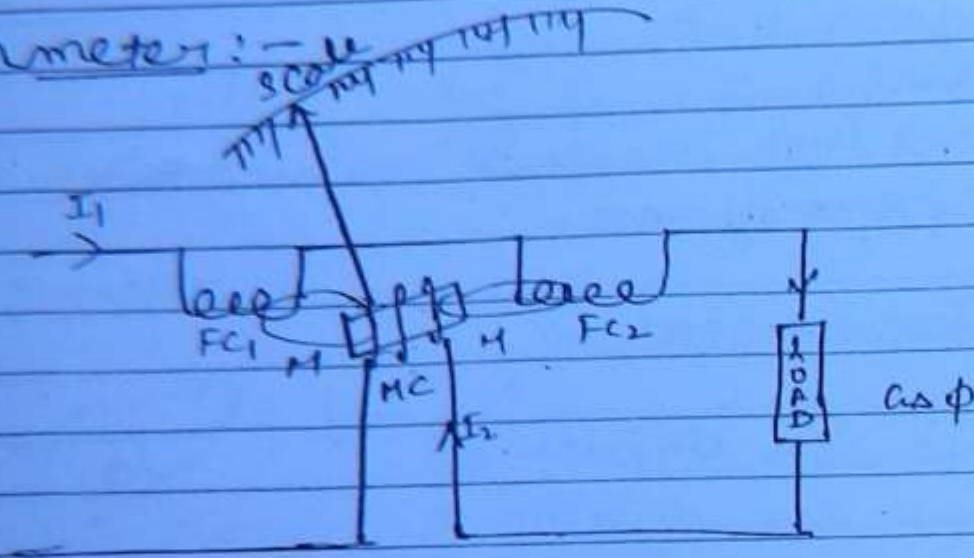

$FC_1, FC_2 \rightarrow$ Fixed coils, $MC \rightarrow$ Moving Coil

$$I_1 = I_2 = I, \quad \theta \propto I_1 I_2$$

$$\therefore \boxed{\theta \propto I^2} \rightarrow \text{RHS Current}$$


② Voltmeter:-

$$I_1 = I_2 = V/R_2$$

$$\theta \propto I_1 I_2$$

$$\theta \propto V^2 / R_2^2$$
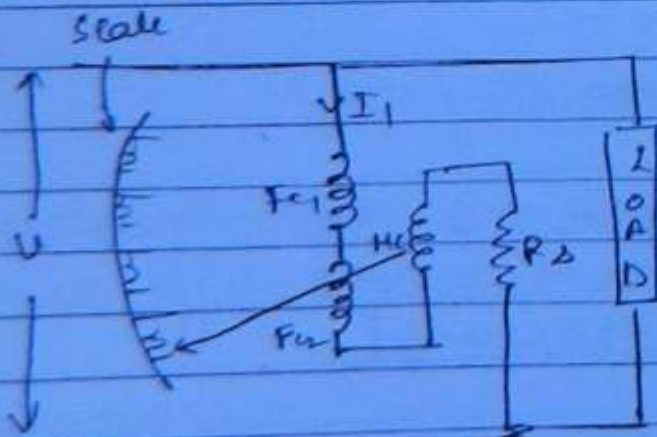
$$\theta \propto V^2 \rightarrow \text{RMS Voltage.}$$




Ammeter is connected in series to the load
 voltmeter is connected in parallel to the load
 the voltmeter is included with series multiple
 resistance (R_s).

(43)

Power Measurement:-

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \phi)$$

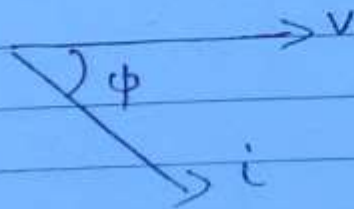

Instantaneous power, $p = vi$

$$\text{Average power, } P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} p(t) \cdot d(\omega t)$$

$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V_m I_m \sin \omega t \cdot \sin(\omega t - \phi) d(\omega t)$$

$$= \frac{V_m I_m \cos \phi}{2}$$

$$\Rightarrow \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi$$

$$P_{avg} = VI \cos \phi$$

$$V = V_{RMS}$$

$$I = I_{RMS}$$

ELECTRODYNAMOMETER WATTMETER:-

$$T_d = I_1 I_2 \cos \phi \cdot \frac{d\theta}{d\phi}$$

$$I_1 = I, \quad I_2 = V/R_s$$

(44)

$$T_d = \frac{VI \cos \phi}{R_s} \cdot \frac{dH}{d\phi}$$

$$T_d = \frac{P_{avg}}{R_s} \cdot \frac{dH}{d\phi}$$

$$\boxed{T_d \propto P_{avg}}$$

$$T_d = T_c$$

$$\frac{P_{avg}}{R_s} \cdot \frac{dH}{d\phi} = K\phi$$


$$\boxed{\phi \propto P_{avg}}$$

- i) wattmeter measures average active power.
- ii) Wattmeter consisting of two fixed coils F_1 & F_2 and these are connected in series to the load to measure the load current. Hence, these coils are called current coil.
- iii) Wattmeter contains moving coils which is provided with internal series multiple resistance. The moving coil is connected in parallel to the load and used to measure potential of source. Hence, moving coil is called potential coil or pressure coil.


∴ A potential coil of the wattmeter is to be highly resistive so that error in measurement of power is minimum.
A potential coil of the energymeter should be highly inductive so that error in the measurement

of energy is minimum.

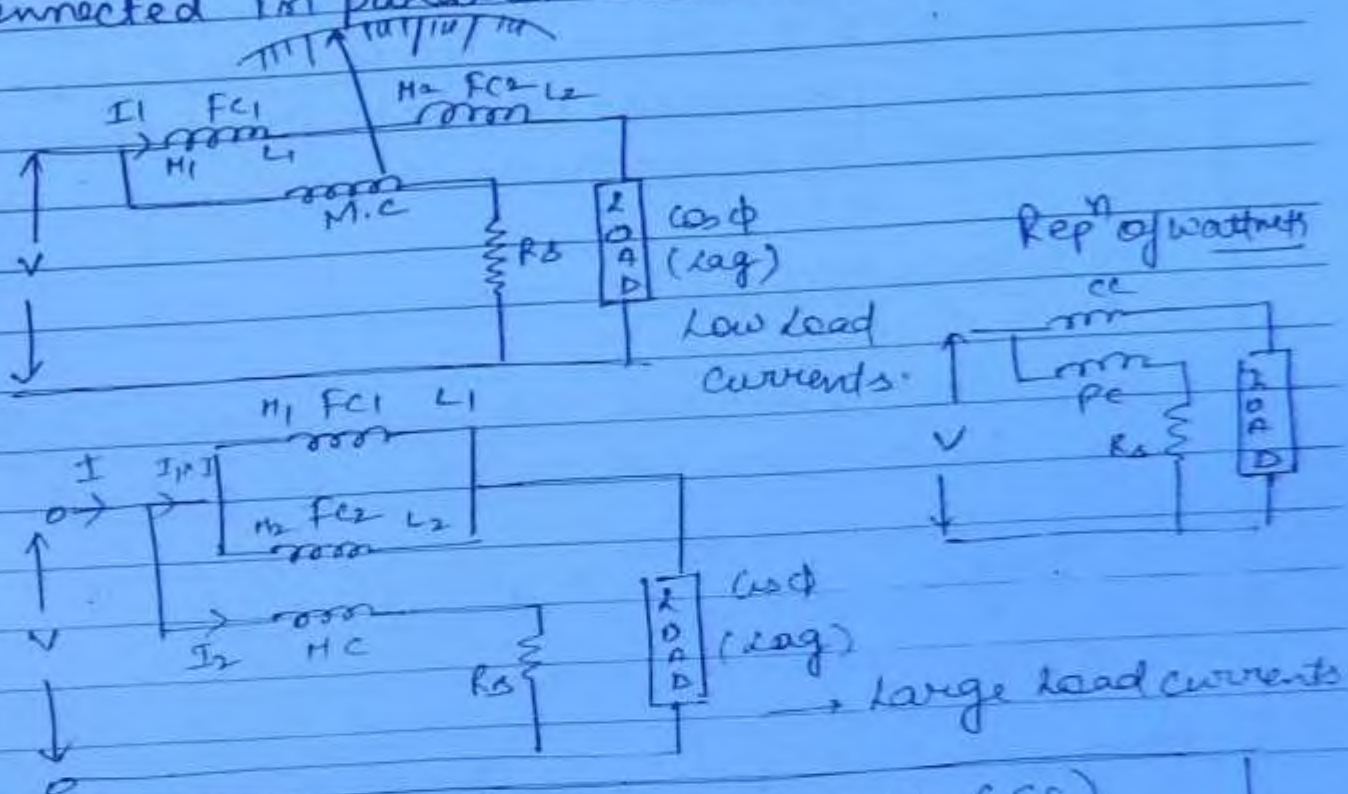For small value of load current's the fixed coil's are connected in series to each other which is in turn connected in series to the load. For large load current's the fixed coil's are connected in parallel to each other.



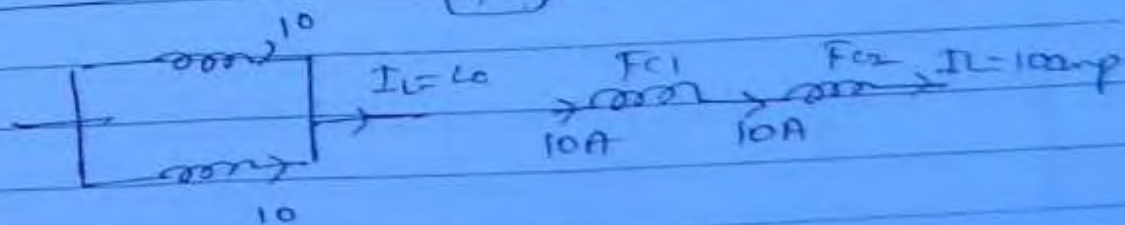- Fixed Coil (FC) = current coil (CC)
- Moving coil (MC) = potential or voltage or pressure coil (PC)



Wattmeter Reading Observations →

- (i) For finding out the Wattmeter reading observe the current flowing through the current coil which is calculated from the supply voltage and load impedance.
- (ii) observe the end terminals of potential coil

Find the angle between potential coil current or voltage to the current coil current by using load power factor in case of 1 ϕ circuit but in case of 3 ϕ ckt ^{angle is} it is calculated by using phasor diagram.

If CT & PT are present in the circuit the ratio of CT & PT are to be used for calculation of present available voltage and current measured by the wattmeter.

(46)

Pavg calculation if Harmonic present \rightarrow


$$v = V_0 + V_1 \sin(\omega t + \phi_1) + V_2 \sin(2\omega t + \phi_2) + \dots$$

$$i = I_0 + I_1 \sin(\omega t + \theta_1) + I_2 \sin(2\omega t + \theta_2) + \dots$$

$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} v i \, dt$$

$$P_{avg} = V_0 I_0 + \frac{1}{2} [V_1 I_1 \cos(\phi_1 - \theta_1) + V_2 I_2 \cos(\phi_2 - \theta_2) + \dots]$$

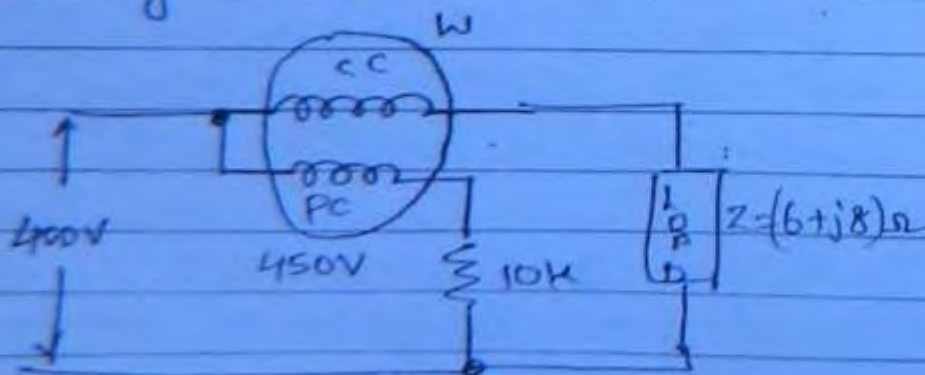Find the wattmeter readings from the following ckt?



$$P = VI \cos \phi$$


$$V = 400 \text{ V}$$

$$I = \frac{400}{\sqrt{6^2 + 8^2}} = \frac{400}{10} = 40 \text{ A}$$

$$\cos \phi = 6/10 \Rightarrow 0.6$$

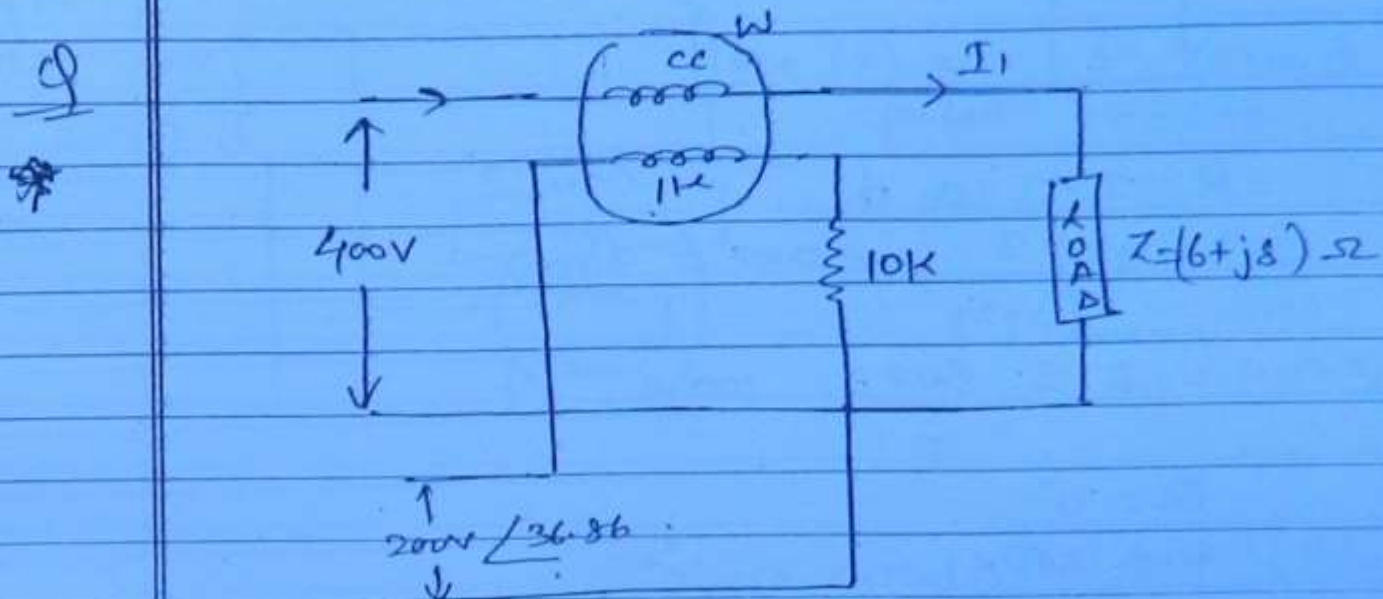(42)

$$P = 400 \times 40 \times \frac{0.6}{1} \Rightarrow 9600 \text{ W} \Rightarrow 9.6 \text{ kW}$$



$$P = VI \cos \phi$$

$$V = 200$$

$$I = \frac{400}{\sqrt{6^2 + 8^2}} = 40 \text{ A}$$


$$\cos \phi = \frac{6}{10} \Rightarrow 0.6$$


$$P = 200 \times 40 \times 0.6 = 4.8 \text{ kW}$$

$$\phi = 36.86 + 53.14^\circ \Rightarrow 90^\circ$$

$$P = VI \cos 90^\circ$$

$$\Rightarrow 0 \text{ Watt}$$

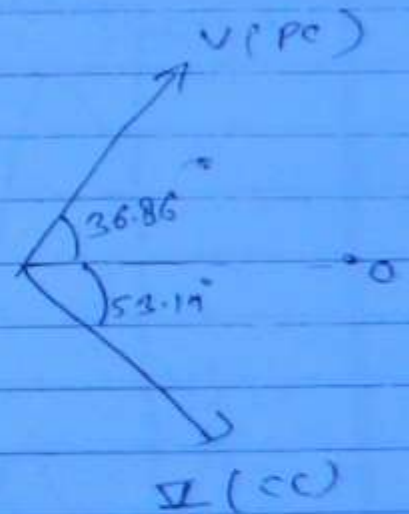

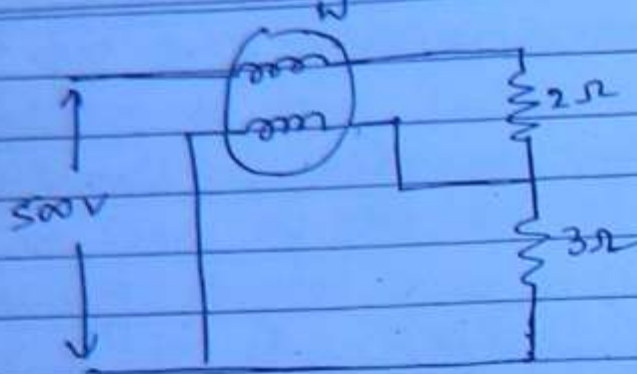

Q8


$$P = VI \cos \phi$$

$$V = \frac{3}{3+2} \times 500 = 300V$$

$$I = \frac{500}{5} = 100A$$

$$\phi = 0^\circ$$
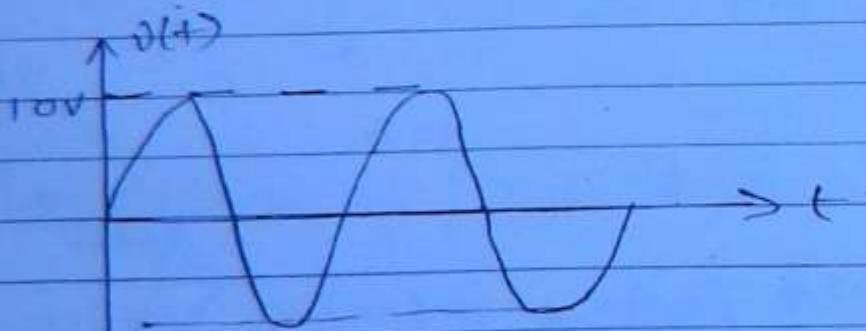
$$P = 300 \times 100 \times \cos 0^\circ = 30kW$$



$v(t)$ is applied to the potential coil. $i(t)$ is applied to the current coil. Find the wattmeter reading?


$$P = VI \cos \phi$$

$$\Rightarrow \frac{10}{\sqrt{2}} \cdot \frac{5}{\sqrt{2}} \cos 30^\circ$$

$$P = 21.65 \text{ W}$$

(49)

Q21

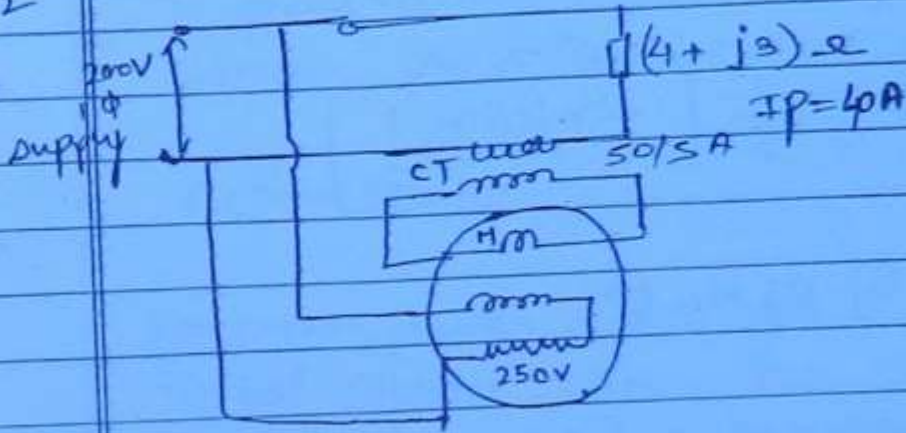

$$P = VI \cos \phi$$

$$V = 200$$

$$I = I_s$$

$$I_P = \frac{200}{\sqrt{16+9}} \Rightarrow 4 \text{ A}$$

$$I_s = 4 \text{ A} \times 5/50$$

$$\Rightarrow 4 \text{ A}$$


$$\phi = \tan^{-1}(3/4)$$

$$P = VI \cos \phi$$

$$\Rightarrow 200 \times 4 \times \cos[\tan^{-1}(3/4)]$$

$$P \Rightarrow 640 \text{ W}$$

Q22

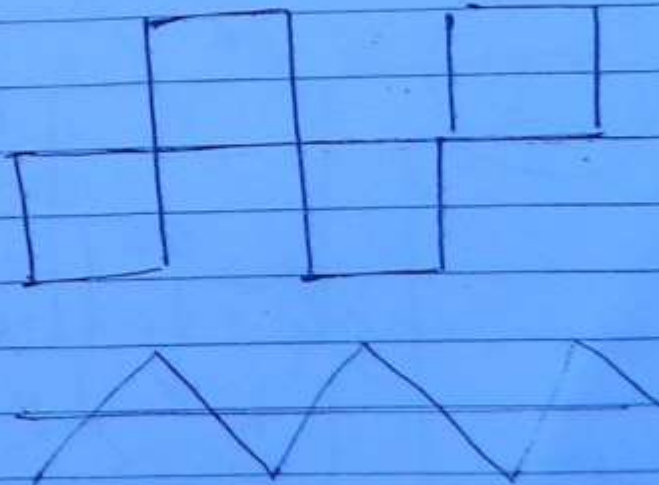

$$V = 10 + 2 \sin(2\omega t + 60^\circ) \rightarrow \text{P.C}$$

$$i = 5 + 3 \sin(\omega t + 30^\circ) + (1.5) \sin(2\omega t + 15^\circ) \rightarrow \text{C.C}$$

$$P_{\text{avg}} = 10(5) + \frac{1}{2} \left[2(0) \cos(\quad) + 2 \times 1.5 \cos(60 - 15) \right]$$

$$\Rightarrow 50 + \frac{1}{2} \left[\frac{2 \times 1.5 \times 1}{\sqrt{2}} \right]$$


$$\Rightarrow 51.06 \text{ watt}$$

Blondel's Theorem \rightarrow For measurement of power in case of n -phase balanced system. The min^m no of wattmeter required is $(n-1)$.

For Measurement of 3 ϕ power by ~~two~~ we require 2 wattmeter.

Measurement of 3 ϕ power by Two Wattmeter Method:-

1) Star load :-

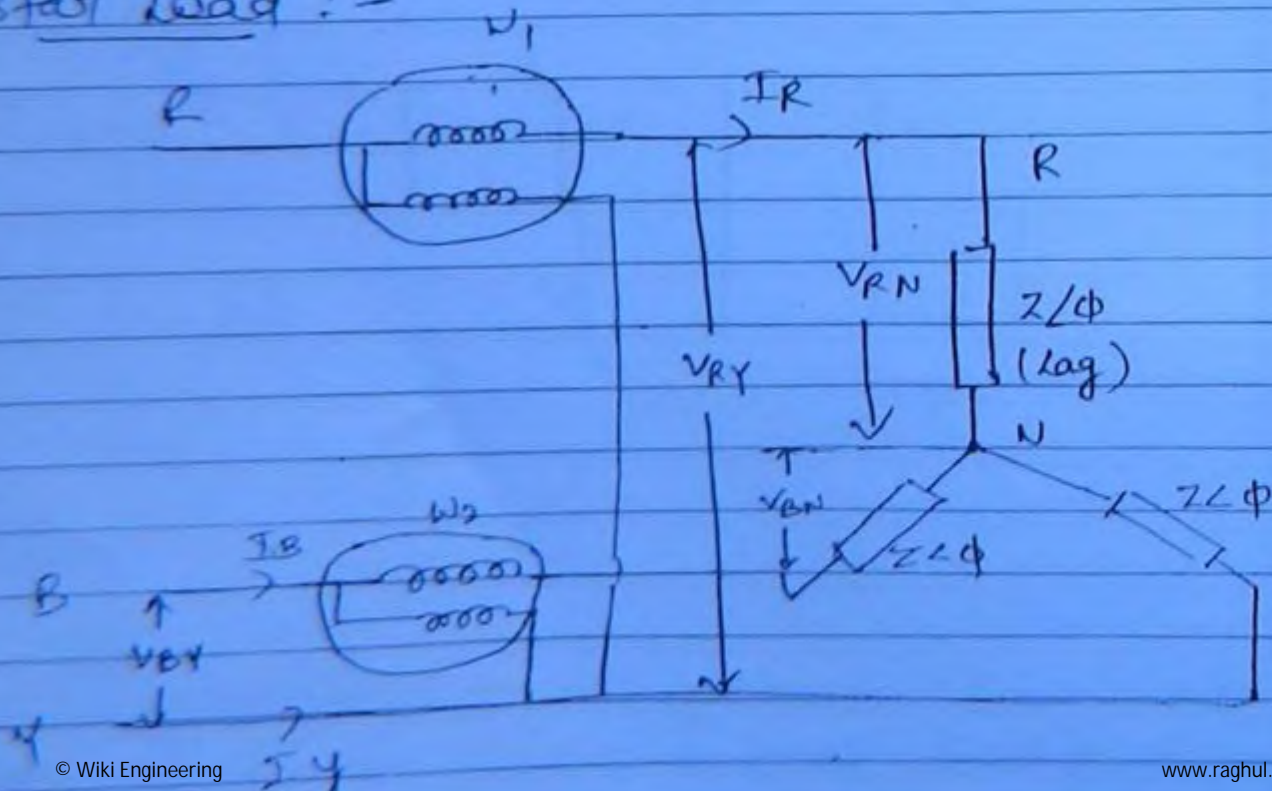

For Star Load :-

$$V_L = \sqrt{3} V_{ph}, \quad I_L = I_{ph}$$

Line voltage (V_L) = V_{RY}, V_{YB}, V_{BR} .

phase voltage (V_{ph}) = V_R, V_Y, V_B .

Line or phase current's $\Rightarrow I_R, I_Y, I_B$.

Active Power :-

Per phase power, $P_{ph} = V_{ph} I_{ph} \cos \phi$.

Total 3 phase power, $P = 3 V_{ph} I_{ph} \cos \phi$.


Reactive Power :-

Per phase $\Rightarrow Q_{ph} = V_{ph} I_{ph} \sin \phi$.

Total 3 ϕ power $\Rightarrow Q = 3 V_{ph} I_{ph} \sin \phi$.

$$W_1 = V_{RY} I_R \cos \angle V_{RY} \& I_R$$

$$V_{RY} = V_R - V_Y$$

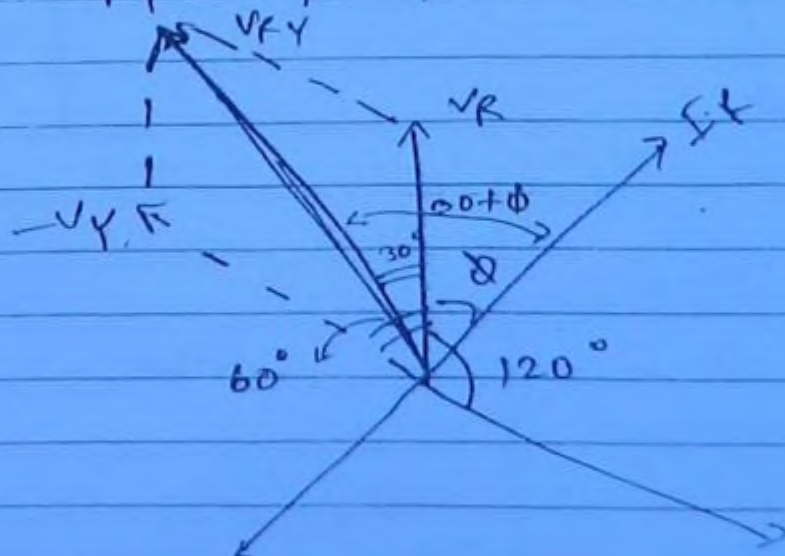


$$W_1 = V_L I_L \cos (30 + \phi)$$

$$W_2 = V_{BY} I_B \cos \angle V_{BY} I_B$$


(52)

$$V_{BY} = V_B - V_Y$$

$$W_2 = V_L I_L \cos(30 - \phi)$$

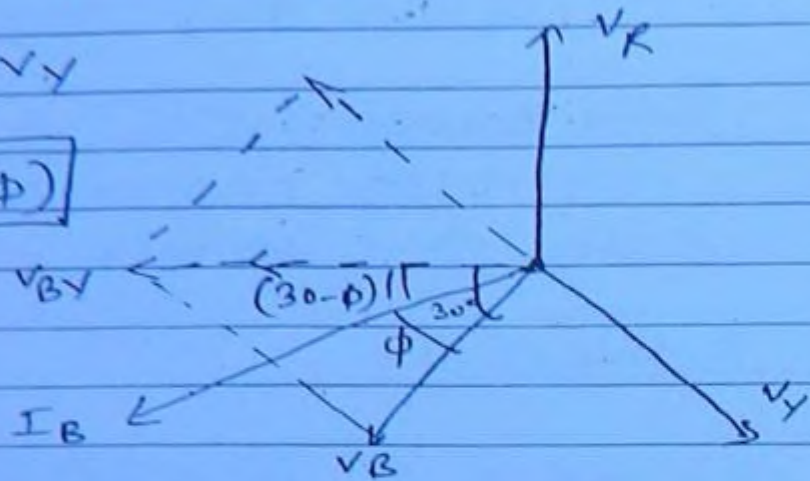

Delta load :-

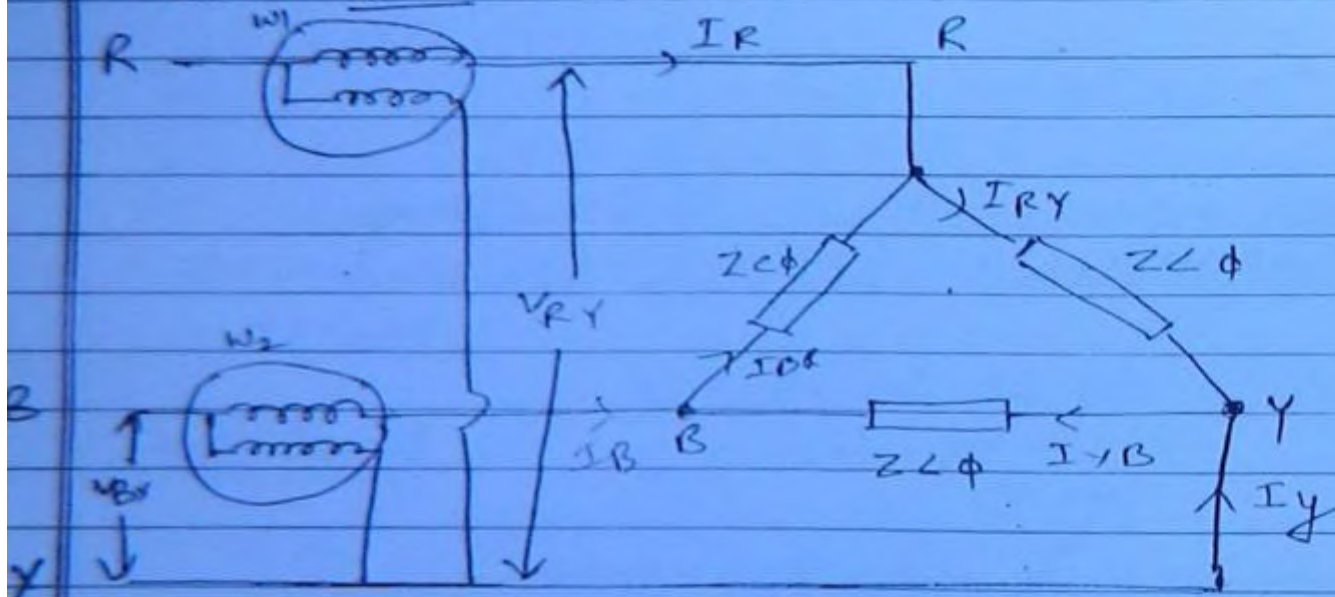

For Δ

$$I_L = \sqrt{3} I_{ph}$$

$$V_L = V_{ph}$$

Line Currents \rightarrow

$$I_L = I_R, I_Y, I_B$$

Phase Current's \rightarrow

$$I_{ph} = I_{RY}, I_{YB}, I_{BR}$$

Line or phase voltages

(S3)

V_{RY}, V_{YB}, V_{BR}

Node R

$$I_R + I_{BR} = I_{RY}$$

$$I_R = I_{RY} - I_{BR}$$

Node Y

$$I_Y + I_{RY} = I_{YB}$$

$$I_Y = I_{YB} - I_{RY}$$

Node B


$$I_B + I_{YB} = I_{BR}$$

$$I_B = I_{BR} - I_{YB}$$

$$W_1 = \underline{V_{RY}} I_R \cos \angle V_{RY} \& I_R$$


$$I_R = I_{RY} - I_{BR}$$
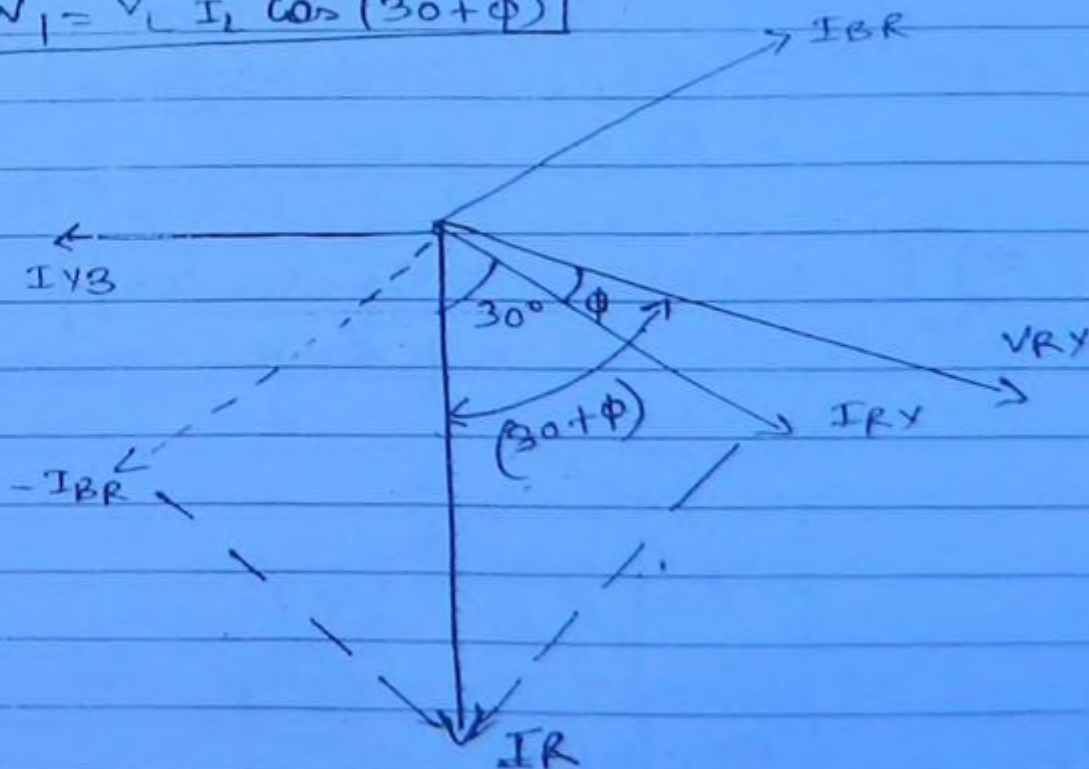
$$\boxed{W_1 = V_L I_L \cos(30^\circ + \phi)}$$



$$W_2 = V_{BY} I_B \cos \angle V_{BY} \& I_B \quad (S4)$$

$$I_B = I_{BR} - I_{YB}$$

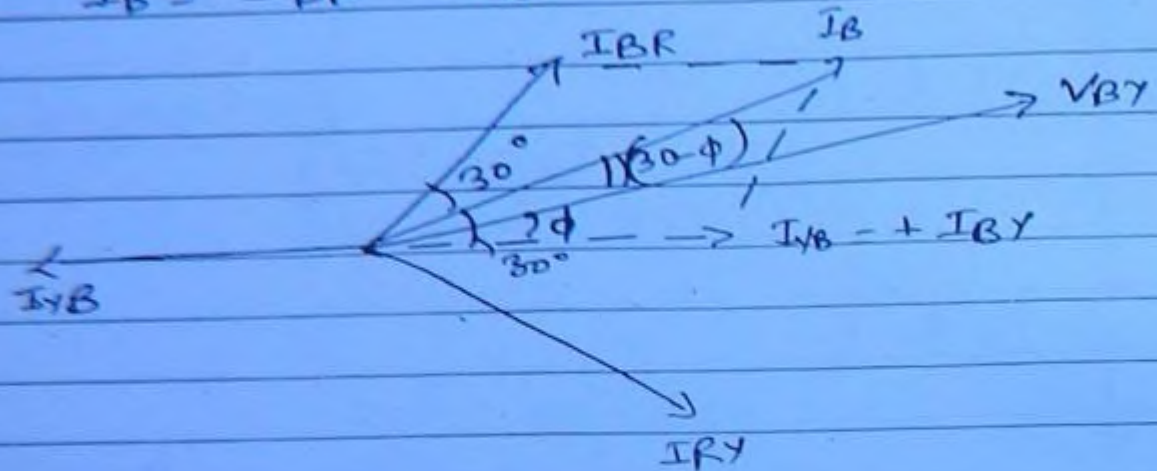


$$W_2 = V_L I_L \cos(30^\circ - \phi)$$


Active Power (P): -

$$\begin{aligned} W_1 + W_2 &= V_L I_L [\cos(30^\circ + \phi) + \cos(30^\circ - \phi)] \\ &= V_L I_L [2 \cos 30^\circ \cos \phi] \\ &= \sqrt{3} V_L I_L \cos \phi \end{aligned}$$
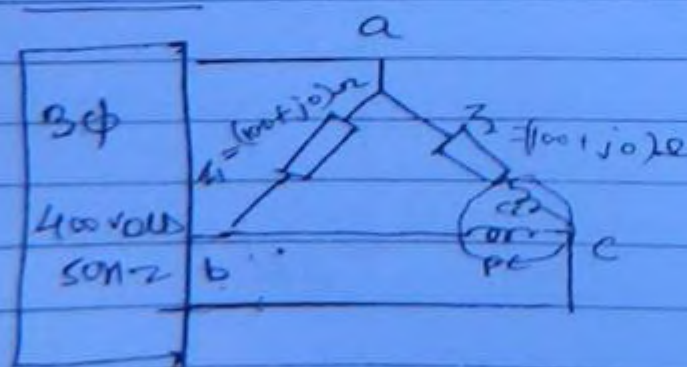
$$\begin{aligned} P &= W_1 + W_2 = 3 V_{ph} I_{ph} \cos \phi \\ &= 3 \phi \text{ Active power.} \end{aligned}$$




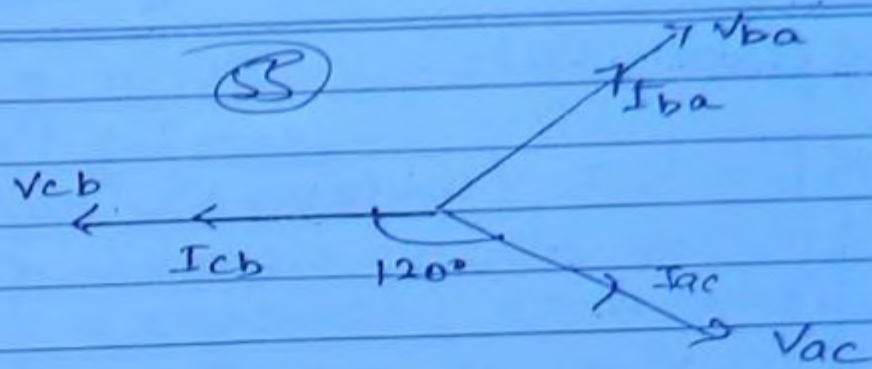W₅ V_{cb} I_{ac} cos \angle v_{cb} & I_{ac}




$$W = \frac{400 \times 400 \times \cos 120^\circ}{100}$$

$$\Rightarrow 800 \text{ W.}$$

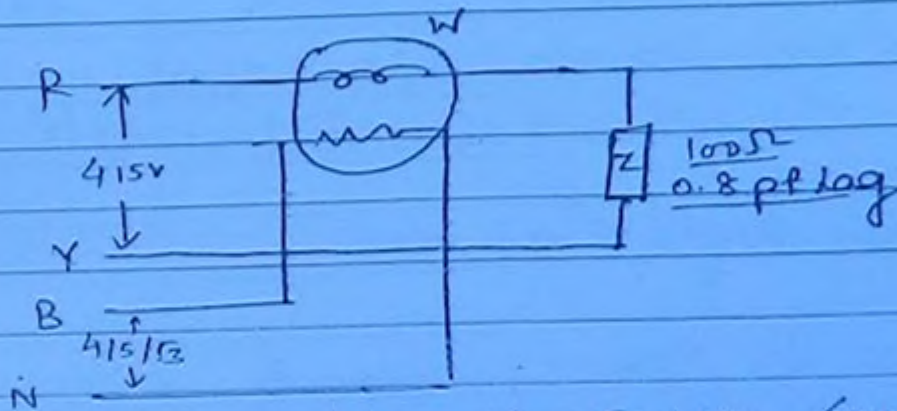
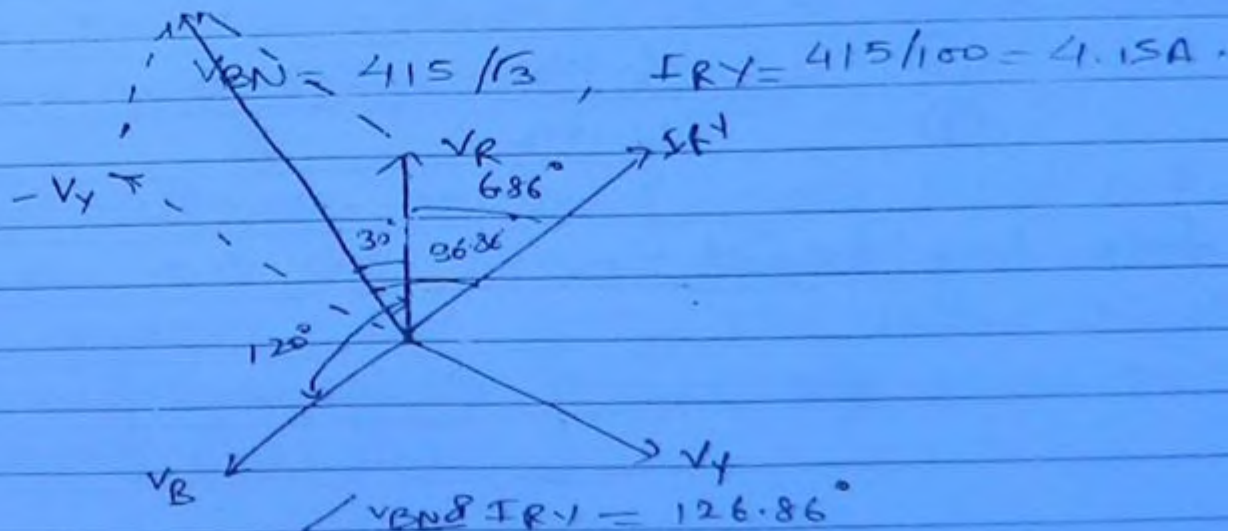
$$W = V_{BN} I_{RY} \cos \angle V_{BN} I_{RY}$$



$$W = 415/\sqrt{3} \times 4.15 \times \cos(126.86^\circ)$$

$$\Rightarrow -597 \text{ W}$$

Reactive power (Q):-

(56)

$$|W_1 - W_2| = V_L I_L [\cos(30^\circ + \phi) - \cos(30^\circ - \phi)]$$
$$\Rightarrow V_L I_L (2 \sin 30^\circ \sin \phi)$$

$$|W_1 - W_2| = V_L I_L \sin \phi = \sqrt{3} V_{ph} I_{ph} \sin \phi$$
$$\Rightarrow \sqrt{3} Q_{ph}$$

$$Q_{ph} = \frac{|W_1 - W_2|}{\sqrt{3}}$$

3 ϕ Reactive power $Q = 3 Q_{ph}$

$$Q = \sqrt{3} (W_1 - W_2)$$

Power factor Angle (ϕ) :-

$$W_1 - W_2 = \sqrt{3} V_{ph} I_{ph} \sin \phi \quad - (1)$$

$$W_1 + W_2 = 3 V_{ph} I_{ph} \cos \phi \quad - (2)$$

$$\frac{(1)}{(2)} = \frac{W_1 - W_2}{W_1 + W_2} = \frac{\tan \phi}{\sqrt{3}}$$

for Lag load :-

$$\phi = \tan^{-1} \left[\frac{\sqrt{3} (W_1 - W_2)}{(W_1 + W_2)} \right]$$

for lead load :-

$$\phi = - \tan^{-1} \left[\frac{\sqrt{3} (W_1 - W_2)}{(W_1 + W_2)} \right]$$

Reading of W_1, W_2 for different load power factors:-

(57)

ϕ	$\cos \phi$	W_1 $V_L I_L \cos(30+\phi)$	W_2 $V_L I_L \cos(30-\phi)$	W $W_1 + W_2$	Observation
0°	1	$\frac{\sqrt{3}}{2} V_L I_L$	$\frac{\sqrt{3}}{2} V_L I_L$	$\sqrt{3} V_L I_L$	Both wattmeters show same so $\cos \phi = 1$ $W_1 = W_2$
30°	0.866	$V_L I_L / 2$	$V_L I_L$	$\frac{3}{2} V_L I_L$	$W_2 = 2W_1$
60°	0.5	0	$\frac{\sqrt{3}}{2} V_L I_L$	$\frac{\sqrt{3}}{2} V_L I_L$	$W_1 = 0$ $W_2 = W$
90°	0	$-V_L I_L / 2$	$V_L I_L / 2$	0	$W_1 = -ve$ $W_2 = +ve$

Note:- If one of the wattmeter, shows negative value, reverse either CC or PC terminals and Record with negative sign.

→ In two wattmeter method if the load p.f is between 0 to 0.5 then one of the wattmeter show negative value bcoz the phase angle b/w voltage & current is more than 90° ($\cos(90+\phi) = -ve$).

§ In the measurement of power on balanced load by two wattmeter method in a 3 ϕ ckt readings to the wattmeter are 3 kW & 1 kW
a) respectively the latter being app obtain after reversing the connection to the current coil. The p.f of the load is

a) 0.277 b) 0.277 c) 0.554 d) 0.866

$$W_1 = 3 \text{ kW}$$

$$W_2 = -1 \text{ kW}$$

$$\phi = \tan^{-1} \sqrt{3} \left(\frac{3 - (-1)}{3 + (-1)} \right)$$

$$\Rightarrow \tan^{-1} \sqrt{3} \left(\frac{4}{2} \right)$$


$$\Rightarrow \tan^{-1} (2\sqrt{3})$$

$$\Rightarrow \boxed{\cos \phi = 0.277}$$

Errors in wattmeter \rightarrow

Error due to Connection : -

Potential coil is on source side : -

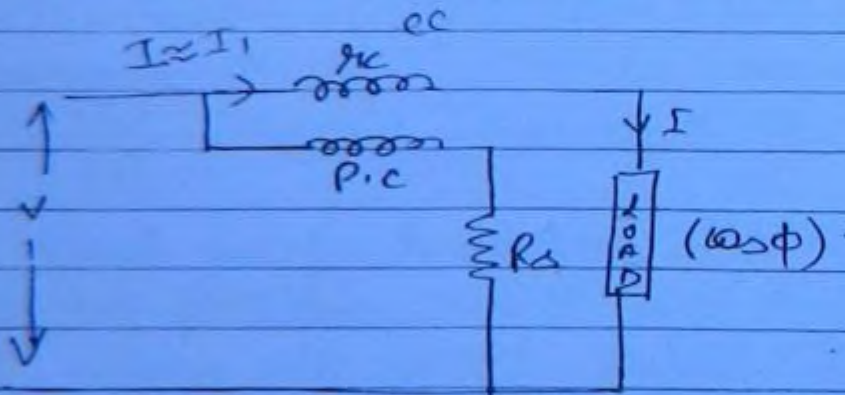

R_s is large hence I_2 is negligible

R_c = C.C internal resistance .

Measured power P_m = True load power (P_T) +
power loss in c.c resistor (R_c)

$$\boxed{P_m = P_T + I^2 R_c}$$


$$\% \text{ Error} = \frac{P_m - P_T}{P_T} \times 100.$$

$$\% \text{ Error} = \frac{I^2 R_c}{P_T} \times 100$$

(59)

Note:- Error is low if load if I is small. Hence this is used for low load currents. (oc test)

b) P.C on load side:-

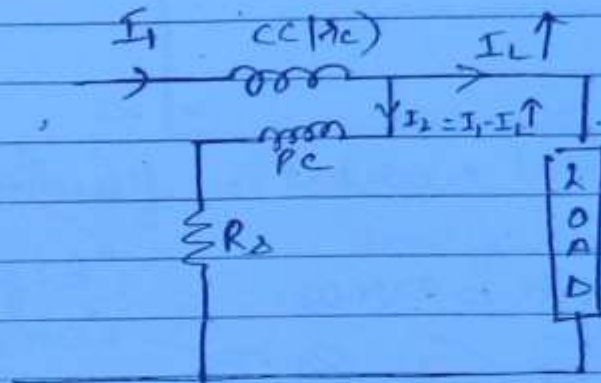

Power loss in R_c is very small compared to R_L loss.

$$P_m = P_T + \text{power loss in PC Resistance } (R_s)$$

$$P_m = P_T + I_2^2 R_s ; I_2^2 R_s = V^2 / R_s$$


$$\% \text{ Error} = E_r = \frac{P_m - P_T}{P_T} \Rightarrow \frac{I_2^2 R_s}{P_T} \times 100$$

Note:- E_r is low if I_2 is small. ($I_2 = I_1 - I_L$). If I_2 is large I_2 is small. Hence used for load currents. (SC test's).

Error's are equal.

$$I^2 R_c = \frac{V^2}{R_s}$$

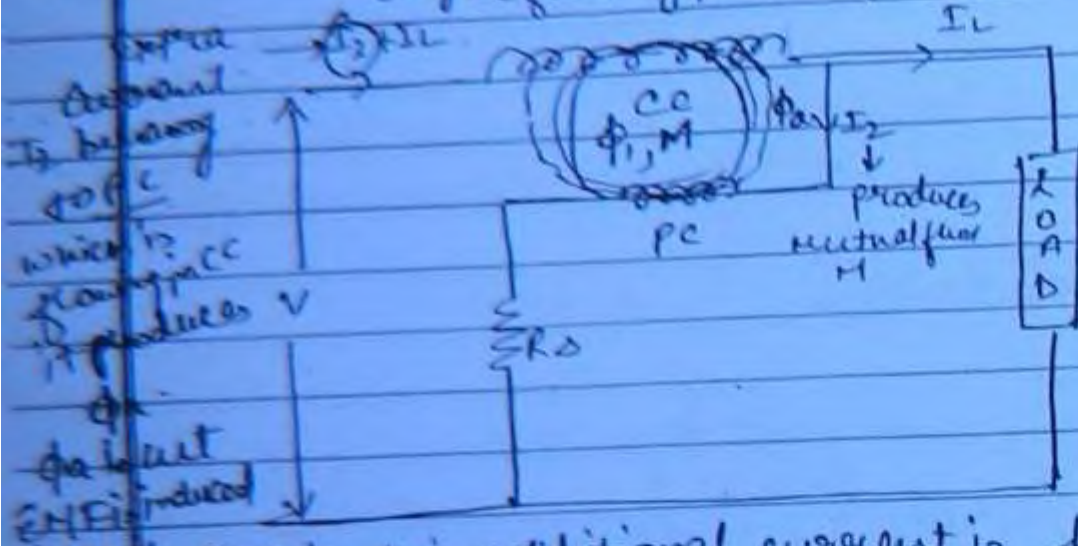
2) Error due to P.C Current flowing incc:-
 only I_L flowing producing flux ϕ , (66)



for compensating of this error.

(Bifilar winding) Compensating coil.

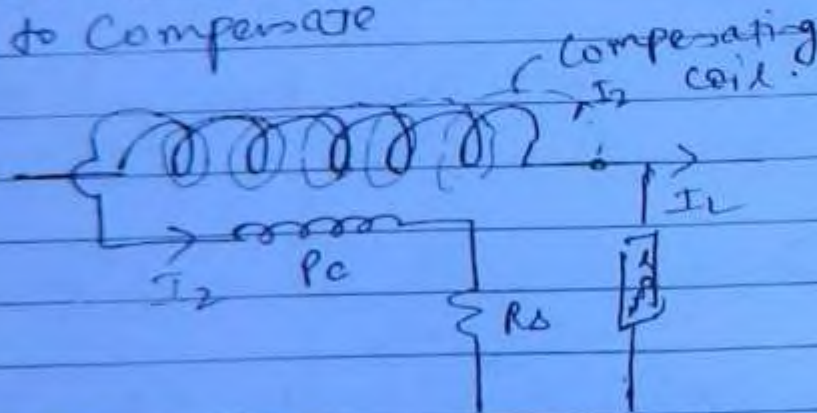cc carries a additional current $I_2 \rightarrow \phi_a$ ϕ_a to compensate





To compensate current in the potential coil.

→ Compensating coil is connected in series to the potential coil to reduce the power loss in the potential coil due to potential coil current flowing in the current coil.

3)

Errors due to potential Coil Inductance (L_P) without Inductance in P.C.:- [Highly Resistive]


(61)

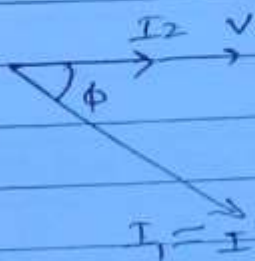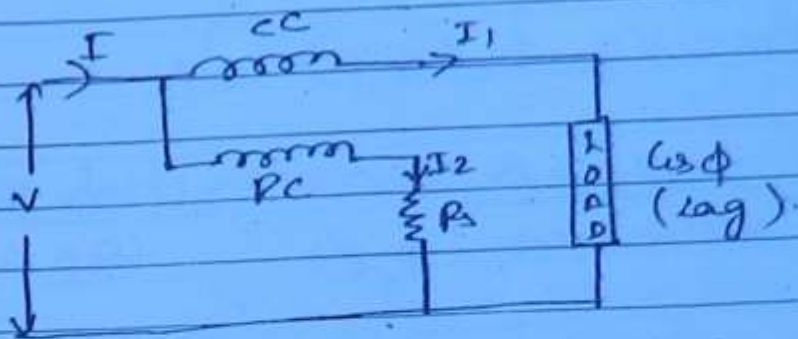

$$T_d = \frac{VI}{R_s} \cos \phi \cdot \frac{dM}{da}$$

$$\text{True power } P_T = VI \cos \phi$$

with Inductance of P.C.:-

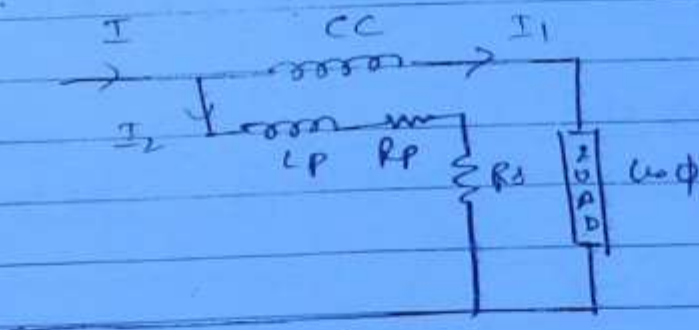


Inductance of P.C. = L_P .


Resistance of P.C. = R_P ($R_P \ll R_s$)

series resistance = R_s
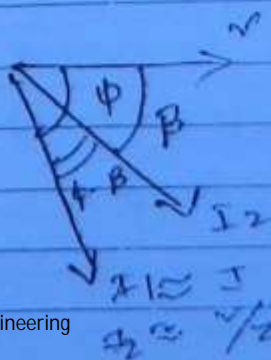
$$\text{Impedance Angle of P.C.} \Rightarrow \beta = \tan^{-1} \left(\frac{\omega L_P}{R_s} \right)$$


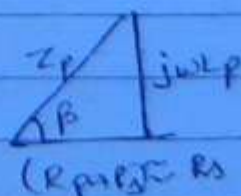
$$T_d \propto I_1 I_2 \cos(\phi + \beta) \frac{dM}{da}$$



$$\cos \beta = \frac{R_s}{Z_P}$$

$$\left[\frac{1}{Z_P} = \cos \beta \right]$$

$$T_d \propto \frac{VI \cos(\phi - \beta) \cos \beta}{R_e} \left(\frac{dM}{d\phi} \right) \quad (62)$$

cosine of
power

$$P_m = VI \cos(\phi - \beta) \cdot \cos \beta$$

$$\frac{P_T}{P_m} = \frac{VI \cos \phi}{VI \cos \beta \cos(\phi - \beta)} = \frac{\cos \phi}{\cos \beta \cdot \cos(\phi - \beta)}$$

$$P_T = P_m \cdot \frac{\cos \phi}{\cos \beta \cdot \cos(\phi - \beta)}$$

$$\text{connection factor} = \frac{\cos \phi}{\cos \beta \cdot \cos(\phi - \beta)}$$

$$\frac{\cos \phi}{\cos \beta \cdot \cos(\phi - \beta)} = \frac{\cos \phi}{\cos \beta [\cos \phi \cos \beta + \sin \phi \sin \beta]}$$

$$\Rightarrow \frac{\cos \phi}{\cos^2 \beta \cos \phi [1 + \tan \phi \tan \beta]} \Rightarrow \frac{\sec^2 \beta}{(1 + \tan \phi \tan \beta)}$$

$$\sec^2 \beta = 1 + \tan^2 \beta$$

$$\text{for small } \beta, \tan^2 \beta \approx 0, 1 + \tan^2 \beta \approx 1$$

$$\frac{P_T}{P_m} = \frac{\cos \phi}{\cos \beta \cdot \cos(\phi - \beta)} \approx \frac{1}{1 + \tan \phi \tan \beta}$$

$$\% \text{ Error} = \frac{P_m - P_T}{P_T} \times 100 = \tan \phi \tan \beta \times 100$$

$$\begin{aligned} \text{Error:- } P_m - P_T &= P_T \cdot \tan \phi \tan \beta \\ &= VI \cos \phi \cdot \frac{\sin \phi}{\cos \phi} \cdot \tan \beta \end{aligned}$$

$$P_m - P_T = VI \sin \phi \tan \beta$$

① For Lag Load:- $\phi = +ve$

$$P_m = P_T + VI \sin \phi \tan \beta$$

$$P_m > P_T$$


② For Leading Load:- $\phi = -ve$

$$P_m = P_T - VI \sin \phi \tan \beta$$

$$P_m < P_T$$

Error for different load power factors:-
[Wattmeter]



ϕ	$\cos \phi$	$\sin \phi$	$\frac{P_m - P_T}{VI \sin \phi \tan \beta}$	Observation
0°	1	0	0	Min Error
30°	0.866	0.5	$0.5 VI \tan \beta$	
60°	0.5	0.866	$0.866 VI \tan \beta$	
90°	0	1	$VI \tan \beta$	Max Error

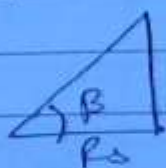

$$\text{Error} = P_m - P_T = VI \sin \phi \tan \beta$$

$$\tan \beta = 0 \Rightarrow \beta = 0 \Rightarrow \text{Error} = 0$$

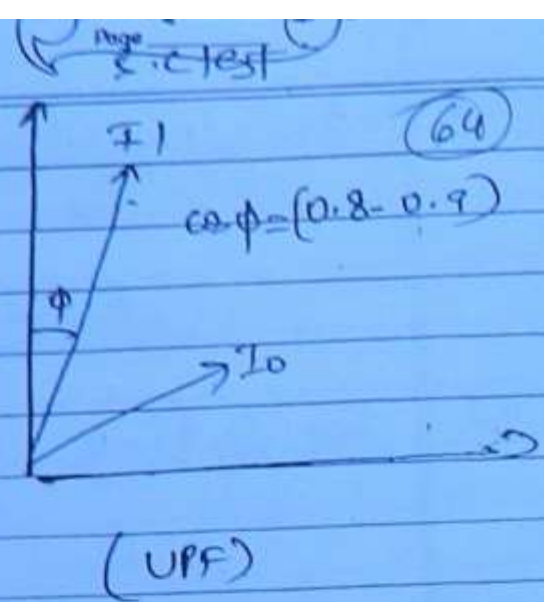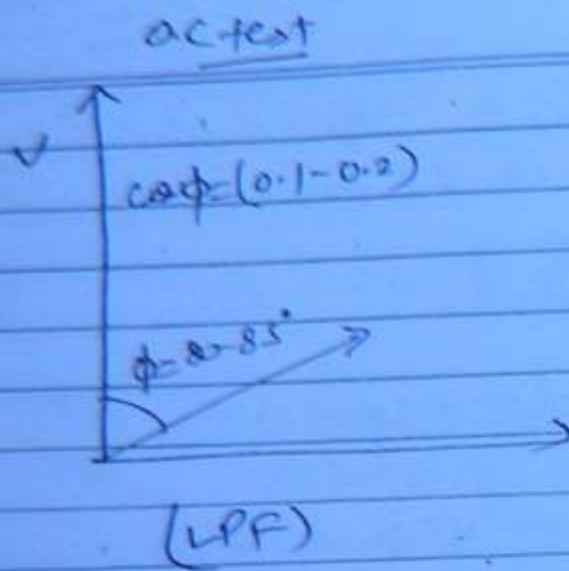The error is becoming zero if $\beta = \text{zero}$ i.e. X_p should be very low compare to R_s hence potential coil should be highly resistive for measuring power more accurately.




LPF wattmeter :-

① $\downarrow T_d = \frac{VI \cos \phi \downarrow}{R_s \downarrow} \frac{dM}{d\theta}$


① Low power factor: - $\cos \phi \downarrow, T_d \downarrow$

$R_s \downarrow, T_d \uparrow$

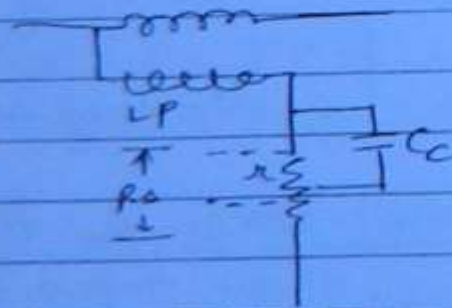② $P_m - P_T = VI \sin \phi \tan \beta \quad \downarrow \tan \beta = \frac{\omega L_P \downarrow}{R_s}$




$C_c = L_P / \omega^2$

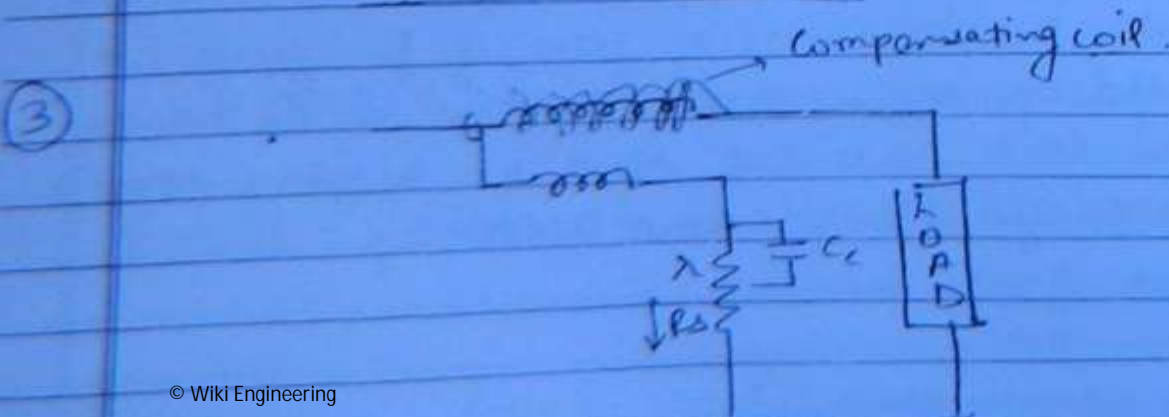

LPF wattmeter's are designed to measure the power more accurately in case of low power factor load condition by compensating the effect of potential coil inductance


(65)

(4) External Mag Fields →

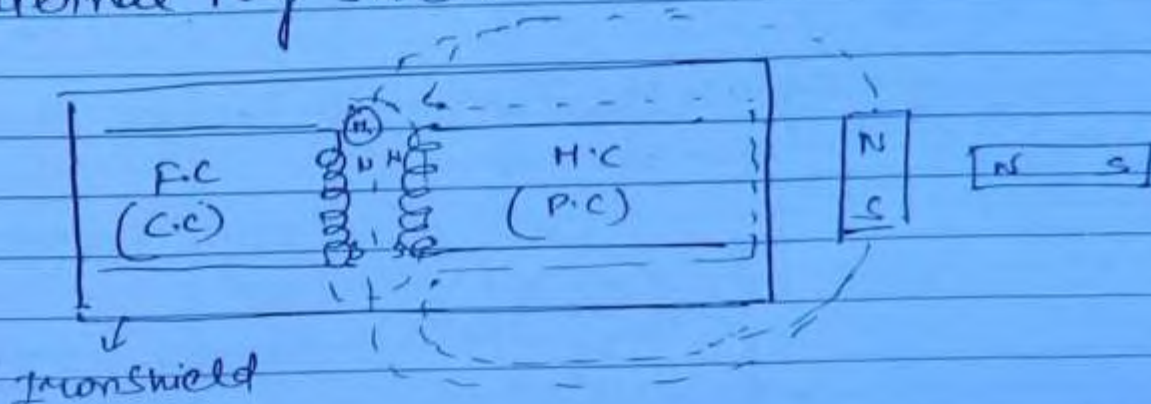

Lab Meters.

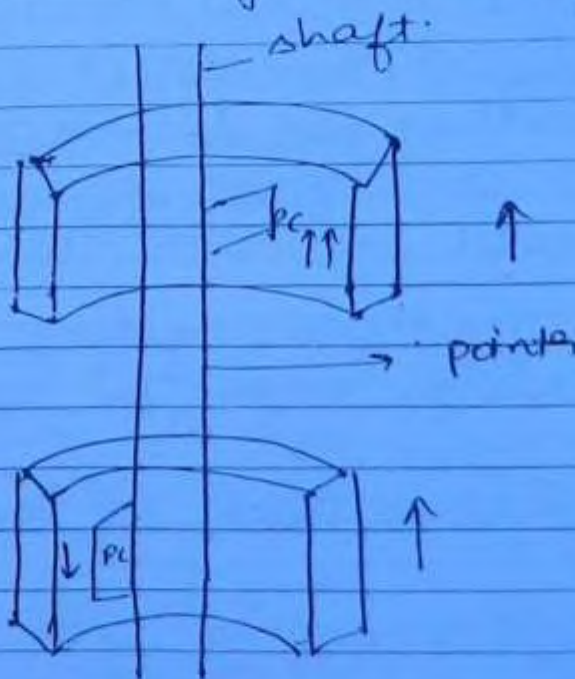Astatic System:- High Precision (or) More Accurate wattmeter.




In Laboratory instrument are iron shielded to reduce the effect of external magnetic field.

In high accurate meters astatic system is used

which the two potential coil's are kept in

the opposite side of spindle (Shaft); In the external magnetic field is applied than it is opposed by one potential coil and added by the other potential coil the net effect on the shaft will be zero so that external magnetic field effect is nullified. (66)

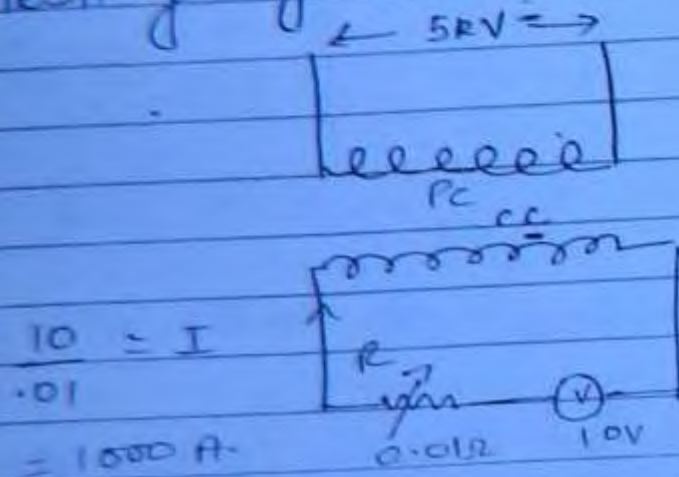→ Testing of wattmeter and Energy Meter →



$$\frac{5 \times 10^6}{2 \times 10^3} = 1000 \text{ A}$$

$$\begin{aligned}
 \text{Energy} &\Rightarrow 5 \times 10^3 \times 10 \times 2 \text{ hr} \\
 &\Rightarrow 10,000 \text{ kWh} \\
 &\Rightarrow 10,000 \times \text{Rs} 5 \\
 &\Rightarrow \text{Rs} 50,000
 \end{aligned}$$

$$\begin{aligned}
 \text{Energy} &= 1000 \times 10 \times 2 \Rightarrow 20,000 \\
 &\Rightarrow 20 \text{ kWh} = 20 \text{ units} \\
 20 \times 5 &= \text{Rs} 100/-
 \end{aligned}$$

Phantom or fictitious loading is used for testing of energy meter and watt


during calibration work of these meter's is minimized.

Potential coil is excited with rated voltage and the current coil is applied with small dc potential with a variable resistor by adjusting the variable resistor rated current is passing through the current coil so that energy consumed by the load can be recorded

by the meter.

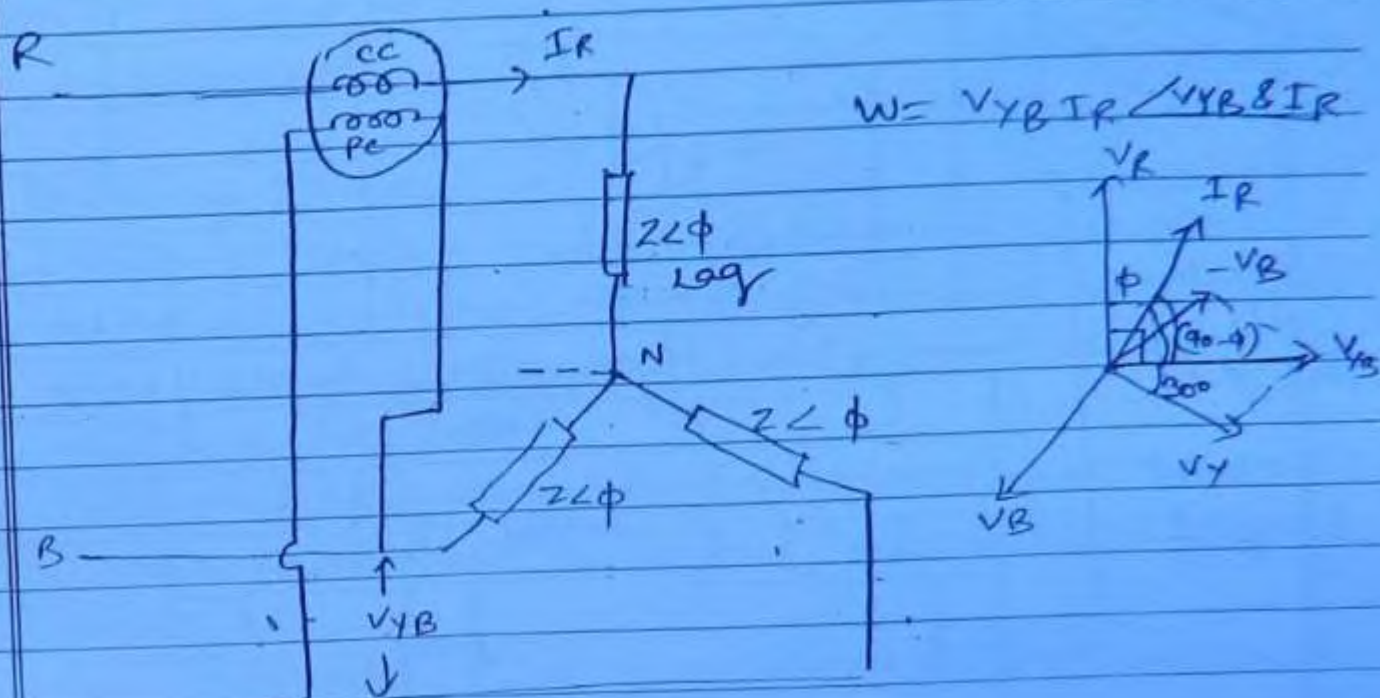(67)

Measurement of Reactive power by Wattmeter



In the Wattmeter current coil is connected to one of the phase (R phase) of a 3ϕ system and the potential coil is connected b/w the remaining two phases (Y and B) then the Wattmeter measures reactive power.

$$W = \sqrt{3} V_{ph} I_{ph} \sin \phi$$

$$W = \sqrt{3} Q_{ph}$$

$$\boxed{Q = 3 \cdot Q_{ph} = \sqrt{3} W}$$

Ch-4

Q1

$$W = V_{ph} I_{ph} \cos \phi$$

$$400 = V_{ph} I_{ph} (0.8)$$

$$V_{ph} I_{ph} = 500$$

$$W = \sqrt{3} V_{ph} I_{ph} \sin \phi$$


$$\Rightarrow \sqrt{3} \times 500 \times 0.6$$

$$\Rightarrow 519.6 \text{ VAR}$$

Energy Meter

P = potential coil
C = current coil

= Permanent Magnet

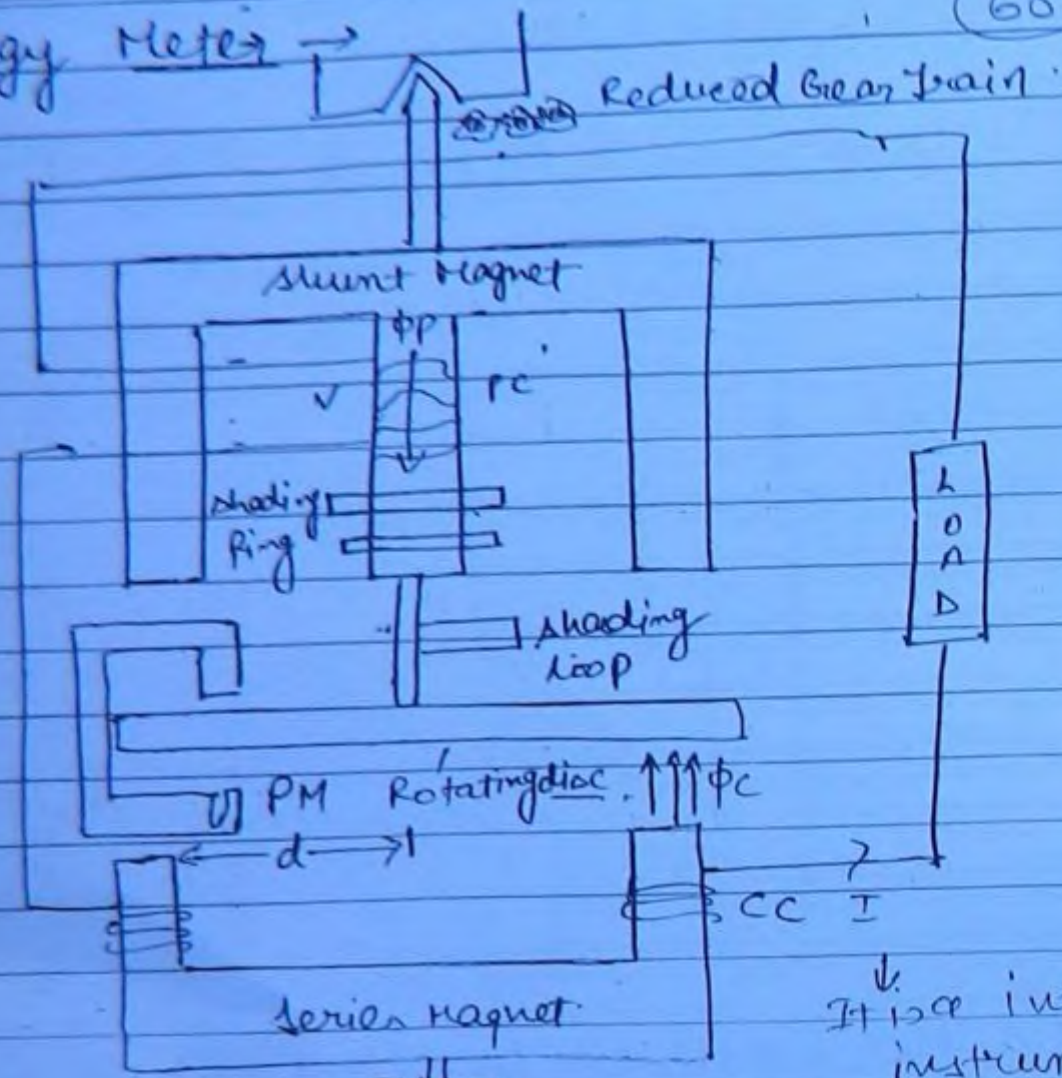

It is an integrating instrument

Energy Meter :- Bearing

$$\begin{aligned} \text{Energy Meter} &= \text{Power} \times \text{Time} \\ &= P \times t \\ &= \sqrt{I} \cos \phi \times t \end{aligned}$$

$$1 \text{ kWh} = 1 \text{ unit}$$

Mechanisms:-


- ① Driving Mechanism - CC, PC
- ② Rotating mechanism - Al Disc
- ③ Braking Mechanism - permanent magnet
- ④ Recording (or) Registering Mechanism. Reduced gear train.

Energy Meter working on a principle of Induction used to measure energy consumed by the load and this energy is cumulatively added over a period of time. Hence it is an integrating instrument.

(69)

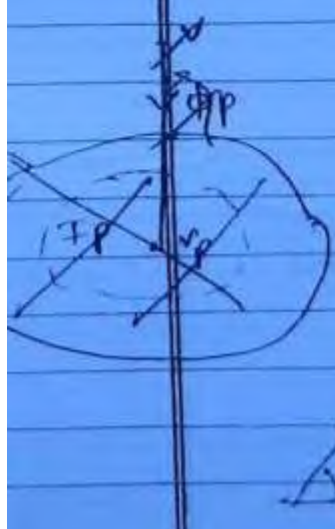(i) Driving Mechanism →

- Driving Torque (T_d):- Energy is proportional to power ($VI \cos \phi$). For measurement of the power the voltage across the load is measured by the potential coil.
- potential coil should be highly inductive so that error is minimum in the measurement of energy.
- The current coil is connected in series to the load which is used to measure current flowing through the load.
- The potential coil produces a flux (ϕ_p) which is flowing through the rotating disc induces an eddy voltage (e/v_p) which is lagging ϕ_p by 90° . This v_p produces an eddy current I_p which lags v_p by angle (α) (impedance angle ϕ of rotating disc).






$$\phi_p = \phi_m \sin \omega t$$

$$v_p = - \frac{d\phi_p}{dt} \Rightarrow -\phi_m \omega \cos \omega t$$

$$v_p = \phi_m \omega \sin (\omega t - 90^\circ)$$

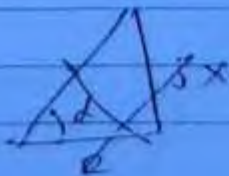
$$v_p \text{ lags } \phi_p \text{ by } 90^\circ$$



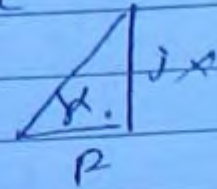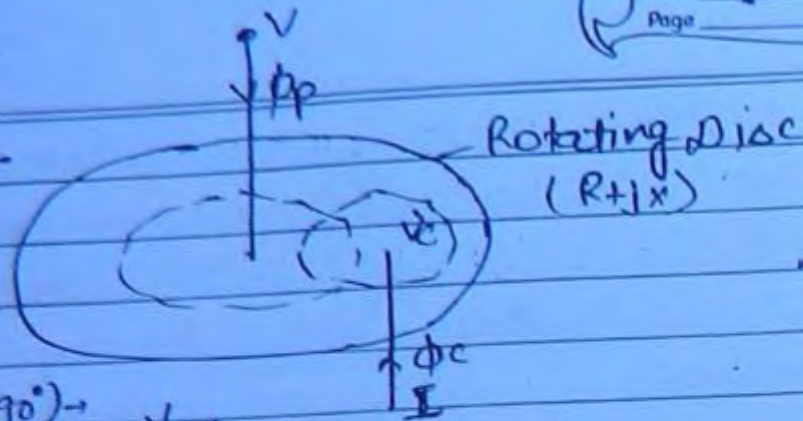


(90°)

V leads Φ_p by $90^\circ \rightarrow$

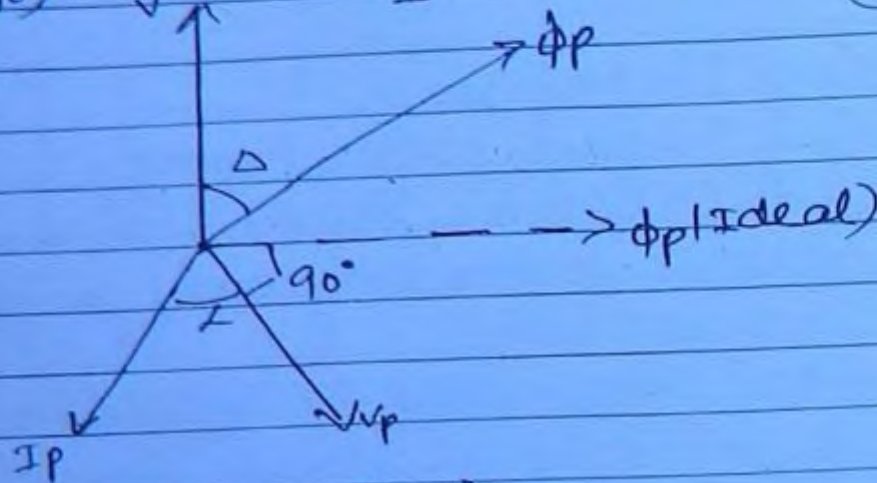


Driving Torque :- (T_d) .

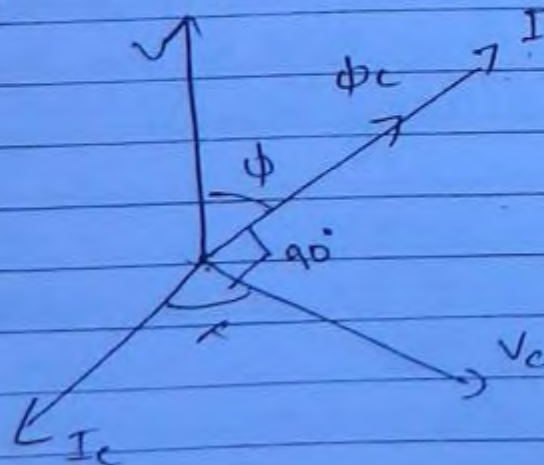The current coil current ^{produces} flux Φ which is passing through the rotating disc induces an eddy voltage (V_c) lagging Φ_c by 90° . Eddy current (I_c) produced due to V_c which lags V_c by angle Δ .



The interaction of ϕ_r and I_c produces a driving torque (7)
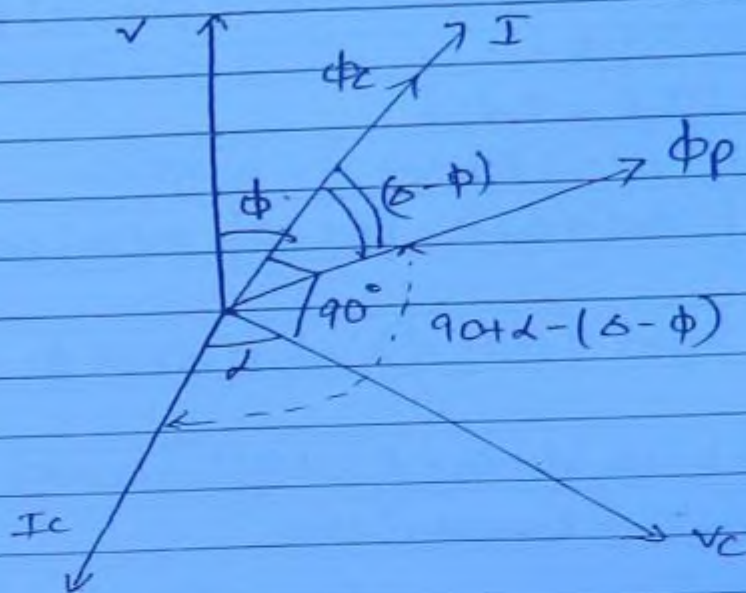
$$T_{d1} \propto \phi_r I_c \cos \angle \phi_r \& I_c$$



$$\phi_r \propto V$$


$$I_c \propto V_c \propto \phi_c \propto I$$

$$\phi_r I_c \propto V I$$

$$T_{d1} \propto V I \cos [(90 + \alpha) - (\delta - \phi)]$$

Interaction of ϕ_c and I_r produces driving torque T_{d2} producing ϕ_c and I_r .
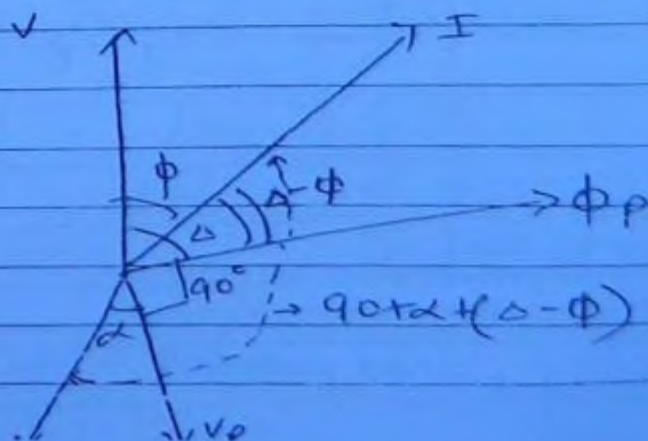
$$T_{d2} \propto \phi_c I_r \cos \angle \phi_c \& I_r$$



$$\phi_c < \pm$$

$$\begin{aligned} \Gamma_p &< \nu_p < \phi_p < V \\ \phi_c \Gamma_p &< V \Gamma \end{aligned}$$

(72)

$$T_{d2} < V I \omega \Delta [90 + \alpha + (\Delta - \phi)]$$

$$T_d < |T_{d1} - T_{d2}|$$

$$< V I \left[\left[\omega \Delta (90 + \alpha - (\Delta - \phi)) \right] - \left[\omega (90 + \alpha + \Delta - \phi) \right] \right]$$

$$< V I \left[2 \sin (90 + \alpha) \Delta \sin (\Delta - \phi) \right]$$

$$< V I \left[2 \cos \alpha \Delta \sin (\Delta - \phi) \right]$$

$$2 \cos \alpha = \text{constant}$$

$$T_d < V I \Delta \sin (\Delta - \phi) = P_m = \text{Measured power}$$

$$\text{True power } P_T = V I \cos \phi$$

$$\text{Error} = P_m - P_T$$

$$\text{Error} = V I [\sin (\Delta - \phi) - \cos \phi]$$

$$\% \text{ Error} = \frac{P_m - P_T}{P_T} \times 100$$

$$\% \text{ Error} = \frac{\sin (\Delta - \phi) - \cos \phi}{\cos \phi} \times 100$$

✓ If $\Delta = 90^\circ$, then the Error is zero so that potential coil should be highly inductive is to be used.

Ch-4

Q2

$$V = 220V$$

$$I = 5A$$

$$\Delta = 85^\circ$$

(23)

$$(1) \cos \phi = \text{UPF} \Rightarrow \phi = 0^\circ$$

$$P_{\text{watt}} = VI [\sin(\Delta - \phi) - \cos \phi]$$

$$\Rightarrow 220 \times 5 [\sin(85 - 0^\circ) - \cos 0^\circ]$$


$$\Rightarrow -4.2W$$

$$(2) \cos \phi = 0.5, \quad \phi = 60^\circ$$


$$P_{\text{watt}} = 220 \times 5 [\sin(85 - 60) - \cos 60^\circ]$$


$$\Rightarrow -85.1W$$

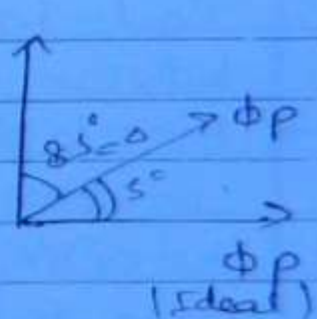→ As the power factor of the load is decreasing than error rises if the potential coil is not inductive.



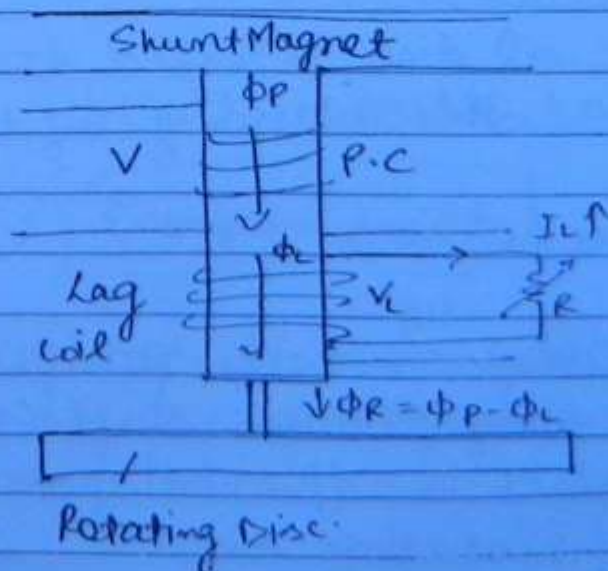Lag Coil / Quadrature / power factor / Shading Ring compensation :-



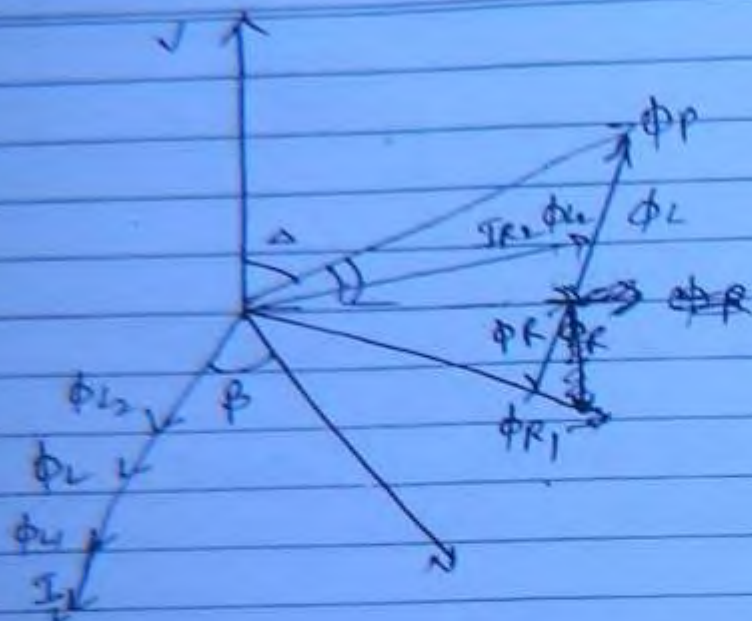

- Lagging coil or shading ring are used to improve the power factor of the potential coil in order to maintain 90° phase disp between ϕ_R & V .
- A variable resistor is used for controlling ϕ_c in case of lag coil.
- The position of the shading ring is adjusted for controlling ϕ_c in case of shading ring. Shading ring is made of copper.


Braking Torque :- (T_b)

Rotating Mechanism

Low weight al disc is used to reduce the friction at the bearing of the shaft or spindle.

Braking Mechanism →

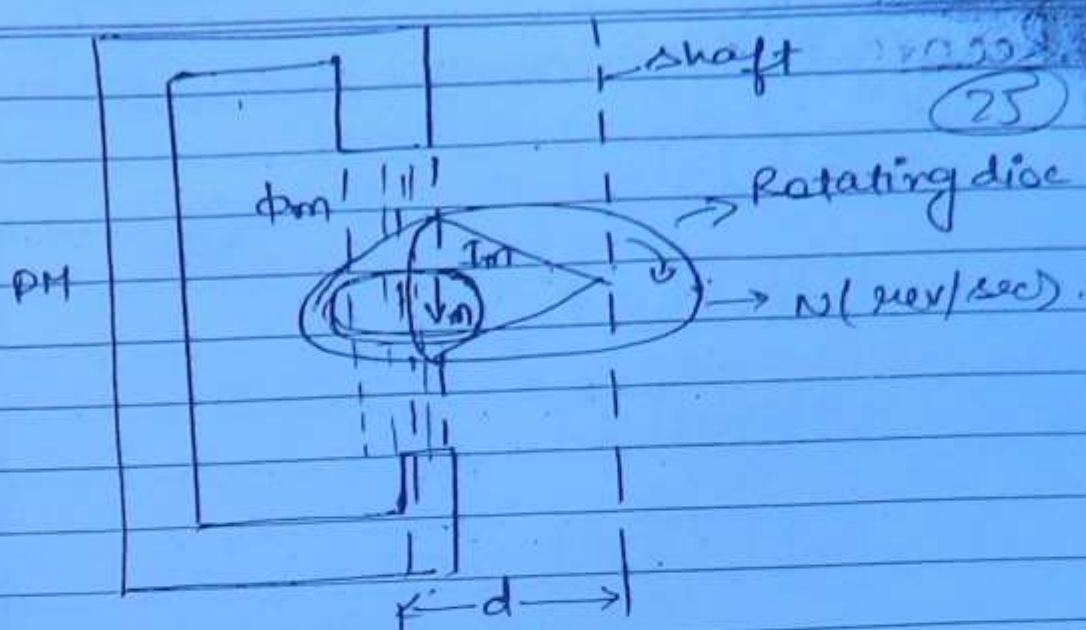- 1) Braking Torque :- ⁽¹⁷⁸⁾ The position of the permanent magnet w.r.t shaft (centre of the rotating disc) is adjusted for controlling the speed of the rotating disc.



$$T_B \propto \Phi_m I_m d$$

$$I_m \rightarrow V_m \Rightarrow \frac{\Phi_m}{\Phi} = N \Phi_m$$

$$T_B \propto \Phi_m N \Phi_m \cdot d$$

$$T_B = K \cdot \Phi_m^2 N \cdot d \quad N = \frac{T_B}{K \Phi_m d}$$

$\Phi_m, d, K = \text{constant's.}$

$$N \propto 1/d$$

$$T_B \propto N$$

At const speed d : -

$$T_d = T_B$$

$$P = N$$

$$\int P \cdot dt = \int N \cdot dt$$

$$\therefore \left\{ \text{Energy} = \int N \cdot dt \right\}$$

By adjusting the distance (d) i.e. posⁿ of permanent magnet w.r.t. to centre of the disc speed of the disc is adjusted.

Recovering & Registering Mechanism:-

0 0 0 0

(2)

0 0 1 0

0 0 9 9

0 1 0 0

Reduced Gear Train mechanism is used to record the energy consumed by the load over a time period so that energy meter is working as an integrating instrument.

Formulae :-

Energy meter Constant $K = \frac{\text{NO of revolutions made by disc}}{\text{Kwhr}}$

$$K = \frac{N}{P \cdot t}$$

$N =$ NO of Revolutions.

$P =$ power in kW.

$t =$ time in hr.

Energy Recorder or Measured in Kwhr

$$W_m = \frac{\text{Total NO of revolutions}}{K}$$

Total Energy Consumed by load in Kwhr

$$W_T = \frac{\sqrt{I} \cos \phi}{1000} \times \frac{t}{3600}$$

$V \rightarrow$ Voltage in V
 $I \rightarrow$ Load Current in A
 Half load $\rightarrow \pm 1/2$
 $\cos \phi \rightarrow$ Load P.f

$t =$ time duration in
 secs of meter

(77)

$$\% \text{ Error} = \frac{\% E_1 = W_m - W_T}{W_T} \times 100$$

$E_1 \rightarrow +ve \rightarrow$ Meter Runs fast.
 $E_1 \rightarrow -ve \rightarrow$ Meter Runs slow.

Pg 42
 Q20

$$W_m = 90/1800 = 0.05 \text{ kWh}$$

$$W_T = \frac{VI \cos \phi}{1000} \times \frac{t}{3600}$$

min (convert to sec multiply by 60)

$$\Rightarrow \frac{230 \times 10 \times \frac{1}{2} \times 1}{1000} \times \frac{3 \times 60}{3600}$$

$$\Rightarrow 0.0575 \text{ kWh}$$

$$\% E_1 = \frac{0.05 - 0.0575}{0.0575} \times 100$$

$$\Rightarrow -13.04\% \Rightarrow 13.04\% \text{ slow}$$

Q4

$$K_1 = 14.4 \text{ A sec/rev.}$$

$$K = \frac{1}{14.4} \frac{\text{rev}}{\text{A sec}}, \quad V = 250 \text{ V}$$

$$\Rightarrow \frac{1}{14.4 \times 250} \times \frac{1}{3600} \text{ rev/kWh}$$

$$\Rightarrow 1000 \text{ rev/kWh.}$$

Error & Compensations in Energy Meter -

(78)

① Friction and Low Load compensation →

Shading loop is used to compensate friction and low load condition. whenever the potential coil is excited flux is passing through the shading loop in some part of the loop this area is called shaded area and the remaining part is non magnetized called unshaded area due to this magnetic field difference, the disc start rotating used for compensating friction and low load condition.



The position of the shading loop can be adjusted.

② Creeping →

If the friction is over compensated by keeping the shading loop nearer to the potential coil. the disc start rotates with only potential coil is excited and there is no load current.

It is called 'creeping'. It produces a creeping error.

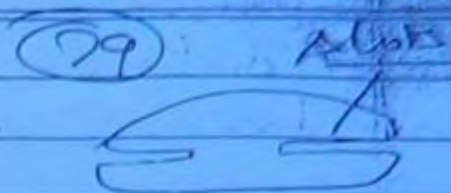
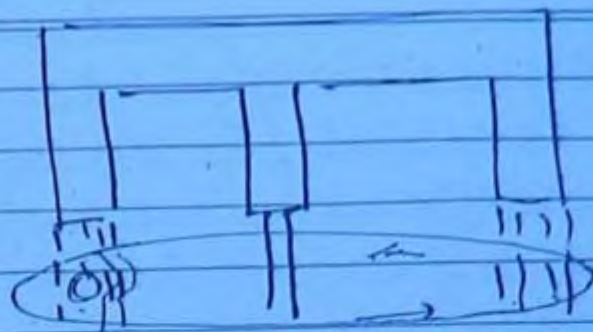
$$\% \text{ Creeping} = \frac{\text{No of revolutions/hr due to creeping}}{\text{No of revolutions/hr due to load}} \times 100$$



For reducing the creeping, two holes on slot's are kept on opposite sides of rotating disc. If these holes are below the side limbs of the shunt magnet then opposing torque are produced so that the disc rotation stops.

Small iron piece is kept on the disc which is attracted by the permanent magnet so that disc rotation stops.

Over voltage compensation →

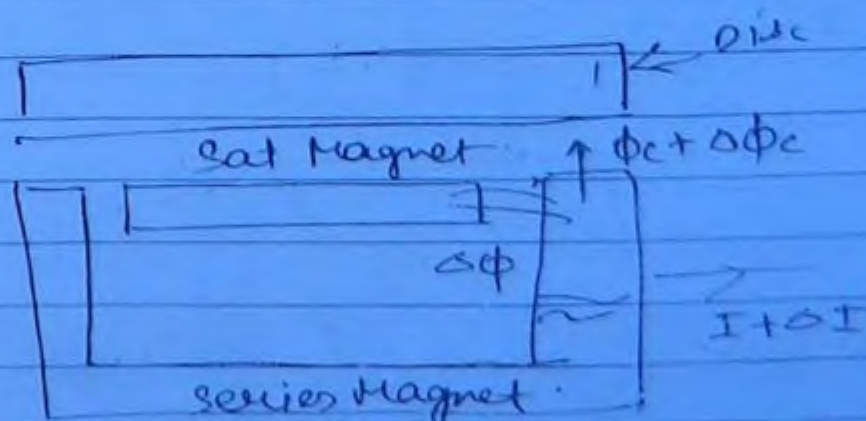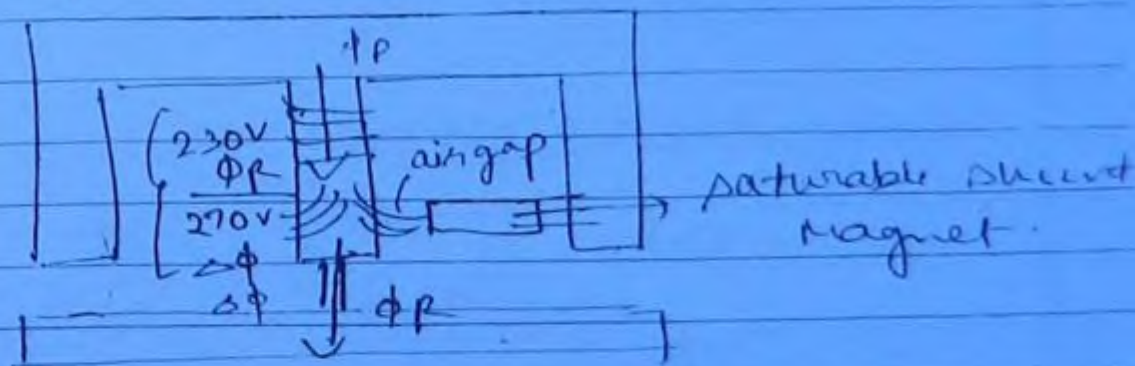

Overload (current)


A saturable shunt magnet is provided between the central limb and side limbs of a shunt magnet which diverts additional flux produced by the additional voltage so that overvoltage is compensated. (83)

Over Current compensation → The saturable magnet is provided between the limbs of a series magnet which diverts the additional flux due to overloading hence compensates the overload.

$$\% \text{creeping error} = \frac{1 \times 60}{\frac{230 \times 5 \times 1}{1000} \times 2400} \times 100$$


$$\Rightarrow \frac{60}{1.15 \times 2400}$$

Power Factor Meter: -

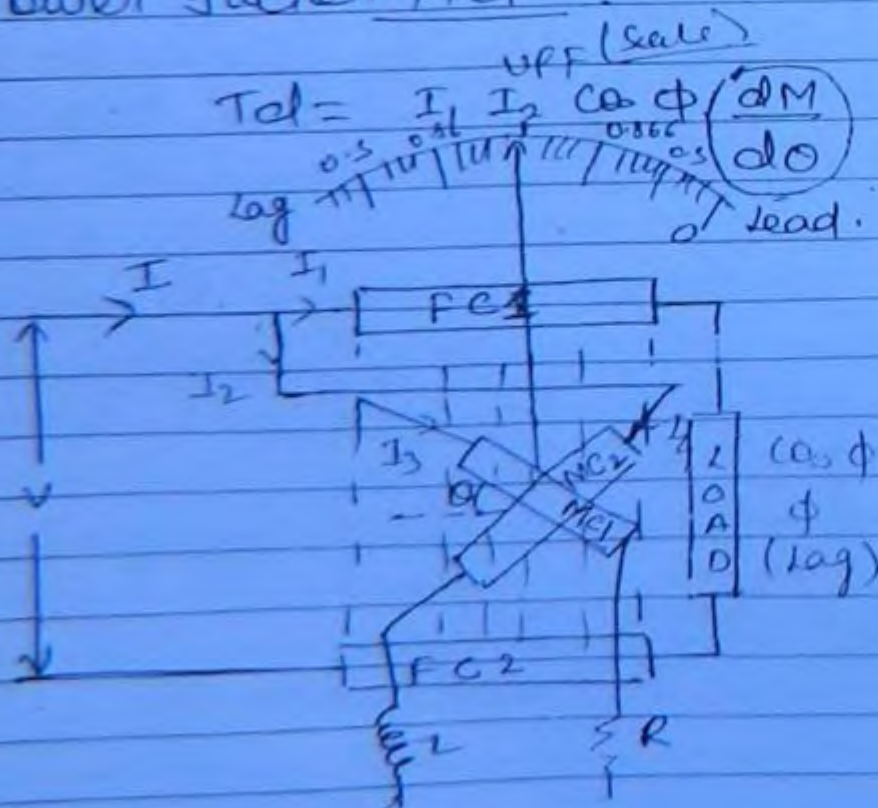

$$T_{el} = \frac{I_1 I_2 \cos \phi}{0.066} \left(\frac{dM}{d\theta} \right)$$

$$\begin{aligned} \theta &\propto I^2 \\ \theta &\propto V \\ \theta &\propto P \\ \theta &\propto \phi \quad (\theta = \phi) \end{aligned}$$

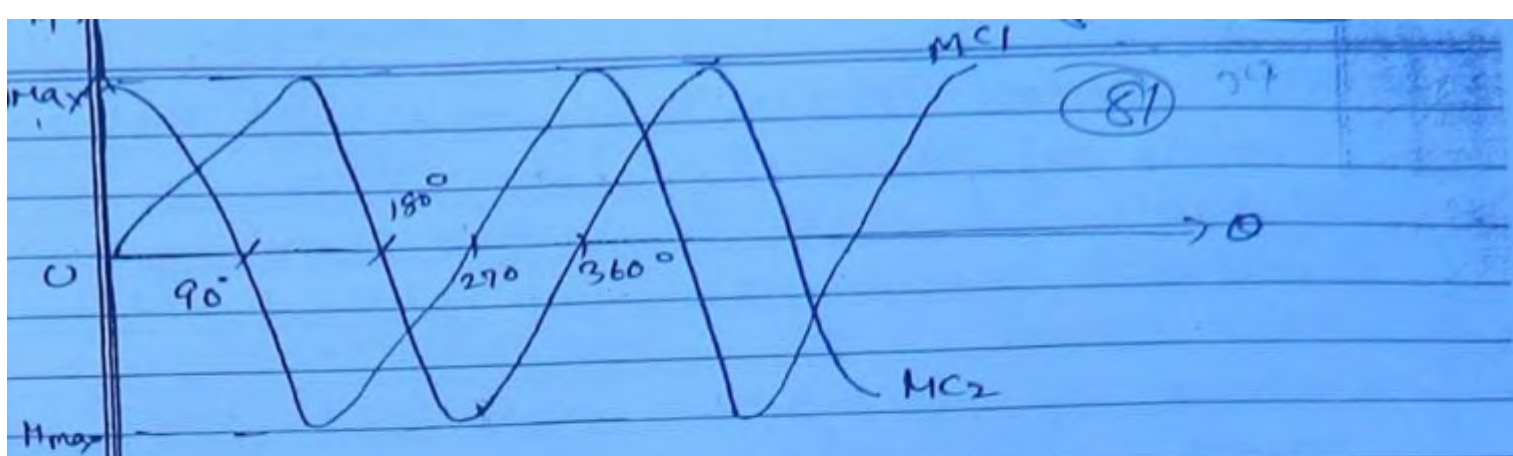

MC1

$$M = M_{\max} \cos \theta$$


$$\left| \frac{dM}{d\theta} \right| = H_{\max} \sin \theta$$

MC2

$$H = H_{\max} \sin \theta$$


$$\frac{dH}{d\theta} = H_{\max} \cos \theta$$

MC1 \rightarrow

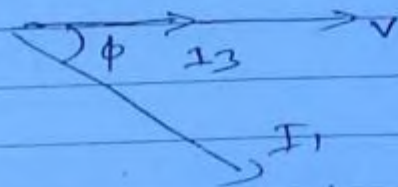

$$T_d = I_1 I_3 \cos \phi \cdot M_{\max} \sin \theta$$

MC2 \rightarrow

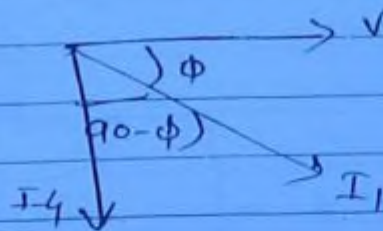

$$T_{d2} = I_1 I_4 \cos(90 - \phi) \cdot M_{\max} \cos \theta$$

$$T_{d2} = I_1 I_4 M_{\max} \sin \phi \cdot \cos \theta$$

At balance,

$$T_d = T_{d2} \quad \text{Assume } |I_3| = |I_4|$$

$$I_1 I_3 M_{\max} \sin \theta \cos \phi = I_1 I_4 M_{\max} \sin \phi \cos \theta$$

$$\tan \theta = \tan \phi$$

$$\theta = \phi$$

Power factor meter is working on the principle of electrodynamometer which consist of two fixed coil and two moving coil's and the moving coil are placed 90° to each other.


In case of 3ϕ system polarised vane power factor meter is used it also works on same principle.

There is no external control torque provided by two spring because the two moving coil's are balanced each other inside the magnetic flux.

Damping torque is provided by the air friction.

Application -


Meggar

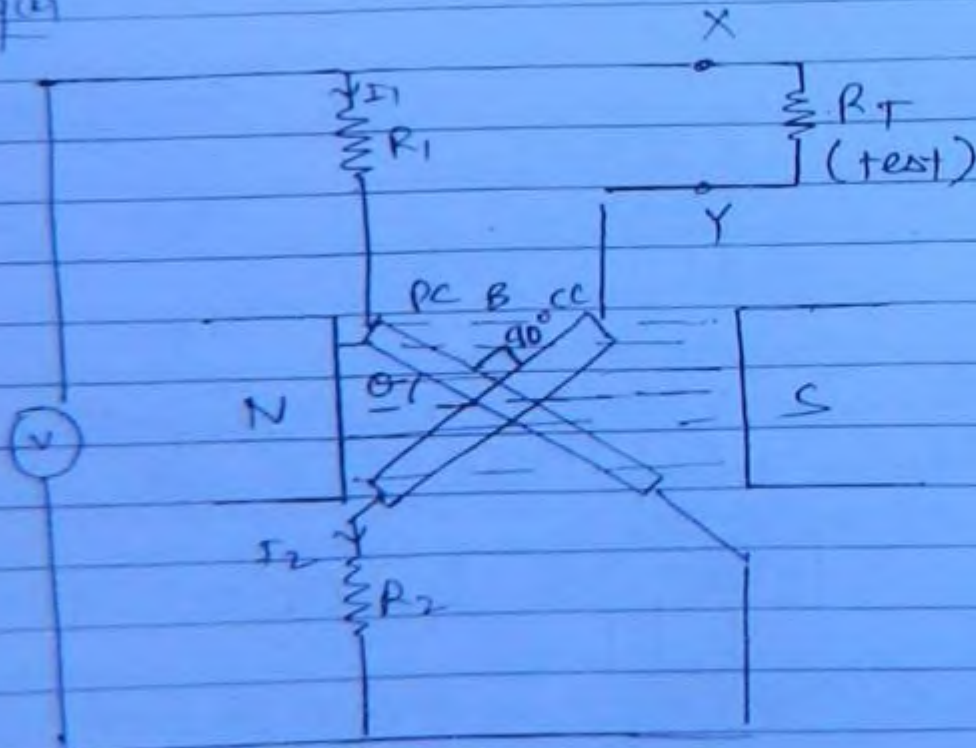


- Megger is a most practical instrument used for measurement of high resistance of insulation of cables and winding insulation of electrical motor, generator and transformers. setting pointer to zero initial position.
- control torque is provided by spring.
- damping torque is provided by air friction.
- Hand driven DC generator is used for providing the supply to the current coil and potential coil.

(84)


Power Frequency Meter →

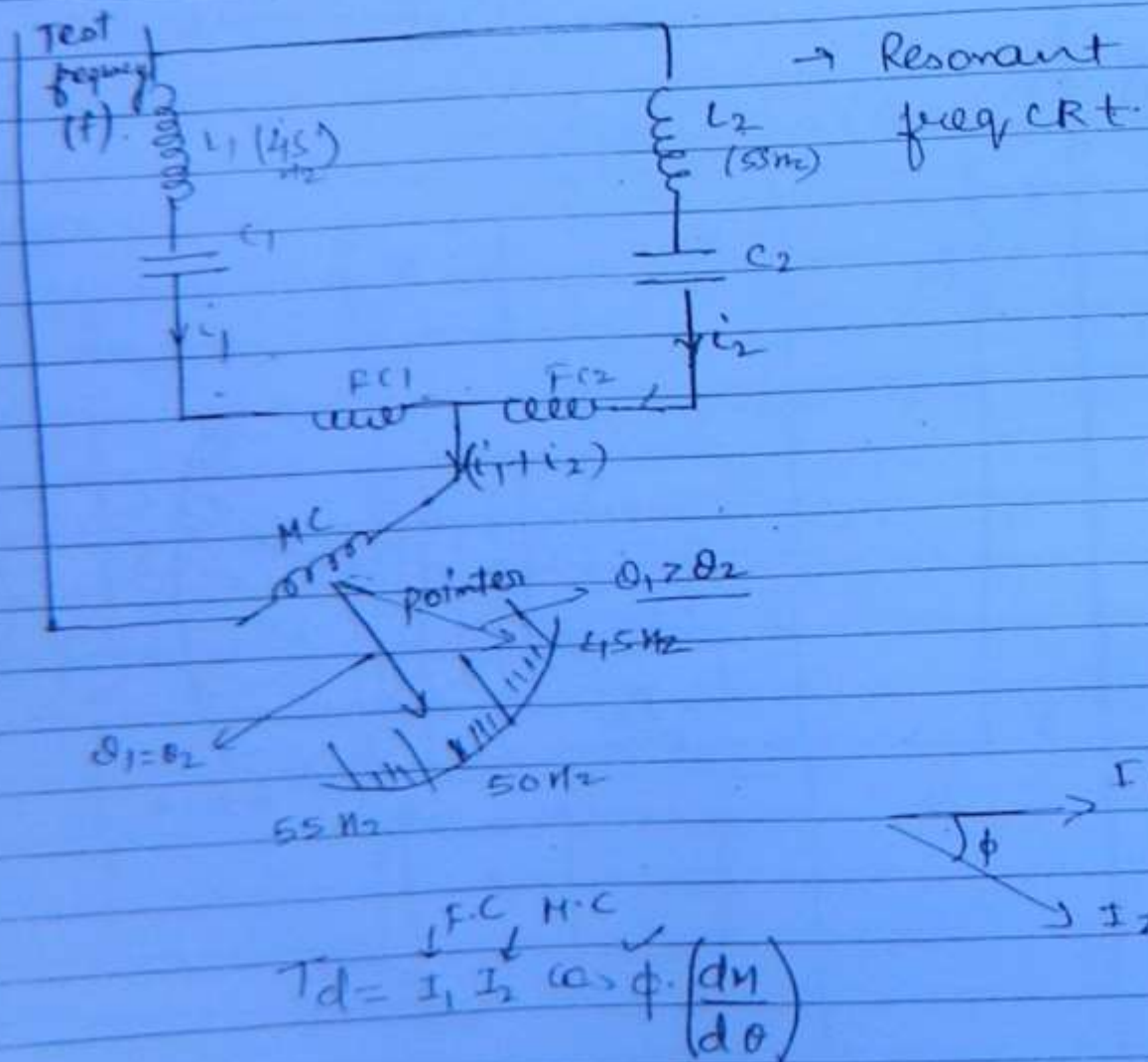

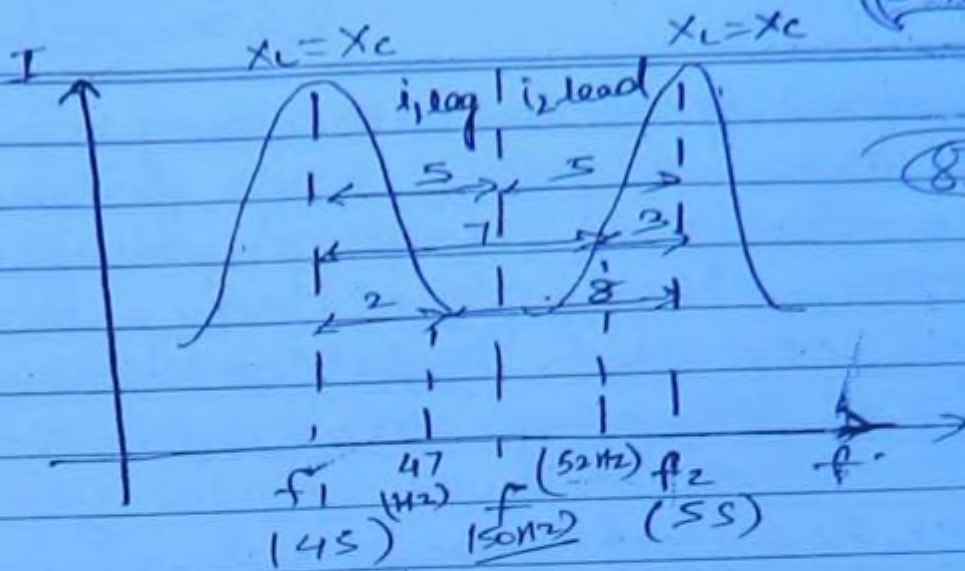

$$f_1 = \frac{1}{2\pi\sqrt{L_1C_1}} = 45 \text{ Hz}$$
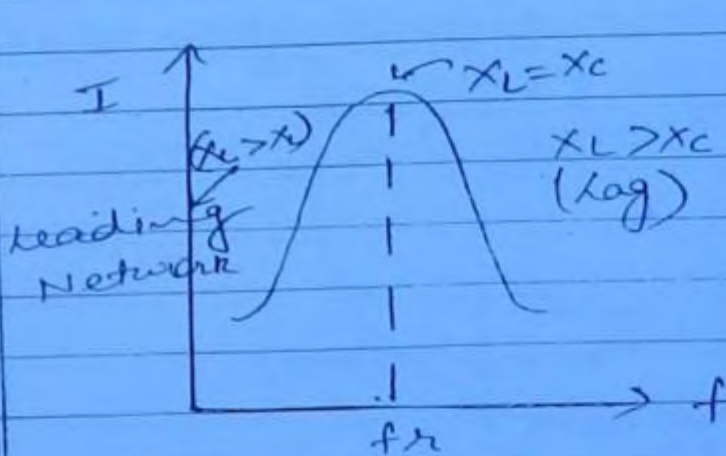
$$f_2 = \frac{1}{2\pi\sqrt{L_2C_2}} = 55 \text{ Hz}$$



$$f < f_r$$

$$\uparrow X_C = \frac{1}{2\pi f C}$$

$$\downarrow X_L = 2\pi f L$$

$$f > f_r, \downarrow X_C = \frac{1}{2\pi f C}, \uparrow X_L = 2\pi f L$$

①

$$f = 50 \text{ Hz}$$

$$f - f_1 = f - f_2$$

$$5 = 5$$

②

$$f = 52 \text{ Hz}, \theta_1 = \theta_2$$

$$(f - f_1) > (f_2 - f)$$

$$\theta_1 > \theta_2$$

③

$$f = 47 \text{ Hz}, (f - f_1) < (f_2 - f_1)$$

$$2 < 8$$


$$\theta_1 < \theta_2$$

Power frequency meter working on a principle of electrodynamometer used to measure the frequency in the power frequency range. Small weight is kept on spindle which provide the controlling torque. Air friction damping is used.

Thermal Meters :- [Heating Effect] (86)

- (i) Hot wire meter
- (ii) Thermocouple meter.

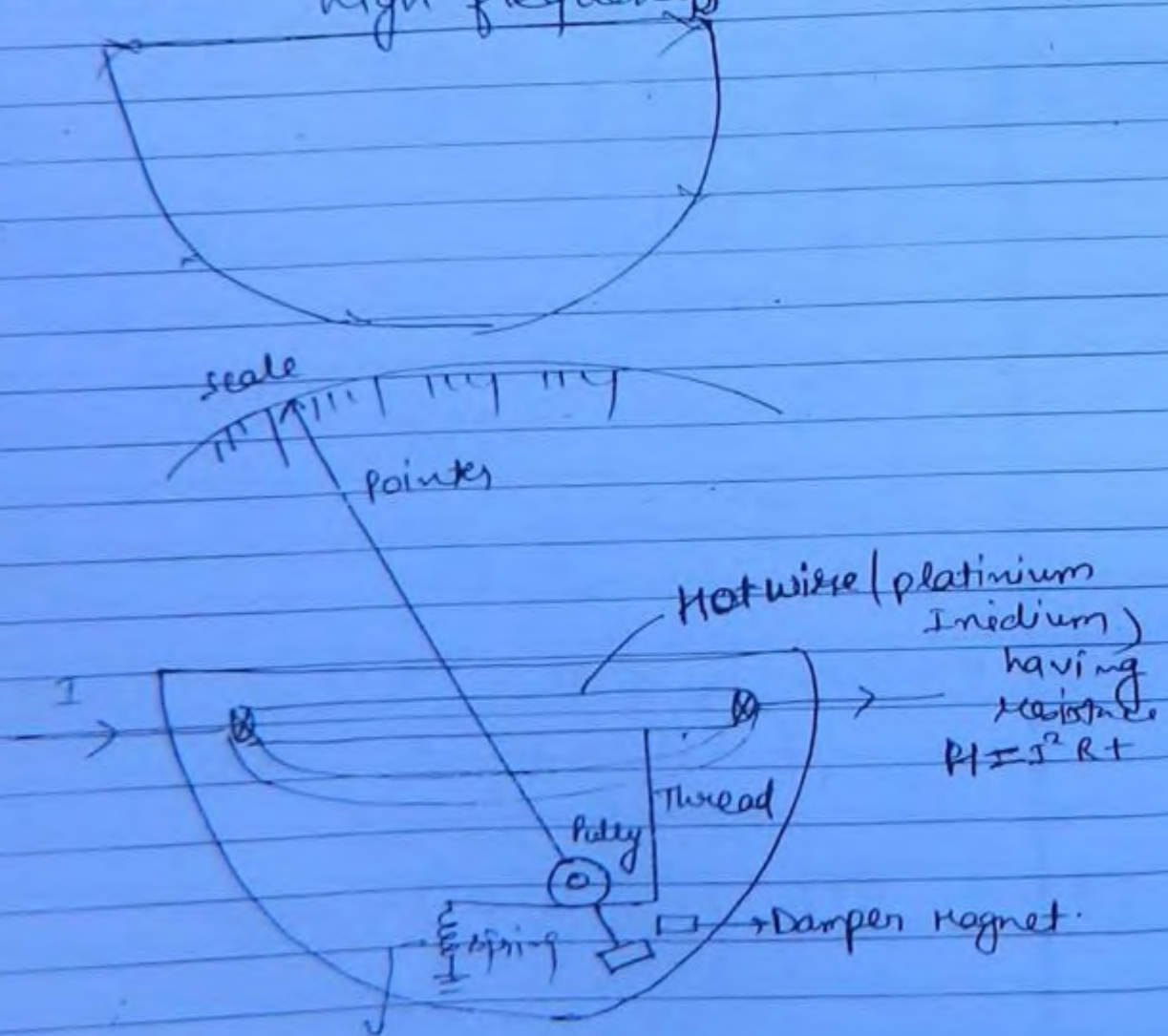(i) Hot wire Meter \rightarrow (Measurement of current at high frequency)



Hot wire Meter working on a principle of heating effect. Whenever, the dc or high frequency current is passing through hot wire due to I^2R losses internal heat is produced so that hot wire expands. The expansion of the hot wire is driving the pulley which in turn moves the pointer which indicate the current reading.



Application →

Used for measurement of high frequency current.

Disadvantage →

Power loss is more, Slow in operation, not suitable for overloading.

(ii) Thermo Couple Meter →

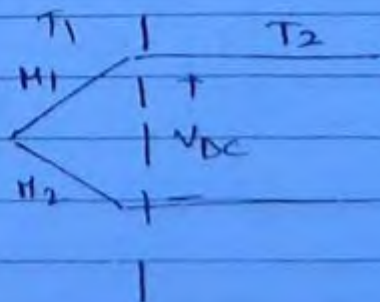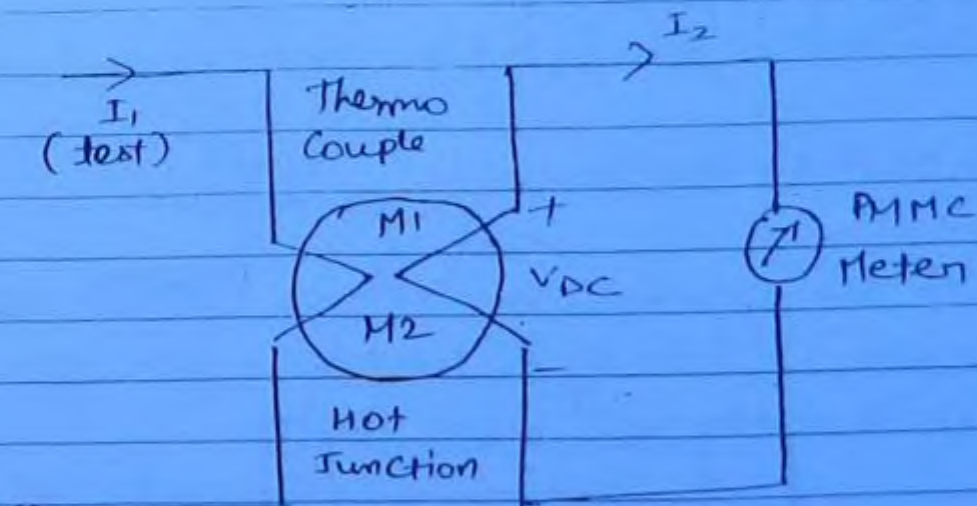

Seebeck effect

The thermocouple meter working on a principle of Seebeck effect.


Seebeck effect \rightarrow If two metal forming a junction and they are operating at two different temp^s the dc potential is produced across the junction. This is measured by using PMMC meter in case of thermocouple meter.


(88)

Application \rightarrow

- Used to measure both dc & ac in case of ac measures RMS Qty of current. The PMMC instrument is calculated to measure RMS Quantity.
- It is used to measure upto 50 MHz of i/p supply frequency.
- It is not suitable for overloading condition.

Electrostatic Meter \rightarrow

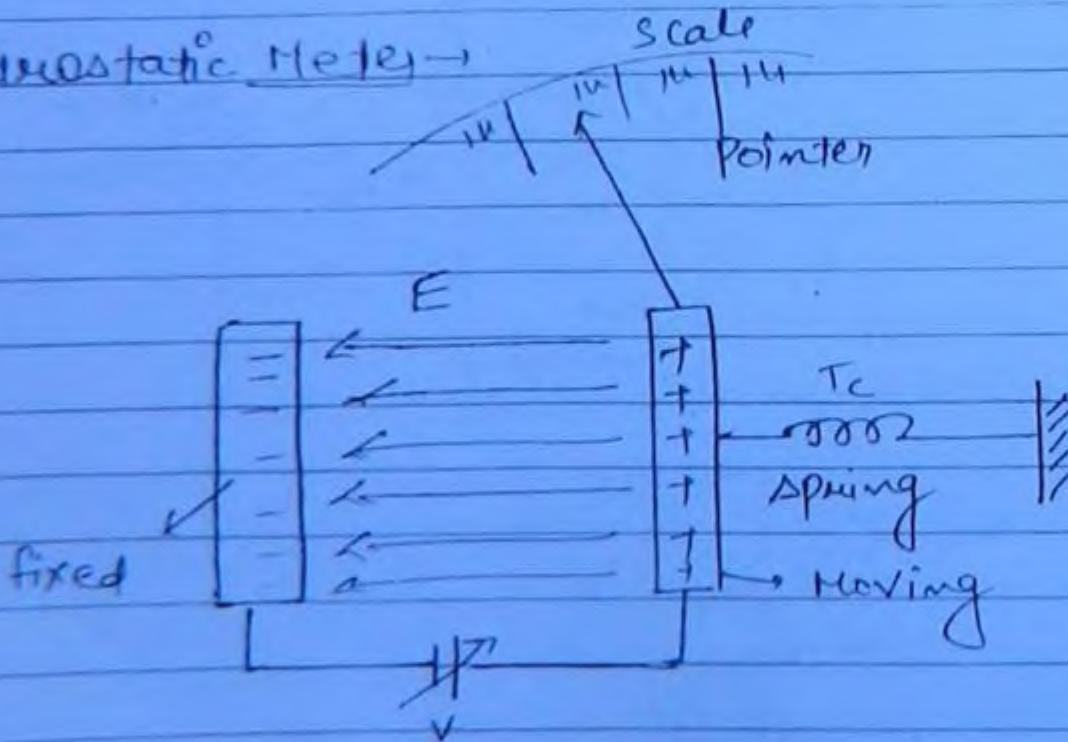

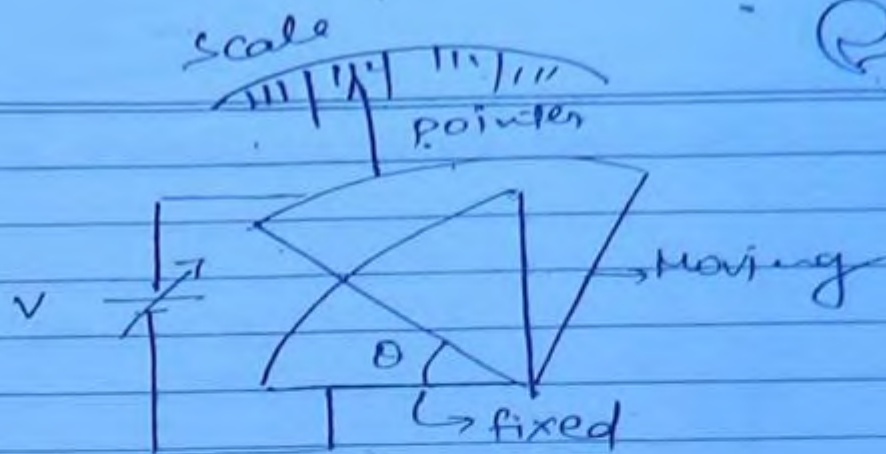

89

MI Meter \rightarrow

$$T_d = \frac{1}{2} I^2 \frac{dL}{d\theta}$$

Electrostatic \rightarrow

$$T_d = \frac{1}{2} V^2 \frac{dC}{d\theta} = K\theta$$

$$[0 < V^2] < \begin{matrix} AC \text{ (RMS)} \\ DC \end{matrix}$$

Electrostatic meter working on the principle of change of electrical field (electrostatic energy) i.e. $\frac{1}{2} CV^2$ b/w the two plates of the capacitor.


- \rightarrow Spring is used for providing controlling torque
- \rightarrow Fluid friction damping is used which provides damping torque.

Application \rightarrow

used for measurement of higher voltages upto 220 kV.

It is provided with series resistor.

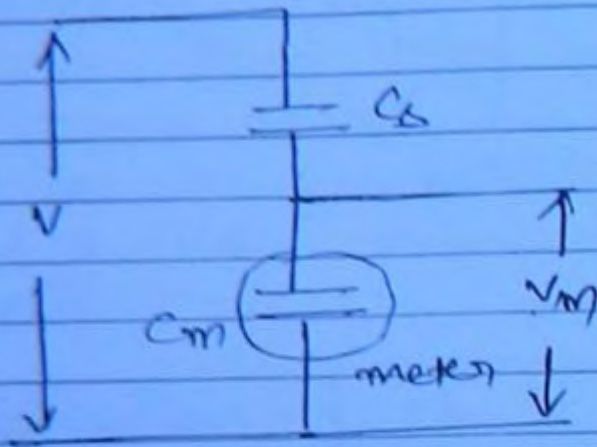Capacitance for the enhancement of electrostatic voltmeter.




$$\frac{V}{V_m} = m \quad (90)$$

$$C_\Delta = \frac{C_m}{(m-1)}$$

C_Δ = Series multiplier Capacitance.

C_m = Meter Capacitance.

Potentiometer → or Null Detector.

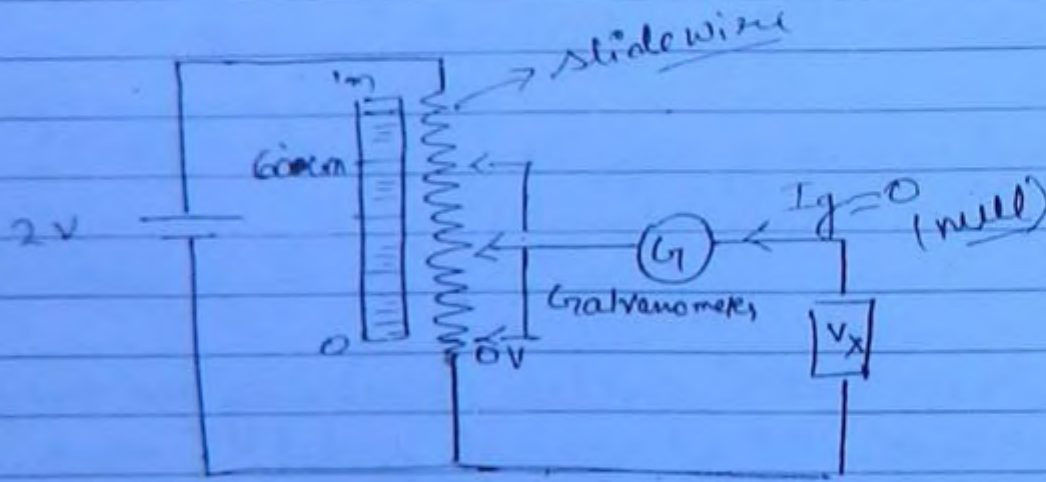

$$1m = 2V$$

$$100 C_m = 2V$$

$$1 C_m = 0.02 V$$


V_x = Test cell

$$V_1 = 60 \times 0.02$$

$$\Rightarrow 1.2 \text{ Volt}$$

$$\boxed{V_x = 1.2 \text{ Volt}}$$

Practical Potentiometer :-

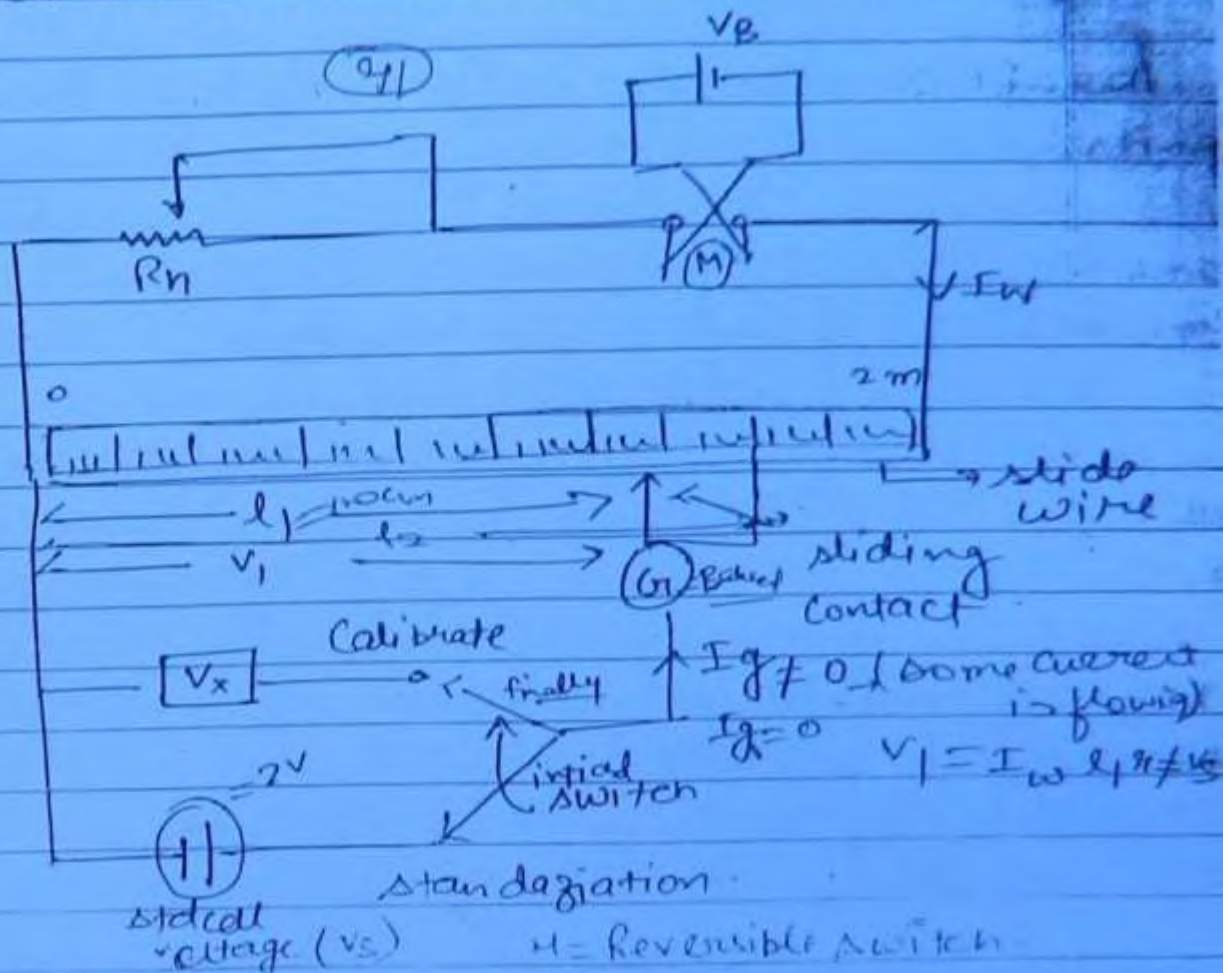


l = Length of slide wire.

R_n = Resistance of slide wire in Ω/m .

l_1 = total resistance of slide wire.

I_w = Working current

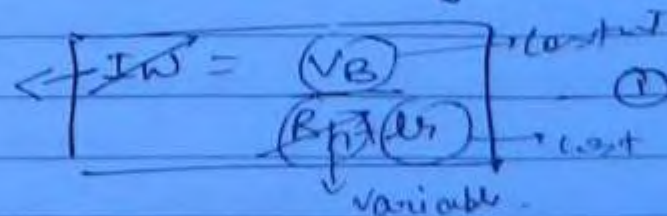$V_s \propto I_w \propto R_n$
 $V_s \propto V_s$ also changes
 $I_g \neq 0$
 Bridge balanced will fail



Switch at standardization

Potentiometer is balanced ($I_g = 0$)

$$V_s = I_w l_1 R_n$$

$$I_w = \frac{V_s}{l_1 R_n} \quad \text{--- (2)}$$

Switch at Calibrate:-

Potentiometer is balanced ($I_g = 0$) at l_2

$$V_x = I_w \cdot l_2 \quad (12)$$

$$\boxed{I_w = \frac{V_x}{l_2 R}} \quad (3)$$

$$(2) = (3)$$

$$\frac{V_s}{l_1 R} = \frac{V_x}{l_2 R}$$

$$\Rightarrow \boxed{V_x = V_s \frac{l_2}{l_1}}$$

Standardization → The process of converting cm scale in terms of voltage is called standardization.


For this process std cell ^{or} known voltage source is used.

Once the instrument is standardized the working (I_w) never be changed.

A reversible switch (M) is used to nullify the effect of thermoelectric emf. Power consumption is very low bcoz the reading is taken at the null position of the galvanometer.

It is more accurate instrument compare to the deflection type of meter's for static measurement. Sensitivity is very high compare to deflecting meter.

- not suitable for measurement of dynamic data (93)
- For these type deflecting meter are used.
- Response is very slow compare to deflecting meters
- In case of ac measurement electrodynamics meter. Ammeter is used as a null detector, it is used for measurement of non electrical quantity like displacement, pressure, force etc along with a voltmeter is connected for indicating the electrical output. The voltmeter should have high resistance to reduce the loading effect otherwise error & accuracy are affected. It is also used as a comparator (summing device) in case of control system application

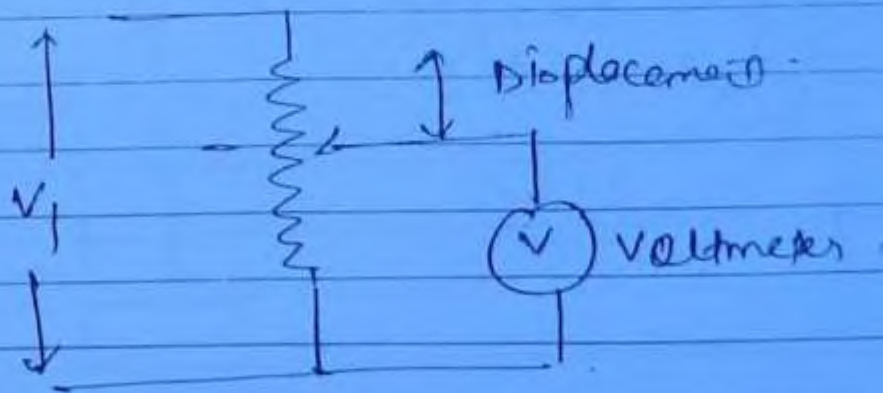

$$V_s = 1.18 \text{ V}$$

$$l_1 = 600 \text{ mm}$$

$$l_2 = 680 \text{ mm}$$

$$V_x = ?$$

94

$$V_x = V_s \frac{l_2}{l_1}$$

$$\Rightarrow 1.18 \times \frac{680}{600}$$

$$\Rightarrow 1.34 \text{ volt}$$

$$\begin{array}{r} 1 \\ 28 \overline{) 39} \\ \underline{28} \\ 110 \end{array}$$

$$\begin{array}{r} 39 \\ 50 \overline{) 19} \\ \underline{10} \\ 14 \end{array} \quad \begin{array}{r} 39 \\ 100 \overline{) 28} \\ \underline{20} \\ 8 \end{array}$$

$$70 \text{ cm} = 1 \Omega$$

$$1 \text{ cm} = \frac{1}{70} \Omega$$

$$50 \text{ cm} = 50/70$$



$$V = I_w \cdot R$$

$$1.45 = I_w \left(\frac{50}{70} \right)$$


$$I_w = 2.03 \text{ A}$$

93

- 93

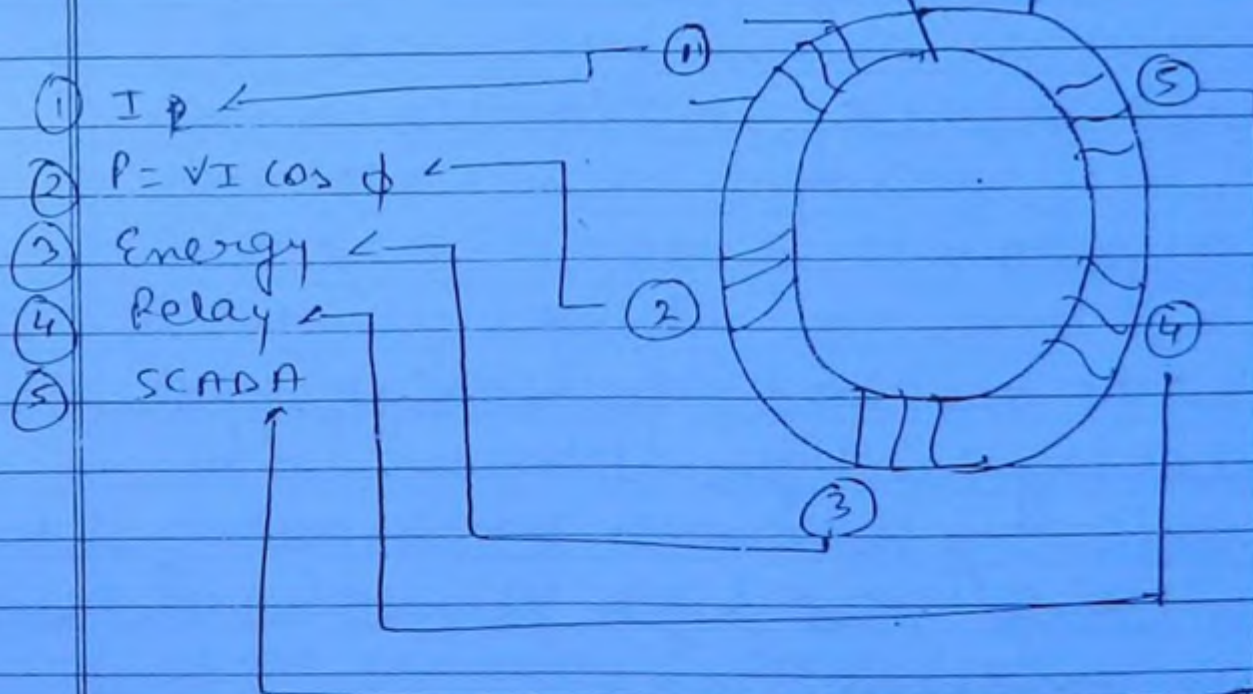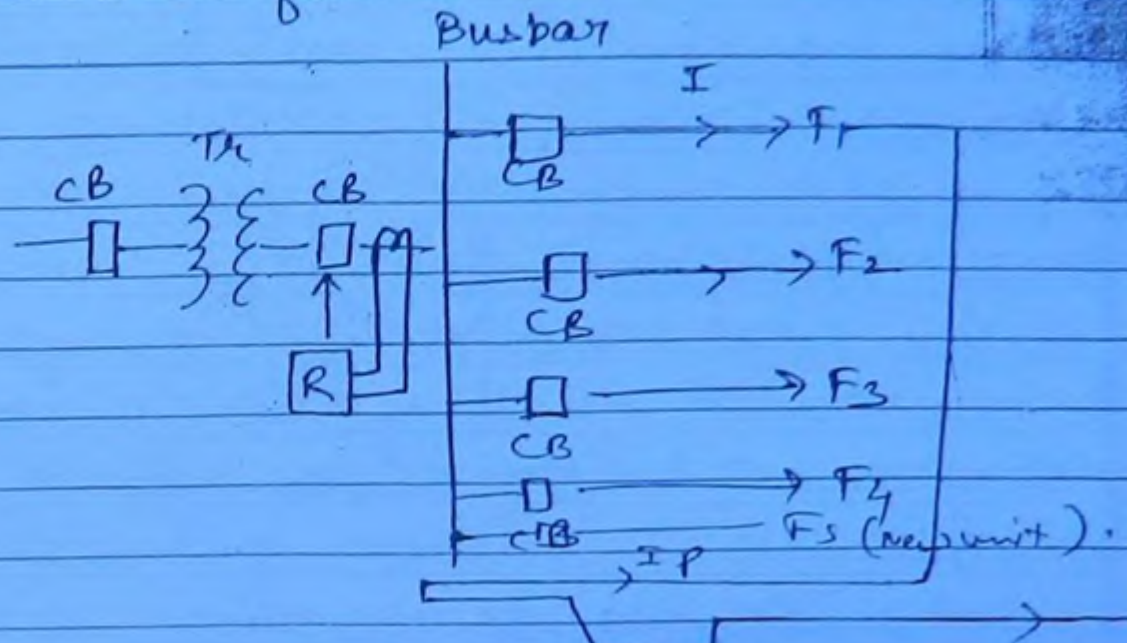

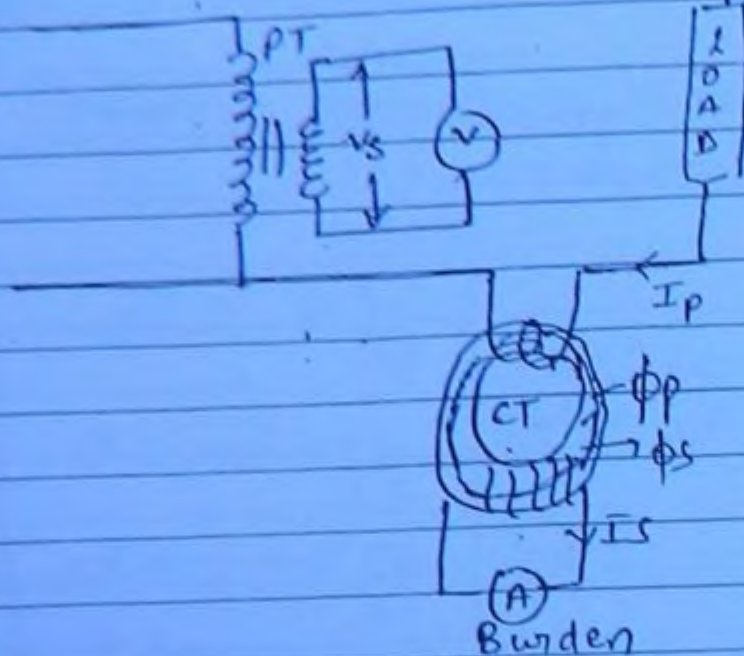Available : $\frac{IP}{IS} = \frac{200/400/600/800}{1A \text{ @ } 5A}$
 Adopted : $400/1A$
 ↓ $600/1A$



(96)

P.T

Rated Secondary $V_s = 110V$.

CT

Rated Secondary $I_s = 1A \text{ or } 5A$.

Advantages →

- (i) CT and PT are used for multiple applications i.e. measuring and protection.
- (ii) The measuring instrument is isolated from the higher voltage and higher current so that need not be insulated.
- (iii) ^{Power} consumption is very low.
- (iv) Higher rating of voltage and current's are reduced to lower voltage and current's.
- (v) Accuracy is higher.
- (vi) Maintenance ^{is} easier.

Current Transformer \rightarrow


(92)

Effect of secondary open \rightarrow

The current X_{mes} is connected in series to the load. Secondary side is connected to the measuring instrument like ammeter, relay etc. If primary is excited the primary flux ϕ_p will set up in the core which induces a voltage in the secondary winding. If the burden is connected on secondary then secondary current I_s flows produces a flux ϕ_s which opposes the ϕ_p .

\rightarrow If the secondary burden is removed i.e. open circuited then ($I_s = 0$) and ($\phi_s = 0$) so that there is no opposing flux to ϕ_p and I_p will not be changed because it is entirely depending on load of the system. The high value of ϕ_p induces high voltage in the secondary which causes insulation damage of the secondary winding and hence secondary of the CT never be open circuited if the primary is excited.

Equivalent ckt of CT \rightarrow

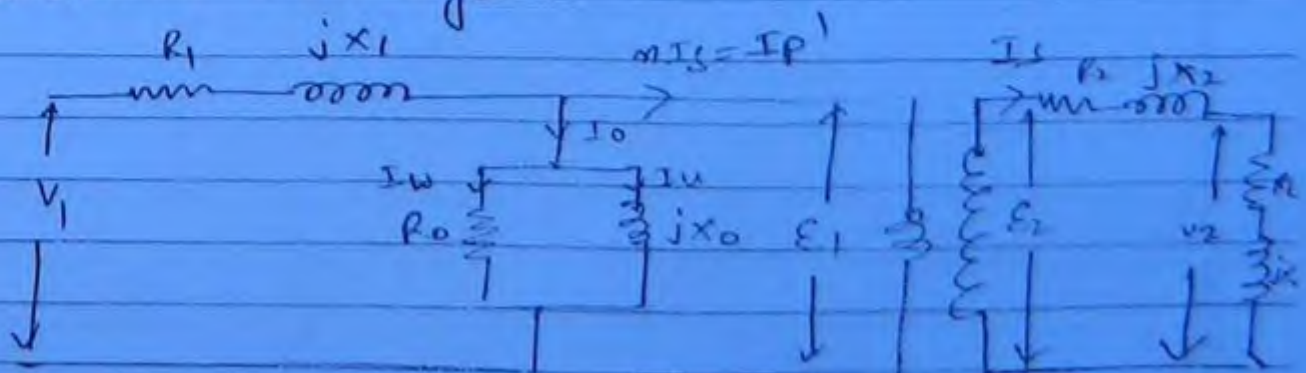

Errors in Instrument x meter's \rightarrow \rightarrow no load component of current I_0 and phase angle error are produced in case of CT's & PT's. (99)

- (i) Ratio Error \rightarrow The transformer turns ratio must be equal to the current ratio in case of ideal condition.

$$n = \frac{N_2}{N_1} = \frac{I_P}{I_S} \text{ [Ideal]}$$

But in practical, CT's $I_P/I_S = n + I_0/I_S$ due to this the turns ratio is not equal to current ratio which produces an error called ratio error.

$$\epsilon = \frac{\text{Nominal Ratio}(K_n) - \text{Actual Ratio}(R)}{\text{Actual Ratio}(R)} \times 100$$

$$\boxed{\% \epsilon \Rightarrow \frac{K_n - R}{R} \times 100}$$

$$K_n \approx n = N_2/N_1$$

$$R = I_P/I_S$$

$$AB = I_0 \cos(90 - (\alpha + \delta))$$

$$AB \Rightarrow I_0 \sin(\alpha + \delta)$$

$$BC = I_0 \sin(90 - (\alpha + \delta))$$

$$\boxed{BC = I_0 \cos(\alpha + \delta)}$$

$$I_P = OC$$

$$OC^2 = OB^2 + BC^2$$

$$OC^2 = (OA + AB)^2 + BC^2$$

$$I_p^2 = [nI_s + I_o \sin(\alpha + \delta)]^2 + I_o^2 \cos^2(\alpha + \delta)$$

$$I_p \approx nI_s + I_o \sin(\alpha + \delta)$$

(100)

$$R = \frac{I_p}{I_s} = \frac{n + \frac{I_o \sin(\alpha + \delta)}{I_s}}{1}$$

$$= n + \frac{I_o \sin \alpha \cos \delta + I_o \cos \alpha \sin \delta}{I_s}$$

$$R \approx n + \frac{I_w \cos \delta + I_u \sin \delta}{I_s}$$

(i) Secondary is pure resistive burden $\phi = 0^\circ$

① I_w is given

$$R = n + \frac{I_w \cos 0^\circ}{I_s} \Rightarrow n + \frac{I_w}{I_s}$$


$$\% \delta = \frac{n - R}{R} \times 100$$

(ii) I_u is given :- Calculate I_p from phasor.

$$R = n + \frac{I_u \sin \alpha}{I_s}$$

$$I_p^2 = I_u^2 + n^2 I_s^2$$

$$I_p = \sqrt{I_u^2 + n^2 I_s^2}$$

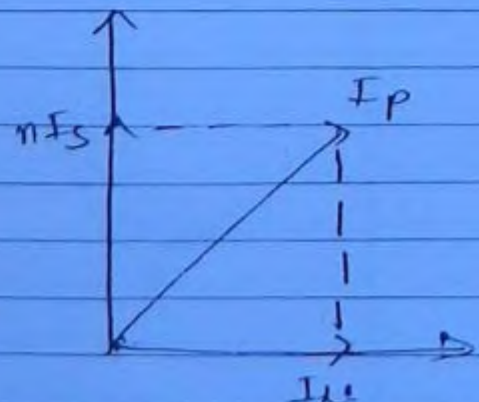

Phasor diagram

$$R = \frac{I_p}{I_s} = \frac{\sqrt{I_H^2 + n^2 I_s^2}}{I_s}$$

(Q1)

$$\boxed{\% \sigma = \frac{n - R}{R} \times 100}$$

Ch-9
Q1

$$N_1 = 1, \quad 500/5 \Rightarrow 100 = n$$

$$I_s = 5 \text{ amp}$$

$$\delta = 0^\circ$$

$$I_u \cdot N_1 = 250 \text{ AT}$$

$$I_u = \frac{250}{1} \Rightarrow 250 \text{ A}$$

$$R = \frac{\sqrt{I_u^2 + n^2 I_s^2}}{I_s}$$

$$\Rightarrow \frac{\sqrt{(250)^2 + (100)^2 (5)^2}}{5} \Rightarrow 111.8$$

$$\Rightarrow \frac{100 - 111.8}{111.8} \times 100$$

$$\sigma \Rightarrow -10.56\%$$

(10)

Phase Angle Error \rightarrow In ideal xmer, the phase angle difference b/w I_p & I_s is 180° but in practical xmer this angle is less by θ due to no load component I_o .

$$\tan \theta = \frac{BC}{OB} = \frac{I_o \cos(\alpha + \delta)}{n I_s + I_o \sin(\alpha + \delta)}$$

$$\text{Assume } n I_s > I_o \sin(\alpha + \delta), \quad \tan \theta \approx \theta$$

$$\theta = \frac{I_0 \cos(2+\delta)}{n I_s}$$

(102)

$$\Rightarrow \frac{I_0 \cos \alpha \cos \delta - I_0 \sin \alpha \sin \delta}{n I_s}$$

$$\theta = \frac{I_u \cos \delta - I_w \sin \delta}{n I_s} \text{ radians}$$

$$\theta = \frac{I_u \cos \delta - I_w \sin \delta}{n I_s} \times \frac{180}{\pi} \text{ degrees.}$$

Pure Resistive Burden. $\delta = 0$.

$$\theta = \frac{I_u}{n I_s} \times \frac{180}{\pi} \text{ degree.}$$

\Rightarrow phase angle difference between I_p & I_s is $180 - \theta$

Q2

$$N_1 = 1 \quad n = \frac{N_2}{N_1} \Rightarrow 500.$$

$$N_2 = 500$$

$$I_s = 5A.$$

$$\delta = 0^\circ$$

$$I_u N_1 = 200$$

$$I_u = \frac{200}{1} \Rightarrow 200.$$


$$\theta = \frac{I_u}{n I_s} \times \frac{180}{\pi} = \frac{200}{500 \times 5} \times \frac{180}{\pi} = 4.6^\circ$$

$$I_p \& I_s \text{ angle} = 180 - 4.6 \Rightarrow \underline{175.4^\circ}$$



Methods of Reducing Error

(i) Reducing the Reluctance → (93)

$$S = \frac{l}{\mu_0 \mu_r A}$$

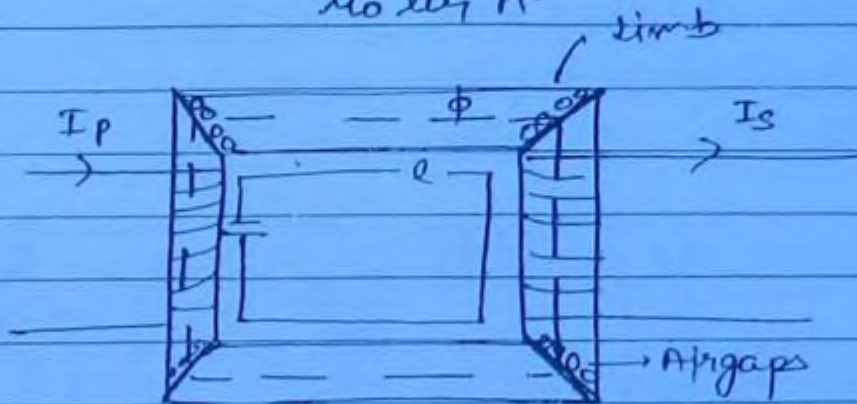

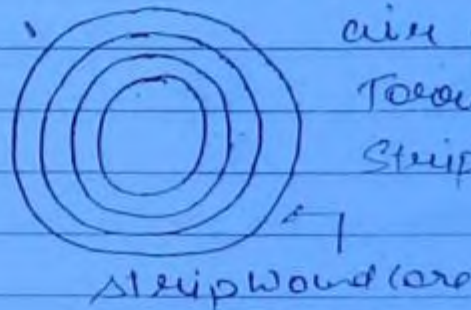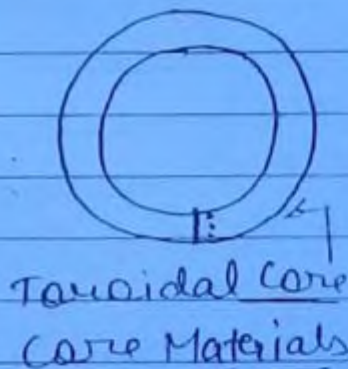we have to reduce these air gaps. Some use Toroidal core and Strip wound core.




Hypernik
permendur
Silicon steel } High μ_r .

→ If the no load component I_0 , is maintain low value than I_w & I_{sc} are maintain low value.

To reduce I_0 , the reluctance of magnetic path is reduced by reducing the no of core joints and hence the distance ^{core is of} between toroidal or strip wound core of circular shape is used.

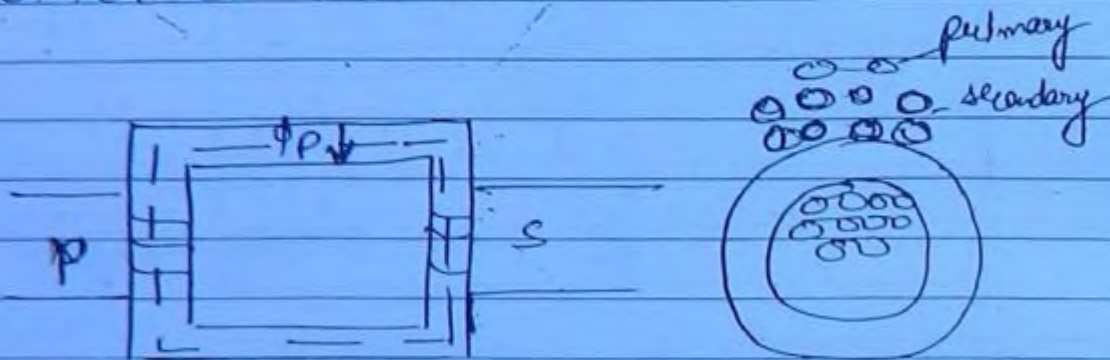(ii) Reducing the distance b/w primary & secondary winding \rightarrow (low)

The air leakage flux is reduced with the distance b/w primary & secondary is maintained as low as possible so that I_0 is maintained low value.



3)
$$K = \frac{N_2}{N_1} = \frac{I_P}{I_S}$$

$$n I_S = I_P = N_2 / N_1$$

(iii) Reducing Primary Turn's \rightarrow

$$n = \frac{N_2}{N_1} = \frac{I_P}{I_S}$$

$$n I_S = \uparrow I_P' = N_2 / N_1 \downarrow \quad (N_1 = 1)$$

$$\downarrow \theta = \frac{I_0 \cos(\alpha + \delta)}{n I_S} = \frac{I_0 \cos(\alpha + \delta)}{I_P' \uparrow}$$

$$R = n + \frac{I_0 \sin(\alpha + \delta)}{I_S} \quad \downarrow$$

$$R = n + \frac{I_0 \sin(\alpha + \delta)}{I_P' \uparrow} \quad \downarrow$$

By maintaining single turn primary winding, I_p is maintained higher so that σ and ϕ are reduced. (105)

(iv) Turns Compensation \rightarrow It is used only for reducing ratio error by reducing the secondary turns compare to the physical no of turns available on the secondary.

$$\sigma = \frac{n - R}{R}$$

$$R = \frac{n + I_0 \sin(\alpha + \delta)}{I_s}$$

$$R = n + K_1$$

$$R = n - K_1 + K_1$$

$$R = n$$

$$\sigma = 0$$

$$n = \frac{500}{5} \Rightarrow 100$$

$$N_1 = 1, N_2 = 100$$

$$R = 111.8 = 112$$

$$R = 112$$


$$= 100 + 12$$

$$= 100 - 12 + 12$$

$$= 88 + 12 = 100$$

$$R = n$$

$$\boxed{\sigma = 0}$$

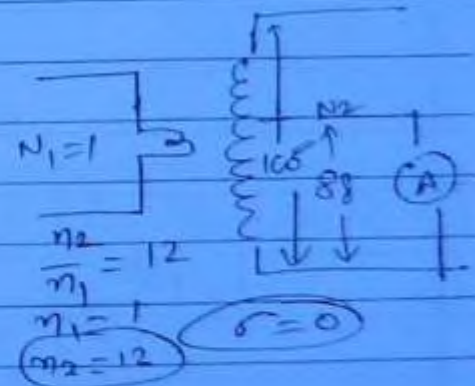

With this method σ is not affected only ϕ is reduced.


- v) WILSON COMPENSATION METHOD → An additional auxiliary short circuit turn is added in series to the secondary winding which causes additional phase lag in the secondary so that the phase angle between the primary and secondary is maintain nearer to 180° and hence the phase angle error is reduced.

(106)

Measurement of RLC :-

AC Bridges :-

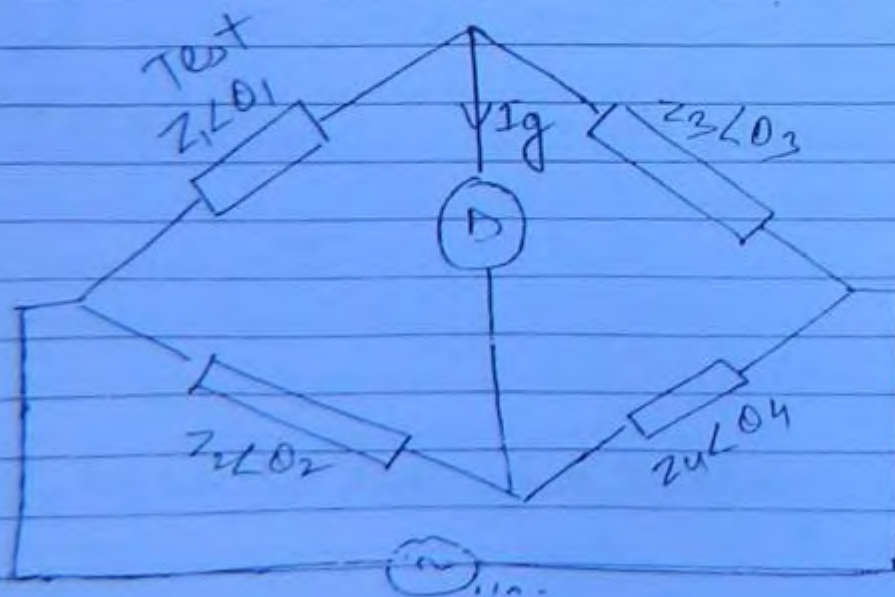- used for Measuring :-
- L, C
 - $R, \mu H$
 - f
 - Dissipation factor (D)
 - Loss Angle ($\tan \delta$)
 - Quality factor (Q)



AC Bridges - Detector (D)

- ① Vibration Galvanometer - 5 Hz - 200 Hz
- ② Telephone Detector - 200 Hz - 2 KHz
- ③ Tuned Amplifier - > 2 KHz.

DC Bridges - Detector

- (i) Galvanometer -

Bridge is Balanced:- (Conditions)

$$(i) |Z_1||Z_4| = |Z_2||Z_3| \quad \text{and} \quad \dots$$

$$(ii) \theta_1 + \theta_4 = \theta_2 + \theta_3$$

Test:-

$$|Z_1| = \frac{|Z_2||Z_3|}{|Z_4|}$$

$$Z_1 = |Z_1| / \theta_1$$

$$\theta_1 = (\theta_2 + \theta_3) - \theta_4$$


$$Z_1 = \left| \frac{Z_2 Z_3}{Z_4} \right| \angle \theta_2 + \theta_3 - \theta_4$$

θ_1	Components of Z_1
0°	R
90°	L
-90°	C
$0 < \theta_1 < 90$	R, L
$-90 < \theta_1 < 0$	R, C

Q

Consider following statement regarding balance AC bridge shown in the given figure for the measurement of the coil Z_1 .

(108)

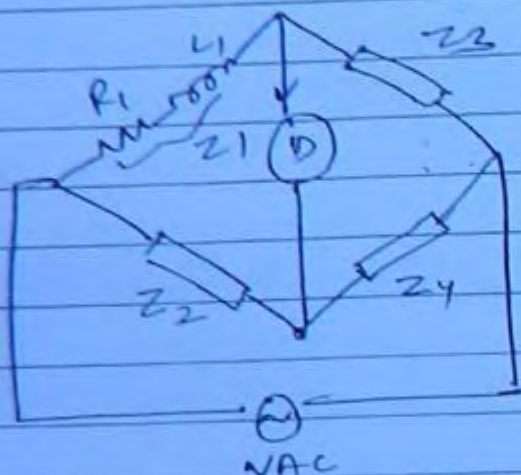

- ① $Z_2 = R_2$ in series with L_2 , $Z_3 = R_3$, $Z_4 = R_4$
- ② $Z_2 = R_2$, $Z_3 = R_3$, $Z_4 = R_4 \parallel L_4$
- ③ $Z_2 = R_2$, $Z_3 = R_3$, $Z_4 = R_4$ in series with L_4
- ④ $Z_2 = R_2 \parallel L_2$, $Z_3 = R_3$, $Z_4 = R_4$

a) 1 and 2 ☒ b) 1 and 4 c) 2 and 3 d) 3 and 4

Ans

$$Z_1 = R_1 + j\omega L_1 \Rightarrow Z_1 = |Z_1| \angle \theta_1 ; \theta_1 = +ve$$

$$\theta_1 = \theta_2 + \theta_3 - \theta_4 \quad Z_1 = \sqrt{R^2 + \omega^2 L_1^2} \angle \tan^{-1} \frac{\omega L_1}{R_1}$$

① $\theta_1 = +ve$ $|Z_1| \angle \theta_1, \theta_1 = +ve$

$\theta_2 = R_2 + j\omega L_2 \Rightarrow +ve, \theta_3 = R_3 \Rightarrow \tan^{-1} \left(\frac{0}{R_3} \right) = 0,$
 $\theta_4 = 0.$

$\theta_1 = \theta_2 + \theta_3 - \theta_4 = +ve + 0 - 0 = +ve.$

② $\theta_2 = 0, \theta_3 = 0, Z_4 = \frac{R_4 \angle j\omega L_4}{R_4 + j\omega L_4} = 90^\circ - \tan^{-1}(\dots) = +ve$

$\theta_1 = 0 + 0 - (+ve) (\theta_4 = +ve) \Rightarrow -ve$

③ $\theta_2 = \theta_3 = 0, \theta_4 = +ve, \theta_1 = -ve$

Measurement of Inductance (L) :-

(109)

- (i) Maxwell L-C bridge - Medium Q coils ($1 < Q < 10$)
- (ii) Hay's bridge - High Q coils ($Q > 10$)
- (iii) Anderson bridge - Low Q coils ($Q < 1$)
- (iv) Owens bridge - Incremental Inductance (all)


Q factor or Quality factor (Q) :-




$$Q = \frac{X_L}{R} = \frac{\omega L}{R}$$


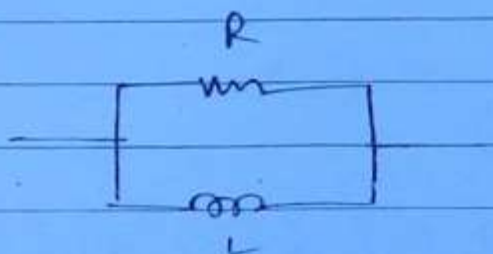
$$Q = \frac{X_C}{R} = \frac{1}{\omega CR}$$



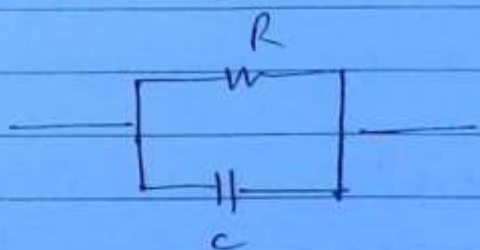
$$Q = \frac{R}{X_L} = \frac{R}{\omega L}$$



$$Q = \frac{R}{X_C} = \omega CR$$

$$Q = \frac{\text{Energy stored by L}}{\text{Energy stored by R}}$$

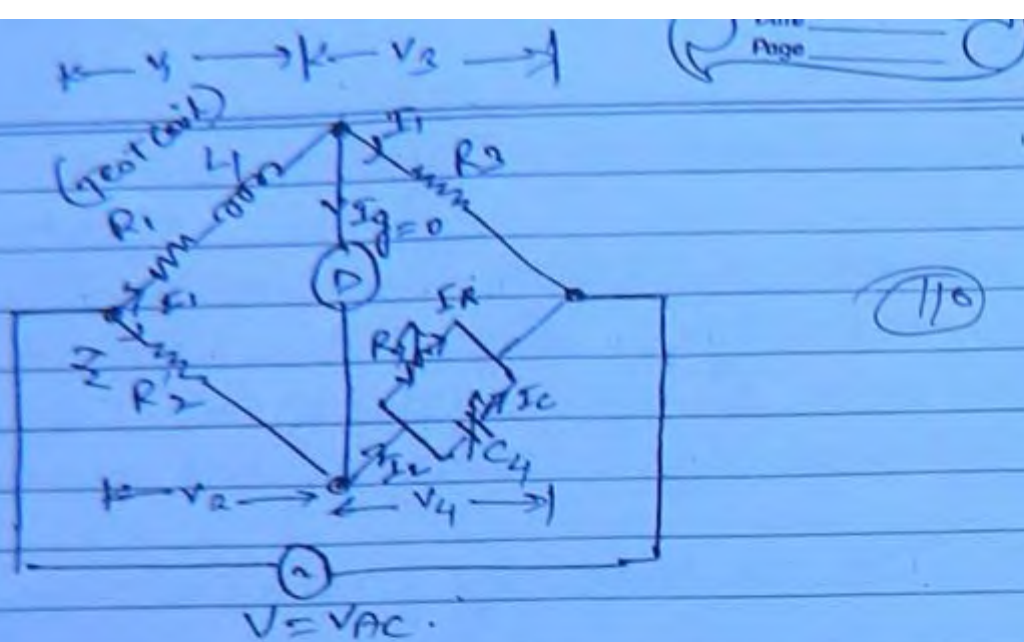- (i) Maxwell L-C Bridge - Medium Q coils ($1 < Q < 10$)



Bridge under balance \rightarrow

$$Z_1 Z_4 = Z_2 Z_3$$

$$(R_1 + j\omega L_1) \frac{R_4}{(1 + j\omega C_4 R_4)} = R_2 R_3$$


$(R_1 + j\omega L_1) R_4 = R_2 R_3 (1 + j\omega C_4 R_4)$
Separate Real & Imaginary terms.

$$\begin{array}{l|l} R_1 R_4 = R_2 R_3 & \omega L_1 R_4 = \omega R_2 R_3 R_4 C_4 \\ \hline \boxed{R_1 = \frac{R_2 R_3}{R_4}} & \boxed{L_1 = R_2 R_3 C_4} \end{array}$$

Sliding Balance:-

The equation of R_1 & L_1 the resistance R_2, R_3 are common if these are selected as variable for bridge balanced more no. of operation's are required these is called sliding balance. To reduce sliding balance independent parameter's R_4 & C_4 are selected as variables.

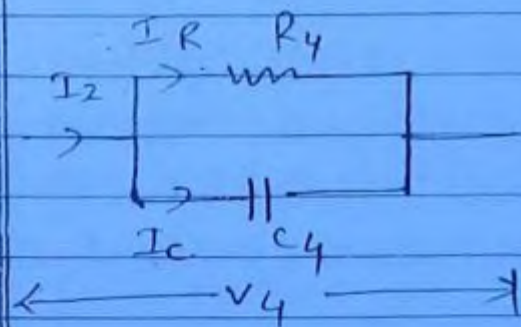If the variables are lying in the same arm of the bridge then the bridge balance is faster. (11)



$V_4 = I_R R_4$, I_R is in phase with V_4
 $= I_C / \omega C_4$, I_C leads V_4 by 90°

$$\nabla I_2 = I_R + I_C$$

$$Q = \frac{WL}{R}$$

$$Q = w \cdot T$$

Limitation of Maxwell Bridge \rightarrow

(1) Not suitable for measurement of high Q coils because the phase angle criteria is not satisfied. Hence Hay's bridge is used.

High Q: $\frac{\omega L_1}{R_1} = \infty$

(112)

R_1 ωL_1
m m m

$$\theta_1 = \tan^{-1}(\omega L_1 / R_1)$$

$$= \tan^{-1}(\infty)$$

$$\theta_1 = 90^\circ$$

$$\theta_1 + \theta_4 = \theta_2 + \theta_3$$

$$\theta_4 = \theta_2 + \theta_3 - \theta_1$$

$$\theta_4 = 0 + 0 - 90^\circ$$

$$= -90^\circ$$

$$-\tan^{-1}(\omega C_4 R_4) = -90^\circ$$


$$\omega C_4 R_4 = \infty$$

↳ NOT practical.

Low Q:- $\frac{\omega L_1}{R_1} = 0$
 $\theta_4 = 0$

In Case of low Q Coil sliding balance occurs so that bridge is not suitable for measurement of low Q coil's. Anderson bridge is used for measurement of low Q coil's.

(2) Hay's Bridge:-

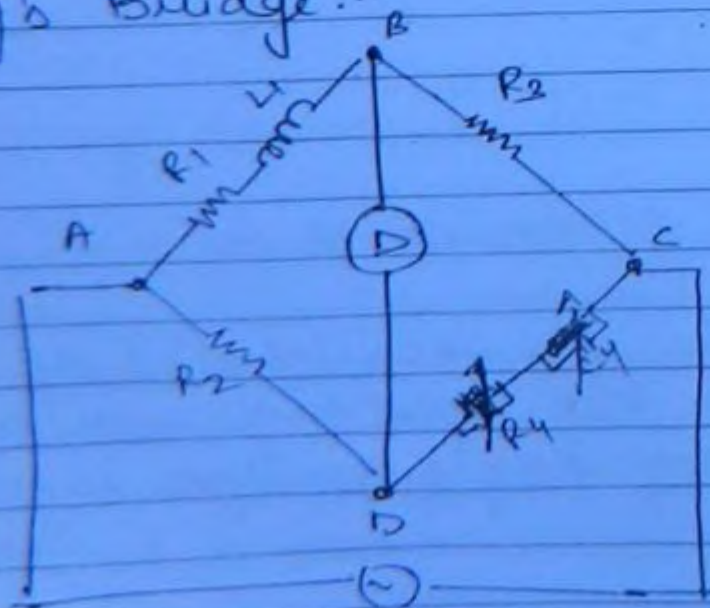

Balance Condition:-

(113)

$$Z_1 Z_4 = Z_2 Z_3$$

$$(R_1 + j\omega L_1) \left(R_4 + \frac{1}{j\omega C_4} \right) = R_2 R_3$$

Separate Real & Imaginary terms:-

$$L_1 = \frac{R_2 R_3 R_4}{(1 + \omega^2 R_4^2 C_4^2)}$$


$$R_1 = \frac{R_4 R_2 R_3 C_4^2 \omega^2}{1 + \omega^2 R_4^2 C_4^2}$$

The equations of R_1 and L_1 all the elements of R_2 , R_3 , R_4 and C_4 are lying so for the bridge balanced initially select R_4 & C_4 as variable's after that select R_2 and R_3 as variable for bridge balanced.

→ Limitation →


Input supply frequency must be known for measurement of R_1 and L_1 .

③ Anderson's Bridge:-

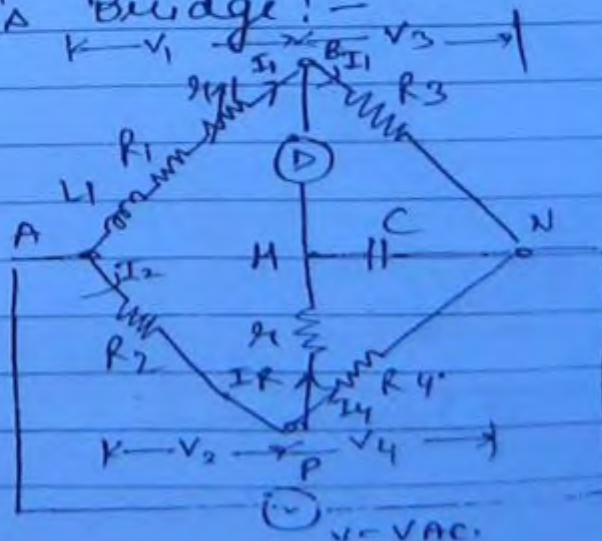

Convert Δ into λ

114

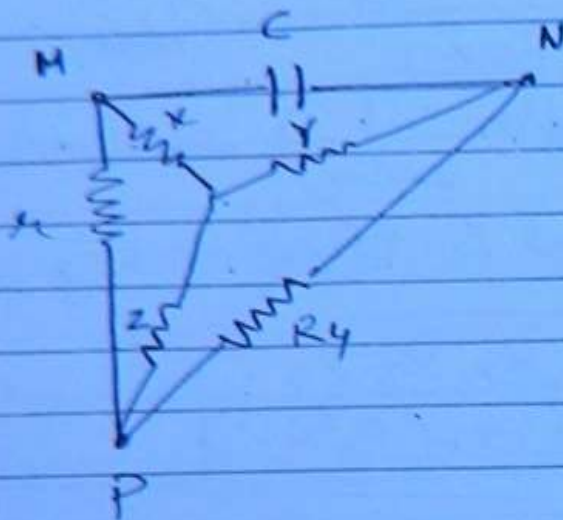


$$Z = \frac{R_1 R_4}{R_1 + R_4 + \frac{1}{j\omega C}}$$

$$Z = \frac{j\omega C R_1 R_4}{j\omega C (R_1 + R_4) + 1} \quad \text{--- (1)}$$

$$V = \frac{R_4 / j\omega C}{R_4 + R_1 + 1/j\omega C}$$
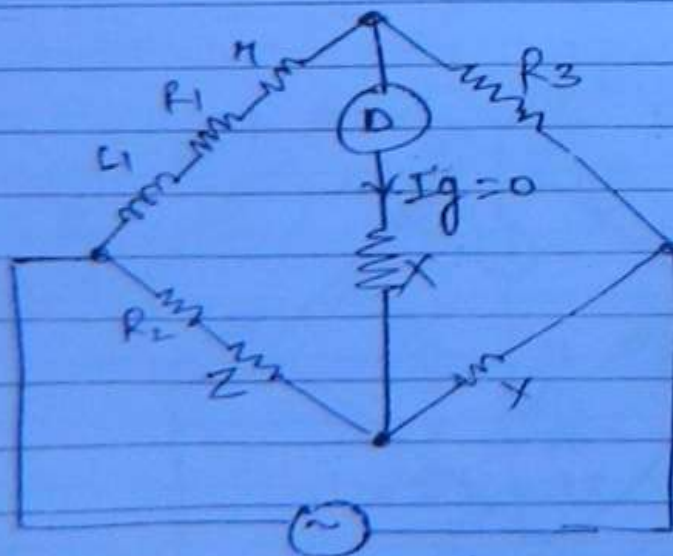
$$V = \frac{R_4}{1 + j\omega C (R_4 + R_1)} \quad \text{--- (2)}$$



Bridge balance ($I_g = 0$) Ignore \times

$$Z_1 Z_4 = Z_2 Z_3$$

$$(R_1 + j\omega L_1) \times = R_3 [R_2 + j\omega L_2] \quad (3)$$

Substitute (1) & (2) in (3) & separate real & Imaginary terms

$$\boxed{R_1 = \frac{R_2 R_3}{R_4} - \omega^2 L_1 L_2} ; \boxed{L_1 = \frac{C R_3}{R_4} (\omega^2 L_2 (R_1 + R_2) + R_2 R_4)}$$

OBSERVATIONS \rightarrow

$$V_{AB} = V_{AM}$$

$$V_1 = V_2 + \omega I R$$

$$V_{BN} = V_{BN} + V_{MN}$$


$$V_3 = 0 + I R / \omega C$$

$I R$ leads V_3 by 90°

$$V_{PN} = V_{PH} + V_{HN}$$


$$V_4 = \omega I R + V_3$$

$$I_2 = I_R + I_4$$

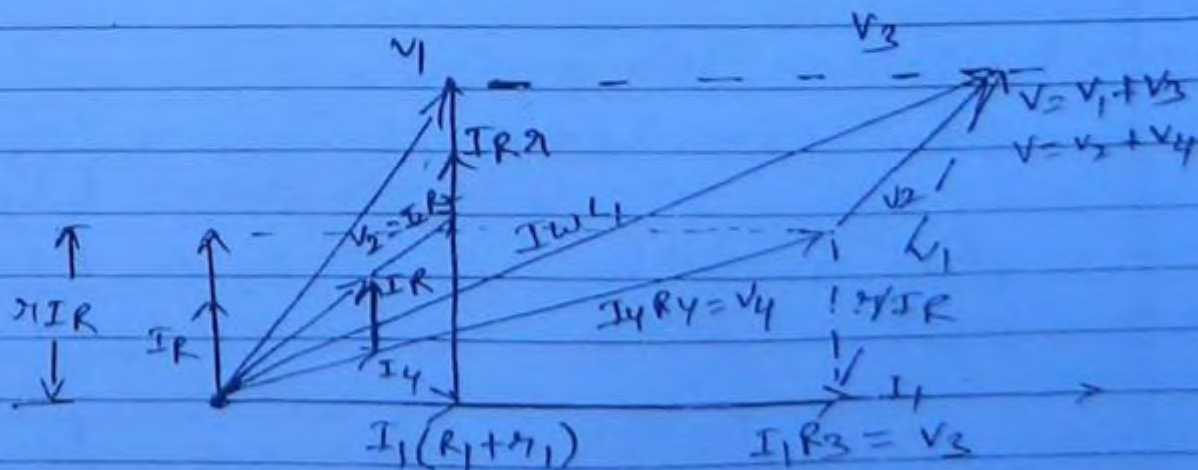

- ① I_1 as Ref
- ② $V_1 = I_1 (R_1 + j\omega L_1)$
- ③ $V_2 = I_1 R_3$
- ④ $V_3 = IR / \omega C$ IR leads V_3 by 90°
- ⑤ IR is phase to IR
- ⑥ $V_4 = V_3 + IR$
- ⑦ $V_4 = I_4 R_4$
- ⑧ $I_2 = I_4 + IR$
- ⑨ $V_2 = I_2 R_2$
- ⑩ $V_1 = V_2 + IR$
- ⑪ $V = V_1 + V_3$
- ⑫ $V = V_2 + V_4$

Owens Bridge: -

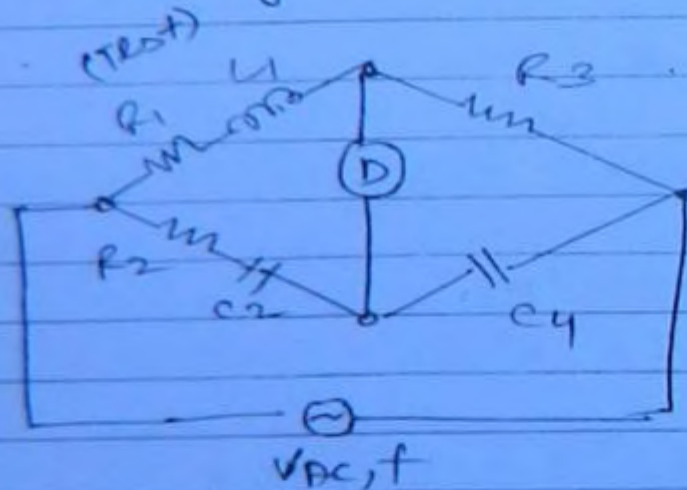

$$Z_1 Z_2 = Z_3 Z_4$$

$$(R_1 + j\omega L_1) \left(R_2 + \frac{1}{j\omega C_2} \right) = R_3 \left(\frac{1}{j\omega C_4} \right)$$

$$\frac{R_1}{j\omega C_4} + \frac{j\omega L_1}{j\omega C_4} = \frac{R_3 R_2 + \frac{R_3}{j\omega C_2}}{j\omega C_4}$$

$$R_3 R_2 = \frac{L_1}{C_4}$$


$$\frac{R_1}{C_4} = \frac{R_3}{C_2}$$

$$\therefore \left[L_1 = C_4 R_3 R_2 \right] \quad \left[R_1 = \frac{R_3 C_4}{C_2} \right]$$

Air Core: -



(112)

Iron Core: -

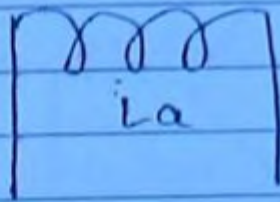


$$L_a = \frac{N^2 \mu_0 A}{l}$$

$B \propto \phi$

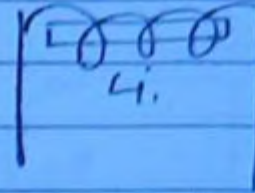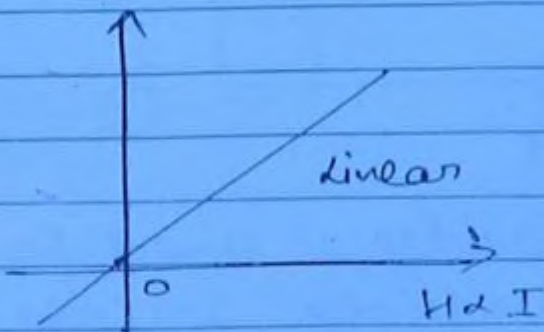

$$L_i = \frac{N^2 \mu_0 A \cdot \mu_r}{l}$$

$$L_i = L_a \cdot \mu_r$$

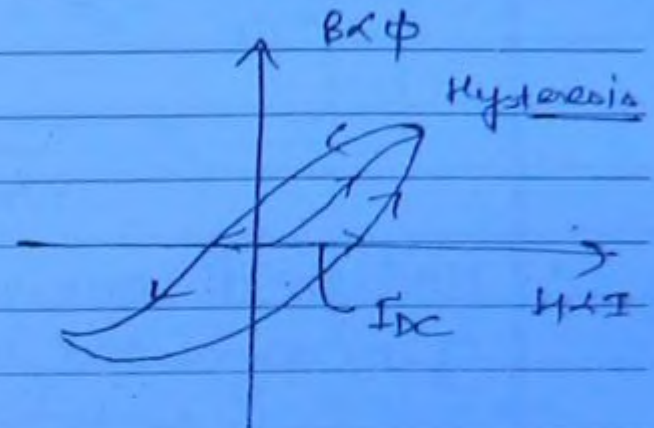


$$L_i = R_2 R_3 C_4$$

$$\frac{N^2 \mu_0 A \mu_r}{l} = R_2 R_3 C_4$$

$$\mu_r = \frac{R_2 R_3 C_4 \cdot l}{N^2 \mu_0 A}$$

For eliminating I_{DC} we use modified Owen's Bridge.

Modified Owen's Bridge \rightarrow

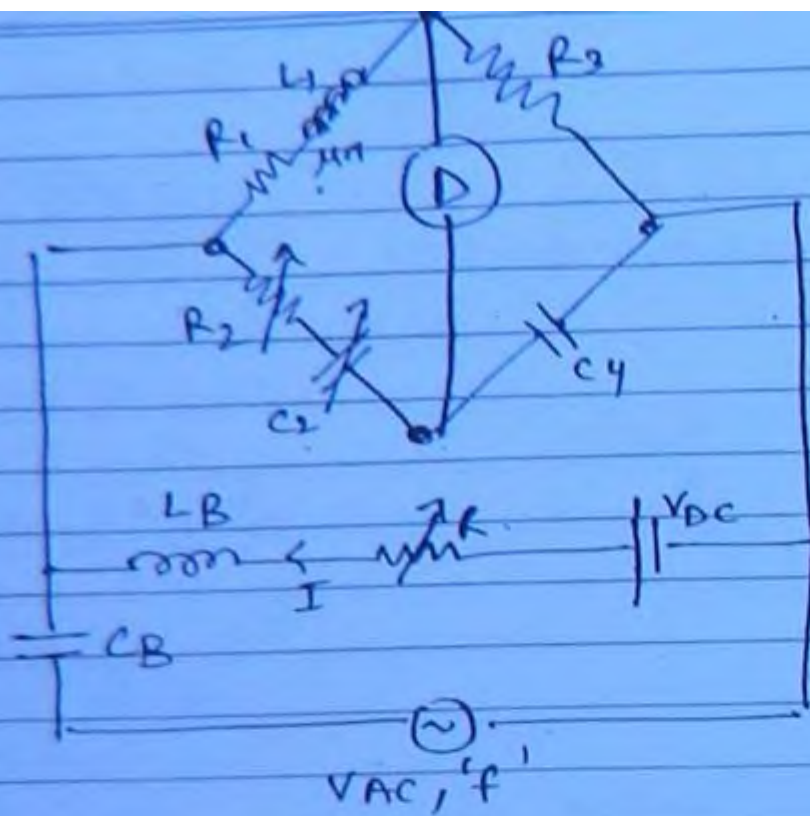

118



- Modified owens Bridge is used for measurement of incremental inductance. In case of air core coil relation ϕ vs flux and current is linear and there is no residual current present if $\phi = 0$.
- In case of iron core coil the ϕ and i produces hysteresis effect small DC Component is present even $\phi = 0$. Due to this the measured value of inductance does not give accurate value.
- To compensate DC Component external DC source is used in the bridge circuit with a variable resistor. The bridge is once again balanced including dc and ac source and L_1 is calculated in terms of R_2, R_3 & C_4 from this μH is calculated.
- The Blocking inductor used to measure block ac and blocking capacitor C_B used to block dc.

Measurement of C:-



(114)

- (1) De Sauty's bridge - $C, D = \tan \delta$
- (2) Schering bridge - $C, D, \epsilon, \epsilon_r$

Pure Capacitor

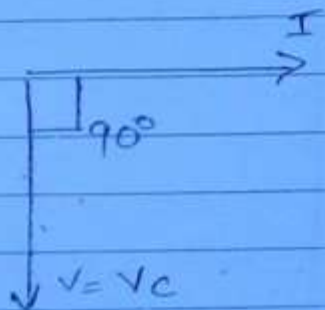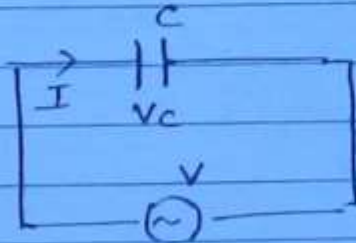

practical capacitor ~

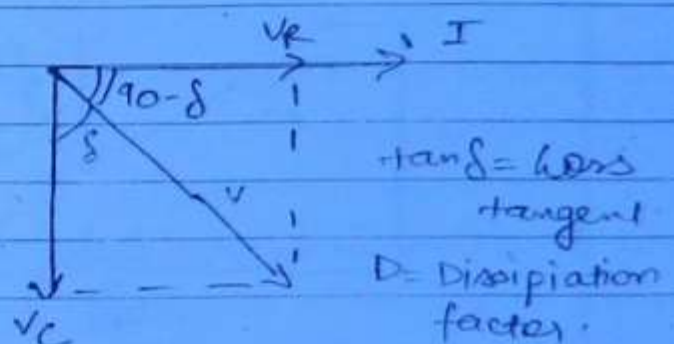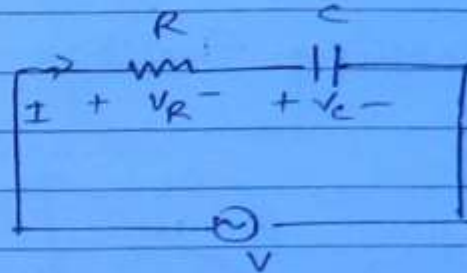


$$D = \tan \delta = \frac{V_R}{V_C} = \frac{RI}{I/\omega C}$$

$$D = \omega CR$$

$$D = \frac{1}{Q}$$

Q = Quality factor.

(i) De Sauty Bridge ~

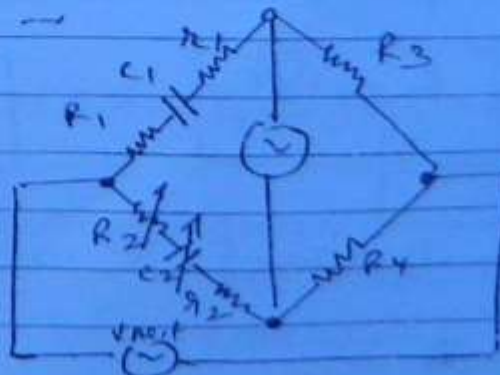

Balance Condition,


$$Z_1 Z_4 = Z_2 Z_3$$

(28)

$$C_1 = \frac{R_4 C_2}{R_3}; \quad R_1 = \frac{(R_2 + R_3) R_3}{R_1} - R_1$$

$$\Rightarrow D = \omega C_1 R_1 \quad R_1 = \frac{(R_2 + R_3) R_3}{R_1} - R_1$$

(2) Schering Bridge :-

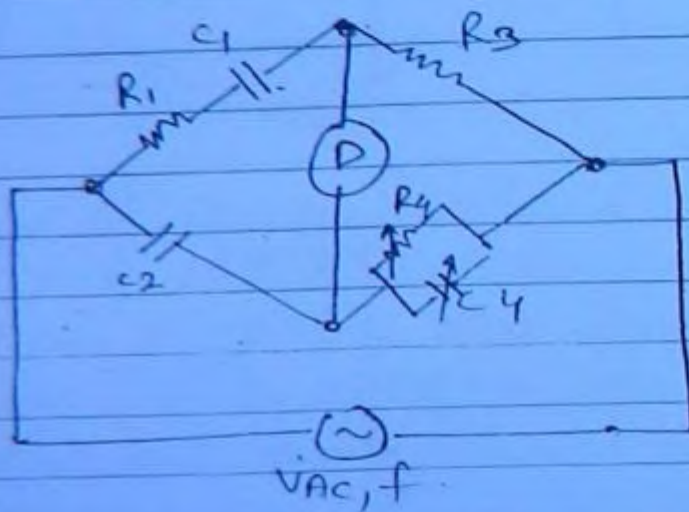

Bridge Balance :-

$$Z_1 Z_4 = Z_2 Z_3$$

$$\left(R_1 + \frac{1}{j\omega C_1} \right) \left[\frac{R_4}{1 + j\omega C_4 R_4} \right] = \frac{R_3}{j\omega C_2}$$

Separate Real & Imaginary terms.

$$R_1 = \frac{R_3 C_4}{C_2}; \quad C_1 = \frac{R_4 C_2}{R_3}$$

$$D = \tan \delta = \omega C_1 R_1$$


$$\Rightarrow \omega \cdot \frac{R_3 C_4}{C_2} \cdot \frac{R_4 C_2}{R_3}$$

$$\boxed{D \Rightarrow WR4 C4.}$$

(121)

Application \rightarrow

Including ϵ_r :-

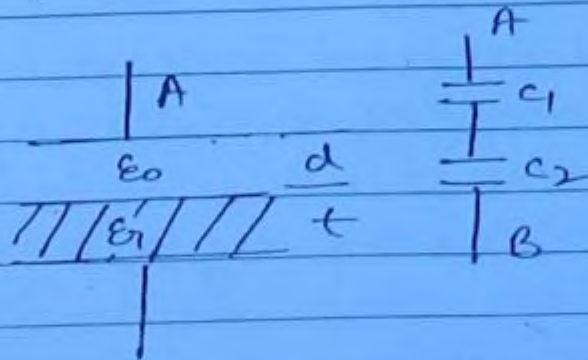

$$C_{AB} = \frac{C_1 C_2}{C_1 + C_2}$$


$$\rightarrow \frac{\epsilon_0 A}{d}, \frac{\epsilon_0 \epsilon_r A}{t}$$

$$\frac{\epsilon_0 A}{d} + \frac{\epsilon_0 \epsilon_r A}{t}$$

$$\boxed{C_{AB} = \frac{\epsilon_0 \epsilon_r A}{(\epsilon_r d + t)}} \quad \text{--- (1)}$$

Measurement of ϵ_r :-

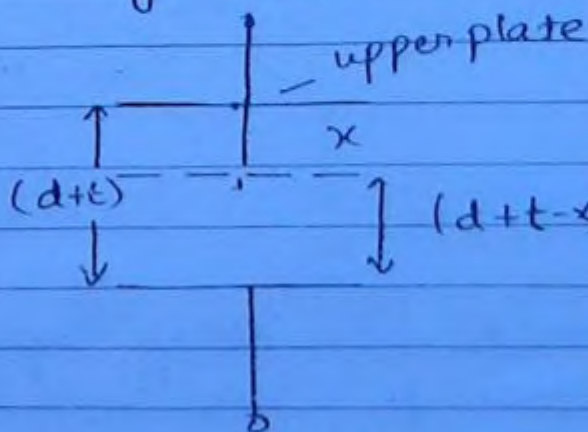Remove dielectric & adjust upper plate to distance 'x' to get same value of C_{AB} :-



$$C_{AB} = \frac{\epsilon_0 A}{(d+t)-x} = \frac{\epsilon_0 \epsilon_r A}{(\epsilon_r d + t)}$$

$$t + \epsilon_r d = d \epsilon_r + t \epsilon_r - x \epsilon_r$$

$$\boxed{\epsilon_r = \frac{t}{t-x}}$$


t = thickness of dielectric
x = Distance adjusted by upper cap. plate

Due to imbalance in the voltages of the arms of the bridge stray capacitance exist b/w the arms and arms to the ground this will causes error in the measurement of unknown capacitance, inductance, ϵ_r , μ_r etc. To eliminate this effect a metal earthed screen is provided around the bridge in case of screening bridge and the screen is connected to the earth so that stray capacitance voltage is discharged to the ground and hence its effect is eliminated. 1.

In case of other bridge circuit's Wagner Earth or Ground Connection is used.

(122)

Wagner Earth or Ground Connection :-

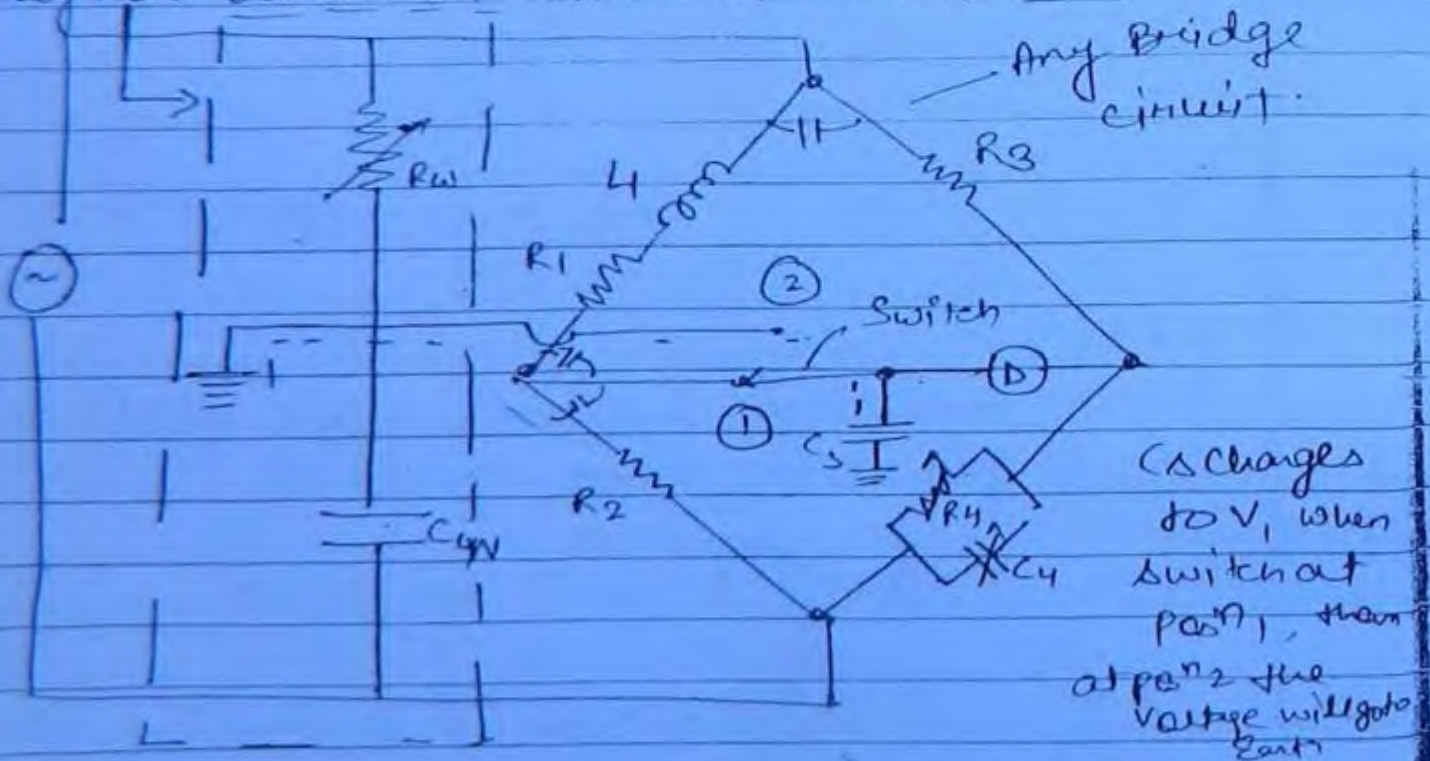

R_W = Wagner Resistance
 C_W = Wagner Capacitance

C_S = stray Capacitance
 b/w arms & arms
 to ground

Wagner earth or ground connection is used to eliminate effect of stray capacitance existing b/w the ^{bridge} arms and arms to the ground.

(723)

Procedure:-


Initially, switch is kept at posⁿ 1 by adjusting the resistor R_4 and C_4 . The detector is balanced by this time the stray capacitance C_s charge to a voltage V_1 .

Now the switch is moved to posⁿ 2 by adjusting R_w bridge is balanced so that the capacitor C_s is discharged to a value to zero through ground.

Now the switch is moved once again to the position 1 by adjusting R_4 , C_4 bridge is balanced C_s is charged to voltage V_2 Now the switch is moved to posⁿ 2 and this voltage is discharged by R_w . This process continues until in either position of switch 1 or 2. The detector indicate the zero value without changing R_w & R_4, C_4 this corresponding to C_s is at ground potential i.e the effect of stray capacitance is eliminated. If wagner correction is initially applied to the bridge circuit's after balancing C_s (eliminating) the actual values of unknown Q & f are measured.

Measurement of frequency (f):-

Wein Bridge $\omega = 2\pi(f)$

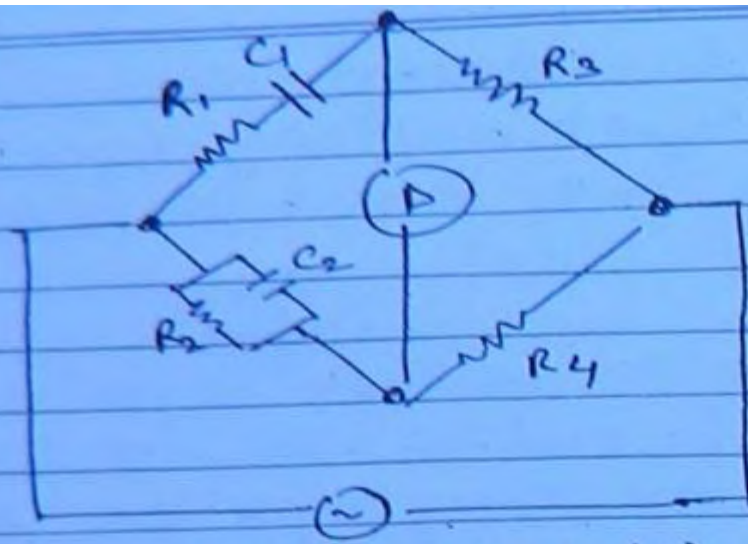

(124)

Balance of Bridge \rightarrow

$$Z_1 Z_4 = Z_2 Z_3$$

$$\left(R_1 + \frac{1}{j\omega C_1} \right) R_4 = \frac{R_3 R_2}{(1 + j\omega C_2 R_2)}$$

$$(1 + j\omega C_1 R_1) (1 + j\omega C_2 R_2) R_4 = R_2 R_3 (j\omega C_1)$$

$$[1 + j\omega(C_1 R_1 + C_2 R_2) - \omega^2 R_1 R_2 C_1 C_2] R_4 = j\omega C_1 R_2 R_3$$

Separate Real & Imag terms.

$$1 - \omega^2 R_1 R_2 C_1 C_2 = 0$$

$$\omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad ; \quad f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

Imaginary terms: -

$$j\omega(C_1 R_1 + C_2 R_2) R_4 = j\omega C_1 R_2 R_3$$

$$\frac{C_1 R_1}{C_1 R_2} + \frac{C_2 R_1}{C_1 R_2} = \frac{R_3}{R_4} \quad (125)$$

$$\left[\frac{R_1}{R_2} + \frac{C_2}{C_1} = \frac{R_3}{R_4} \right]$$

$$\rightarrow \text{If } R_1 = R_2 = R, \quad C_1 = C_2 = C$$

$$\left[f = \frac{1}{2\pi C} \right], \quad \left[\frac{R_3 - 2}{R_4} \right]$$

Limitation \rightarrow

If a signal containing harmonics than the bridge balanced is difficult. Hence, it is not suitable for measurement of harmonic signal.

Medium R \rightarrow wheat stone

\rightarrow Carey Foster Slide wire \rightarrow (Compa)

Low R \rightarrow Kelvin Double bridge

High R \rightarrow Meggar

Measurement of R :-


\rightarrow Winding Resistance of Electrical
Earth conductors etc.

(i) Low Resistance - ($R \leq 1 \Omega$)

(ii) Medium Resistance - ($1 \Omega < R \leq 100 K \Omega$)

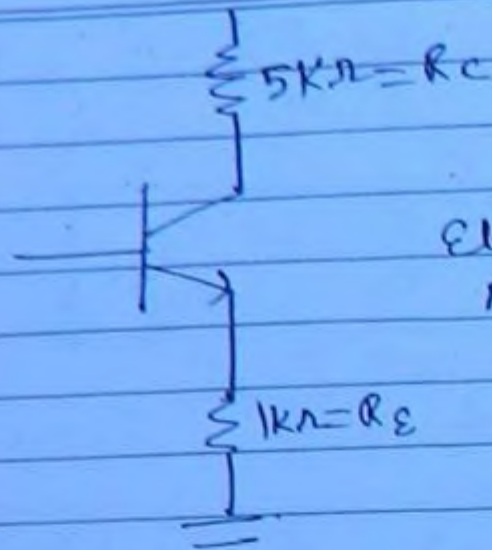(iii) High Resistance - $R > 100 K \Omega$

\swarrow Winding Insulation of E.H.C, Cable Insulation \downarrow Electrical Accessories



Electronic
Accessories.

126


Medium Resistance Methods →

- (i) Voltmeter Ammeter Method. (V-I) Method
- (ii) Wheat Stone Bridge. → Practical.
- (iii) Carey Foster Bridge.
- (iv) Substitution Method.
- (v) Ohm Meter.

(i) V-I Method :-

$$R = \frac{V}{I} = \frac{\text{Voltmeter Reading}}{\text{Ammeter Reading}} = R_m$$

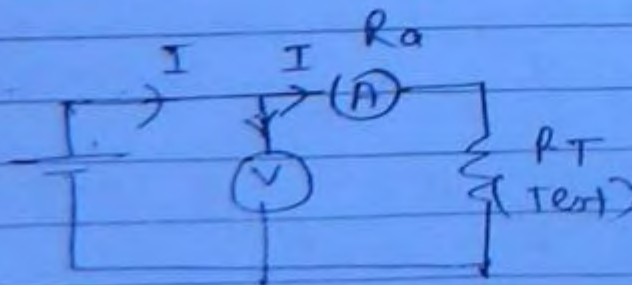(a) Ammeter near to test Resistance (R_T).



$$V = I(R_a + R_T)$$

$$\frac{V}{I} = R_a + R_T$$

$$R_m = R_a + R_T$$


$$\% E = \frac{R_m - R_T}{R_T} \times 100$$

$$\% E = \frac{R_a}{R_T} \times 100$$

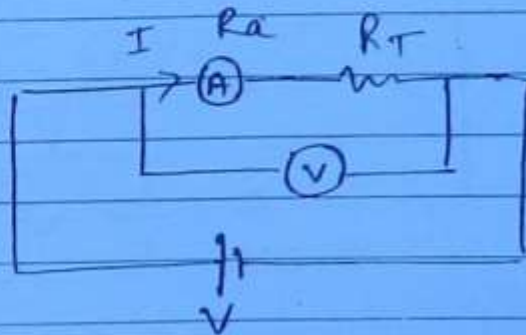(127)


E is low if $R_T \gg R_a$

Medium $R \rightarrow 1\Omega \rightarrow \text{Low}$
 $\rightarrow 100\text{K}\Omega \rightarrow \text{High}$



This arrangement is suitable for measurement of R_T higher than R_a so that error is minimum and hence suitable for measuring high resistances in the medium scale.

(b) Voltmeter near to R_T :-

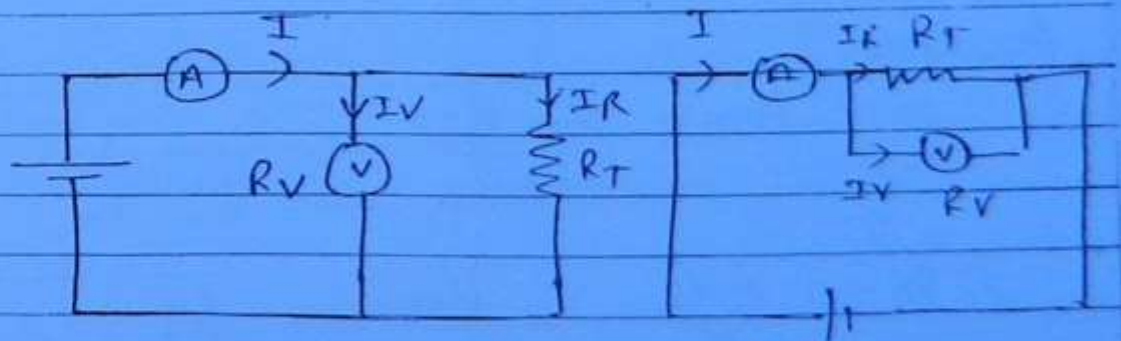

Assume R_a is negligible.
 Internal resistance of voltmeter = R_V

Exact Analysis \rightarrow

(128)

$$I = I_R + I_V$$

$$I_V = V/R_V$$

$$I_R = I - I_V$$

$$I_R = I - V/R_V$$

$$R_T = V/I_R$$

$$\% \text{ Error} = \frac{R_m - R_T}{R_T}$$

$$\Rightarrow \frac{V/I - V/I_R}{V/I_R}$$

$$\Rightarrow \frac{I_R - I}{I}$$

$$\Rightarrow \frac{-I_V}{I} = -\frac{V}{I R_V}$$

$$\boxed{\% \text{ Er} = -\frac{V}{I R_V} \times 100}$$

V = Voltmeter Reading
 I = Ammeter Reading.

Approximate Analysis \rightarrow

Assume,

$$R_m = \frac{R_V R_T}{R_V + R_T} \approx R_T = \frac{V}{I}$$

$$\therefore \% \text{ Er} = \frac{-V}{I R_V} = -\frac{R_m}{R_V} = -\frac{R_T}{R_V}$$


Er is low if $R_T \ll R_V$

Hence suitable for low value of R_T .

(ii) Substitution Method:-

(129)

(Test)

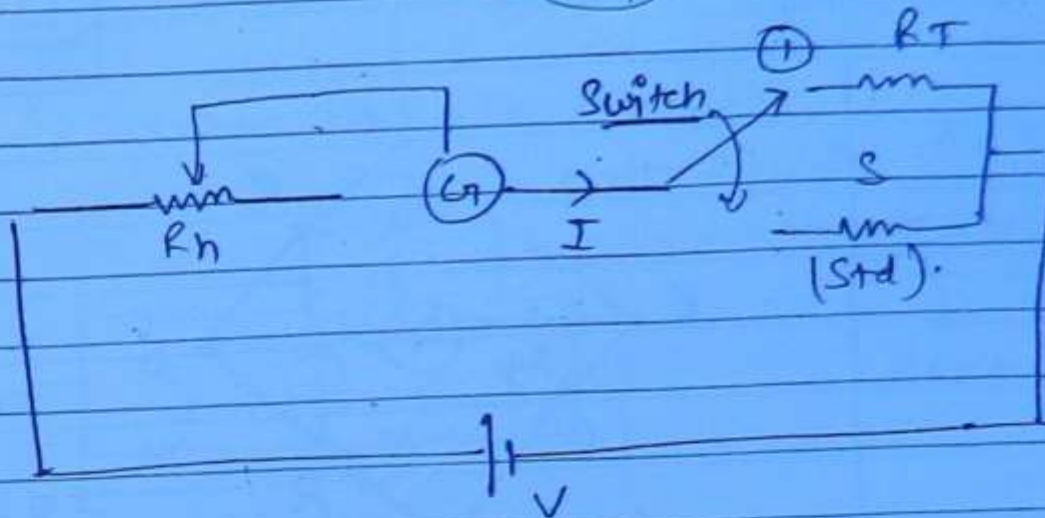

Switch at (1)

Switch at (2)

$$V = I_1 [R_h + R_T + R_g] \quad V = I_2 [R_h + R_g + S]$$

(1) (2)

$$(1) = (2)$$


$$I_1 [R_h + R_T + R_g] = I_2 [R_h + R_g + S]$$

$$R_T = \frac{I_2}{I_1} [R_h + R_g + S] - (R_h + R_g)$$

$$\text{If } I_1 = I_2, \quad \boxed{R_T = S}$$

③ WHEATSTONE BRIDGE :-


130

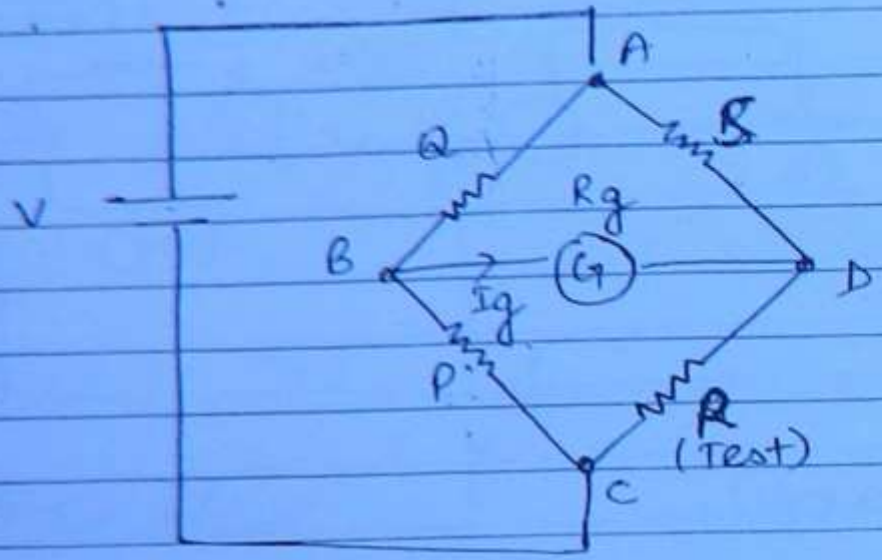

$$I_g = 0$$

$$RQ = PS$$


$$R = \frac{PS}{Q}$$

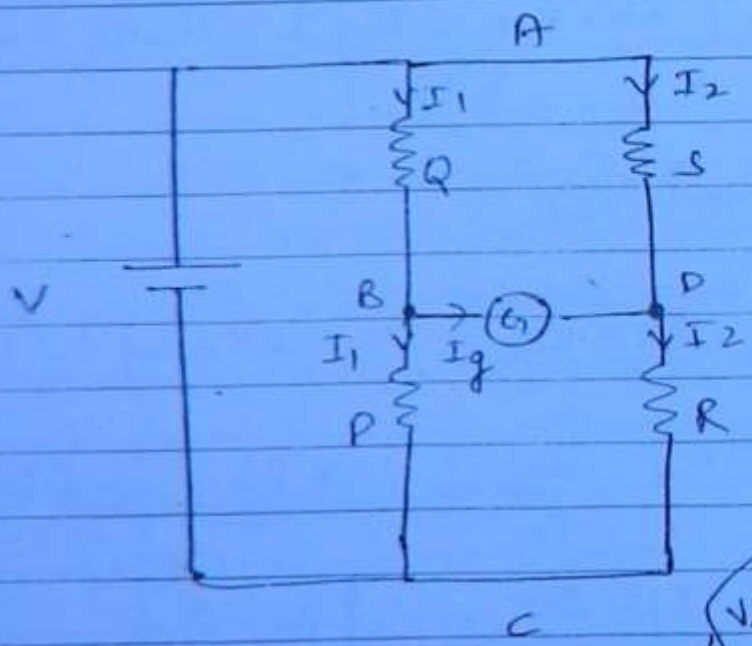

$$V_{BD} = V_B - V_D$$


$$\Rightarrow \frac{P}{P+Q} \cdot V - \frac{R}{R+S} \cdot V$$
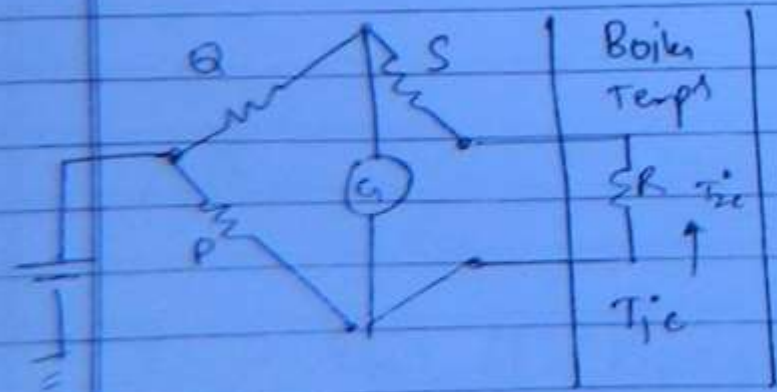
$$V_{BD} = V \left[\frac{PS - RQ}{(P+Q)(R+S)} \right]$$



$$R_2 = R_1 [1 + \alpha (T_2 - T_1)]$$


Calculation of I_g - R_{th}

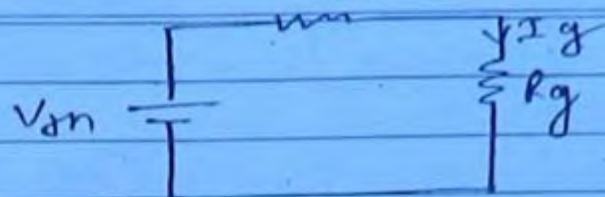

$$I_g = \frac{V_{th}}{R_{th} + R_g}$$

(131)

Theremin Equivalent ckt.

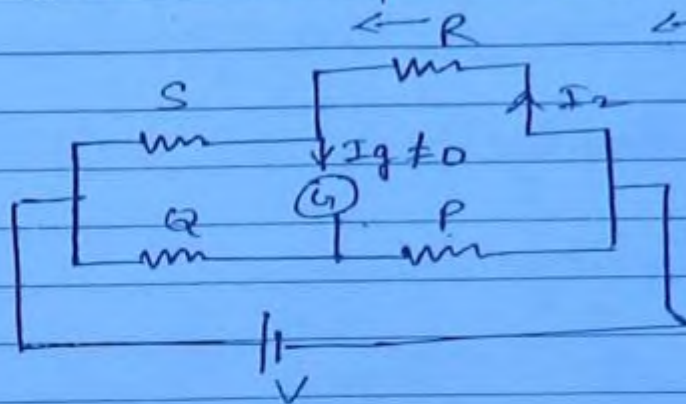


Fluid 600 T/hour

$$I_2^2 R = R_c$$

Heat.

$V_{th} = V_{BD}$

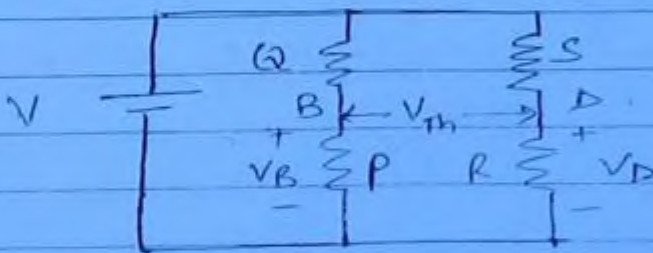


$$V_{th} = V_B - V_D$$

$$= V \left[\frac{P}{P+Q} - \frac{R}{R+S} \right]$$


$$V_{th} = V \left[\frac{PS - RQ}{(P+Q)(R+S)} \right]$$

$R_{th} = R_{BD} [V=0]$

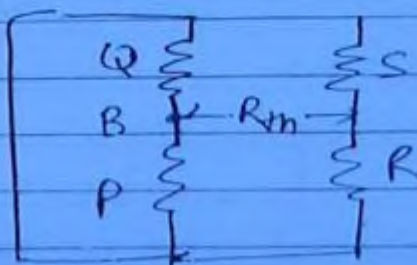


$$R_{th} = R_{BD} = \frac{PQ}{P+Q} + \frac{RS}{R+S}$$

$$I_g = \frac{V_{th}}{R_{th} + R_g}$$

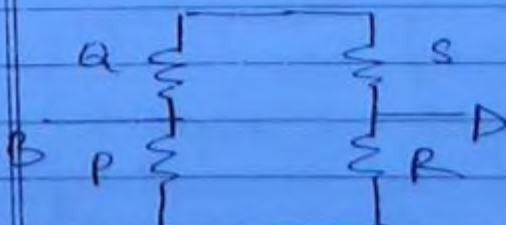
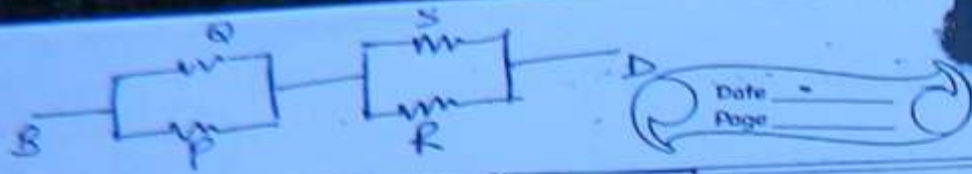
$$I_g = \frac{V [PS - RQ]}{(P+Q)(R+S)(R_{th} + R_g)}$$



2) Bridge is balanced $I_g = 0$

$$PS - RQ = 0$$

(132)

$$R = \frac{PS}{Q}$$

→ Measurement of Test resistance.

Sensitivities of Bridges :-

(i) Current Sensitivity

$$S_i = \frac{\theta}{I_g} \text{ mm/}\mu\text{A}$$

(ii) Voltage Sensitivity

$$S_v = \frac{\theta}{V_{th}} \text{ mm/V}$$

(iii) Bridge Sensitivity


$$S_B = \frac{\theta}{(\Delta R/R)} \text{ deflection of galvanometer (mm)}$$

$$S_B = \frac{V_{th} \cdot S_v}{(\Delta R/R)} \text{ mm}$$

In case of bridge circuit sensitivity is an important parameter compare to accuracy, resolution, precision, linearity etc. for a small change in the non electrical quantity to be measured is to be sensed by changing the resistance R to a value $(R + \Delta R)$

This change should be detected by change in the current through the galvanometer, (I_g) which produces deflection so that the galvanometer indicates max^m value i.e its sensitivity is maximum. (P33)

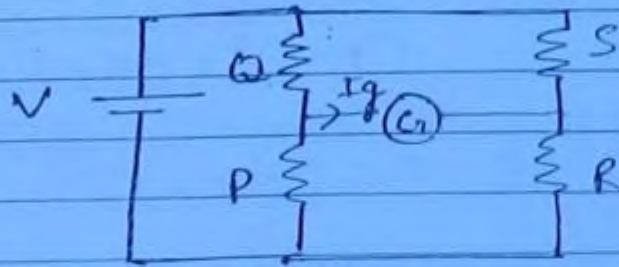Condition for Max^m Sensitivity [S_{Bmax}]




Under Bridge balance: -

$$\frac{P}{Q} = \frac{R}{S}$$

$$\left[\frac{P}{P+Q} = \frac{R}{R+S} \right] \quad \text{--- (1)}$$

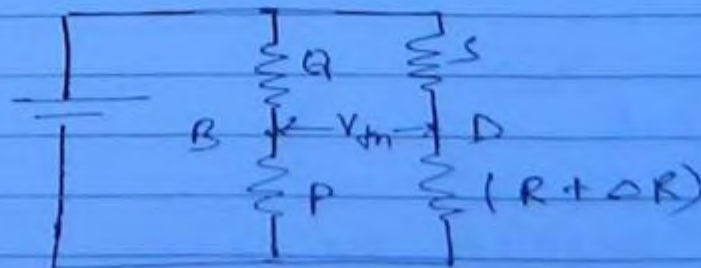for small change in R to $(R + \Delta R)$:-



$$V_m = V_B - V_D$$

$$\Rightarrow V \left[\frac{P}{P+Q} - \frac{(R+\Delta R)}{(R+\Delta R+S)} \right]$$

(134)

$$\Rightarrow V \left[\frac{R}{R+S} - \frac{R+\Delta R}{(R+\Delta R+S)} \right]$$

From Ist.

$$V_{th} = V \left[\frac{R(R+\Delta R+S) - (R+S)(R+\Delta R)}{(R+S)^2 + (R+S)\Delta R} \right]$$

Assume $(R+S)\Delta R \ll (R+S)^2$

$$V_{th} = V \left[\frac{R^2 + \cancel{R\Delta R} + RS - \cancel{R^2} - \cancel{R\Delta R} - S^2}{(R+S)^2} \right]$$

$$\boxed{|V_{th}| = \frac{V \cdot S \cdot \Delta R}{(R+S)^2}} \quad \text{--- (2)}$$

$$S_B = \frac{V_{th} \cdot S_V}{(\Delta R/R)} = \frac{V S \Delta R \cdot S_V}{(\Delta R/R) (R+S)^2}$$

$$\Rightarrow \frac{V S_V}{\left(\frac{R^2 + 2RS + S^2}{R} \right)}$$

$$S_B = \frac{V S_V}{\left(\frac{R}{S} + \frac{S}{R} + 2 \right)}$$

for max^m value of S_B

$$\left[\frac{R}{S} = \frac{S}{R} = \frac{P}{Q} = 1 \right]$$


→ condition for $S_{B \max}$

$$S_B(\max) = \frac{V_S v}{4}$$

(133)


Under Bridge balance condition.

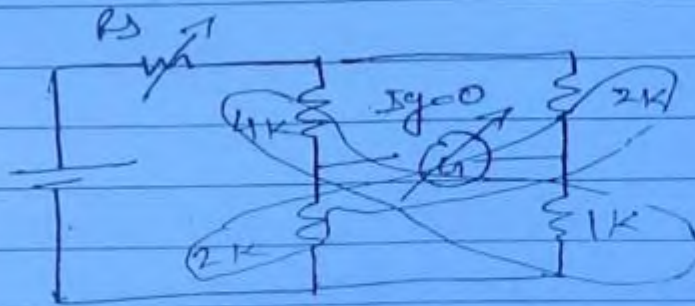- (i) the product of resistances in opposite arms of the bridges are equal i.e. $PS = RQ$.
- (ii) If $PS = RQ$ then $I_g = 0$ and it is independent of galvanometer internal resistance and source voltage internal resistance.
- (iii) the voltage across the galvanometer is zero.



when $2K \times 2K = 4K \times 1K$
Then

$$I_g = 0$$

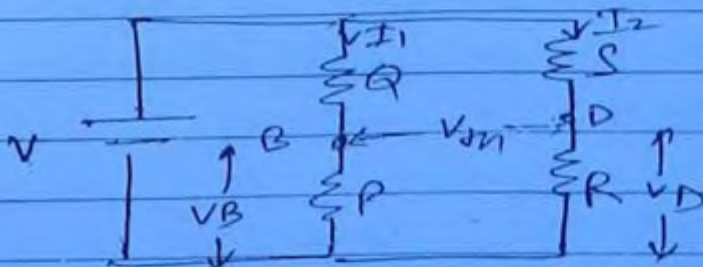

$$PS = RQ$$

$$V_{gm} = V_B - V_D = 0$$

$$V_B = V_D \quad (I_g = 0)$$

$$I_1 P = I_2 R$$

$$\frac{I_1}{I_2} = \frac{R}{P}$$


$$V_B = V_D$$

$$I_1 Q = I_2 S$$

$$\frac{I_1}{I_2} = \frac{S}{Q}$$

$$\boxed{\frac{R}{P} = \frac{S}{Q}}$$

Find I :-

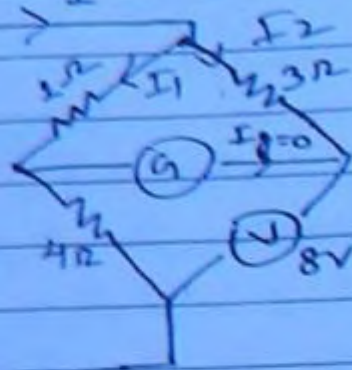

136

$$4I_1 = 8$$

$$I_1 = 2 \text{ A}$$

$$2I_1 = 3I_2$$

$$2 \times 2 = 3I_2$$

$$I_2 = \frac{4}{3} \text{ A}$$


$$I = I_1 + I_2$$

$$\Rightarrow 2 + \frac{4}{3}$$

$$I \Rightarrow \frac{10}{3} \text{ A}$$

Limitation of wheat Stone Bridge \rightarrow

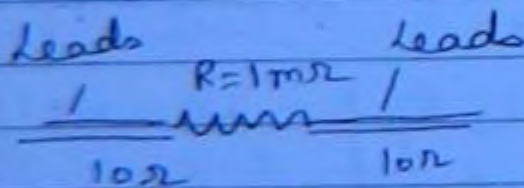
Not suitable for measurement of low resistance because it cannot eliminate the effect of lead resistance.




$$R = \frac{P \cdot S}{Q}$$

$$\Rightarrow \frac{20 \cdot 001}{1}$$


$$\approx 20 \Omega$$

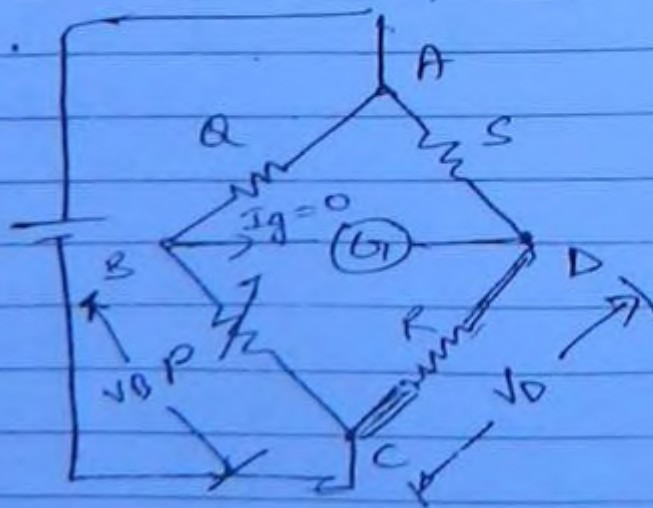


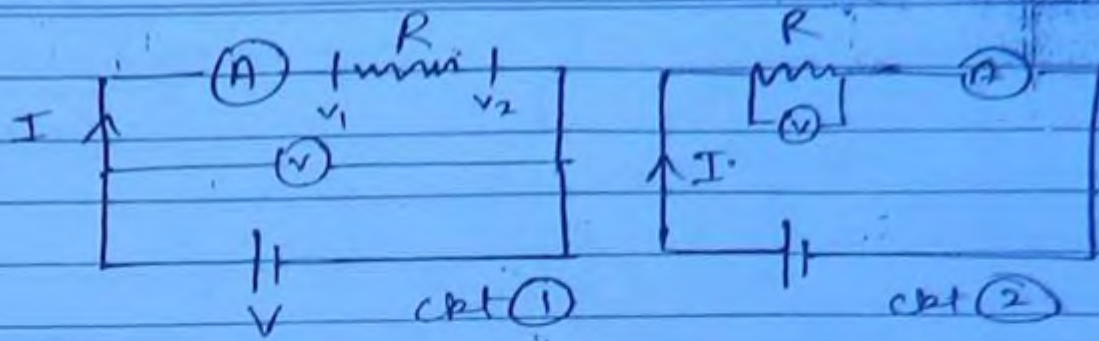


Symbol:-

(137)

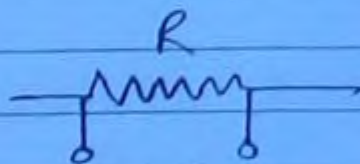Low Resistance :- 

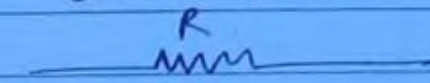Medium Resistance :- 

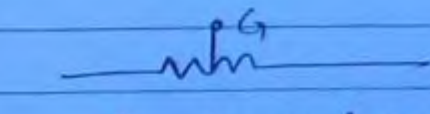
High Resistance :- 


G = Guard terminal.

→ Kelvin Double bridge is used for $\frac{1}{1000}$ elimination of lead resistance hence used for measurement of low resistance.

→ Not suitable for measurement of high resistance due to sensitivity of the bridge is affected due to the leakage current's flowing in the high resistance material.

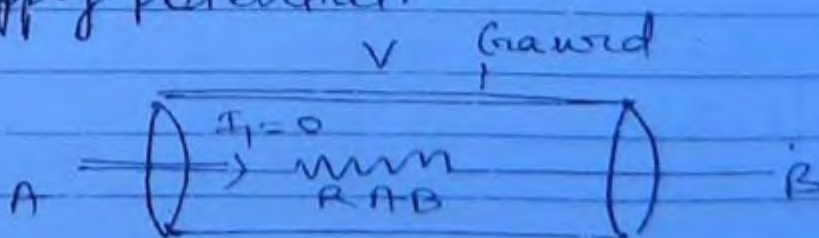→ To eliminate the leakage current effect's guard terminal is provided which is maintained at supply potential.




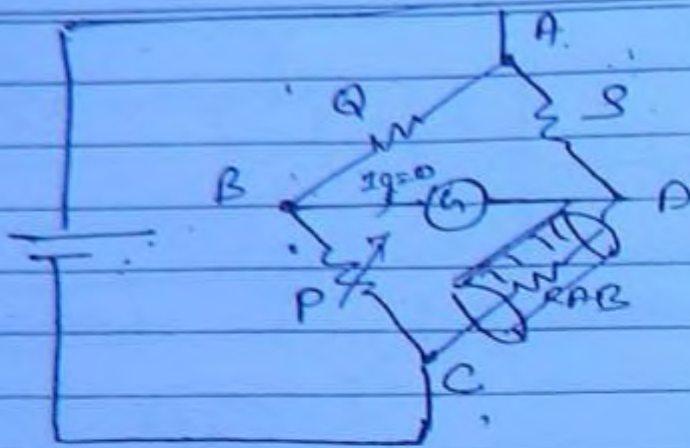

Megohm
bridge.

138

4) Carey Foster slide wire →

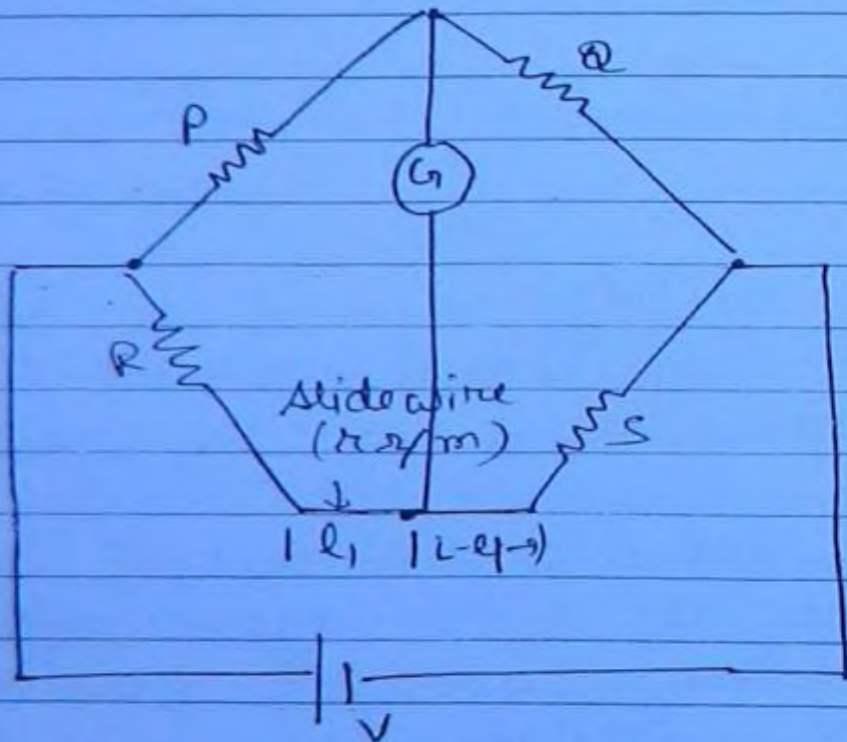


Bridge balance at A :-

$$[R + l_1 r] Q = P [S + (L - l_1) r]$$

$$\boxed{\frac{R + l_1 r}{S + (L - l_1) r} = \frac{P}{Q}} \quad \text{--- (i)}$$

W.P. in interchanging P & S \rightarrow

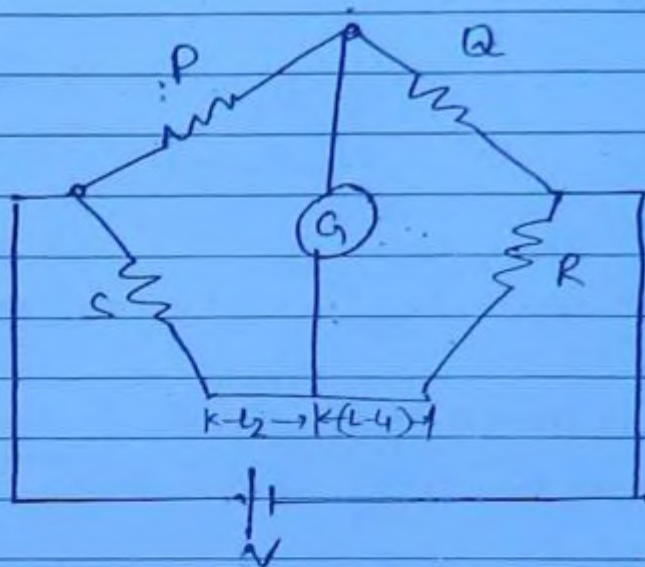

Bridge balanced at B: -

$$\frac{P}{Q} = \frac{S + l_2 r}{R + (L - l_2) r} \quad \text{--- (2)}$$

$$(1) = (2)$$

Solve,

$$\boxed{R - S = (l_2 - l_1) r}$$

Unknown resistance R is measured by comparing with standard resistance value

Ohm Meter: -


$$R = V/I$$

$V \Rightarrow$ Constant

$$R \propto 1/I$$

$$R \propto \frac{1}{\text{Ammeter Reading}}$$

① Series ohm Meter:-

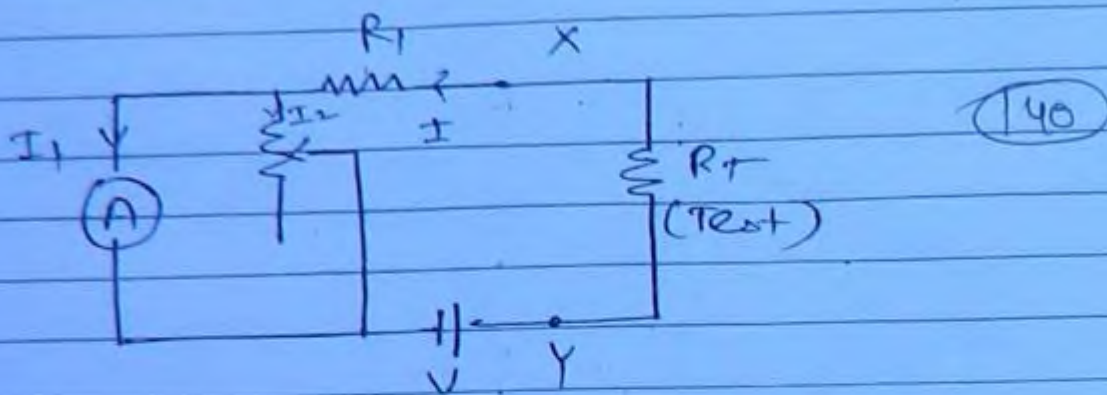

R_2 = Zero Resistance adjustment Resistor.

R_1 = Current Limiting Resistor.

X-Y open

$$R_T = \infty$$

$$I_1 = 0$$


X-Y short.

$$R_T = 0$$

$$I_1 = \text{max}$$

$$(R_T = 0)$$

$$I_{\text{max}} = I_1$$

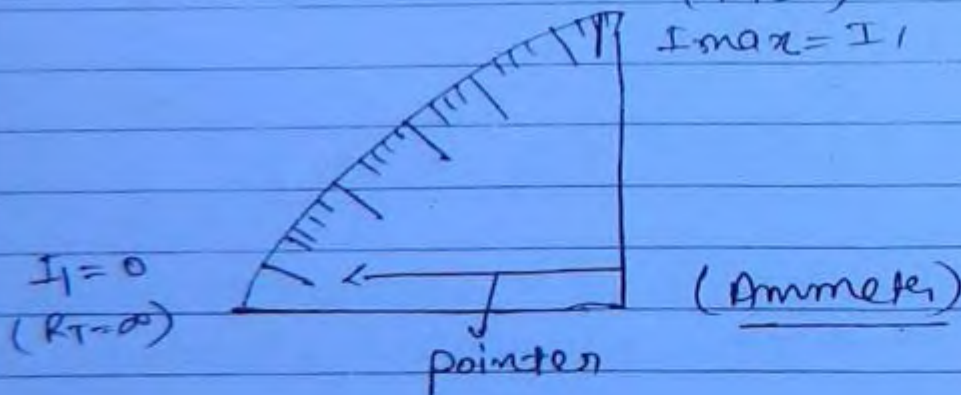


The ammeter is calibrated to measure the resistance over wide range from low value to the high value.

Ammeter is connected in series to the test resistance hence it is called series ohm meter. If the battery source potential is reduced than the current flowing through meter is reduced and indicate less value.

at $R_T = 0$ for adjustment of this value the variable resistance R_2 is used.

(ii) Shunt ohm Meter:-

(T4)

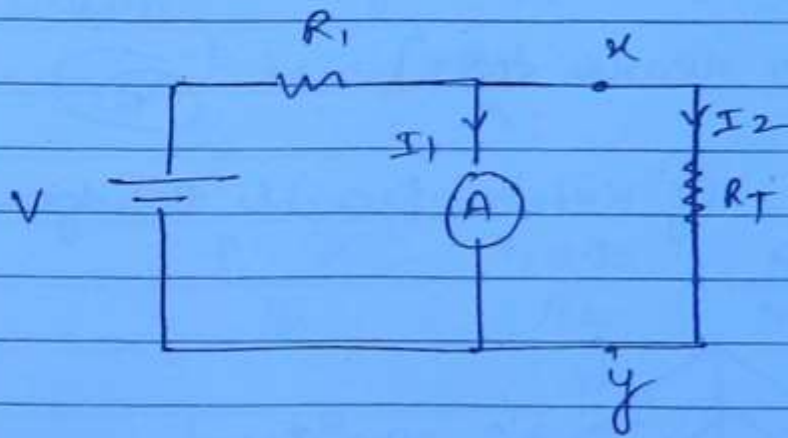

$x-y$ open


$$R_T = \infty$$

$$I_1 = I_{\max}$$

$x-y$ short

$$R_T = 0$$

$$I_1 = 0$$

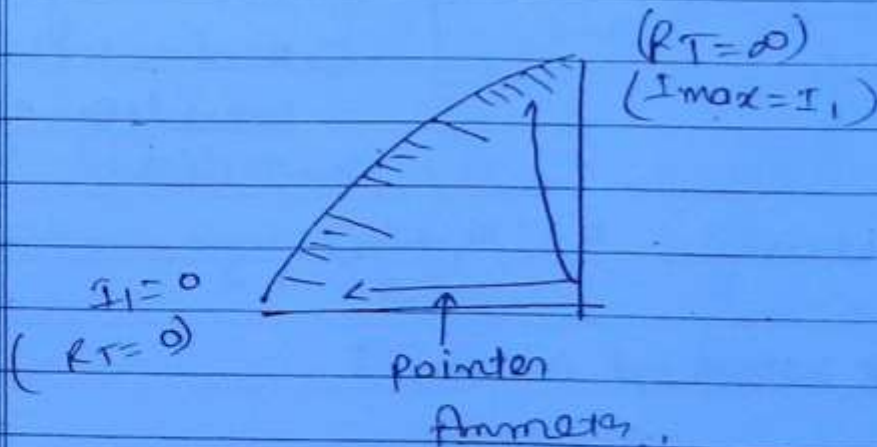


→ It is used for measurement of low resistance in the medium scale.

Low Resistance Measurement Methods:-

- (i) Kelvin Double bridge. \rightarrow Most practical
- (ii) potentiometer Method. (Accuracy is more).
- (iii) V-I Method
[Voltmeter nearer to RT]

(142)

Basic Circuit of Kelvin Double Bridge:-

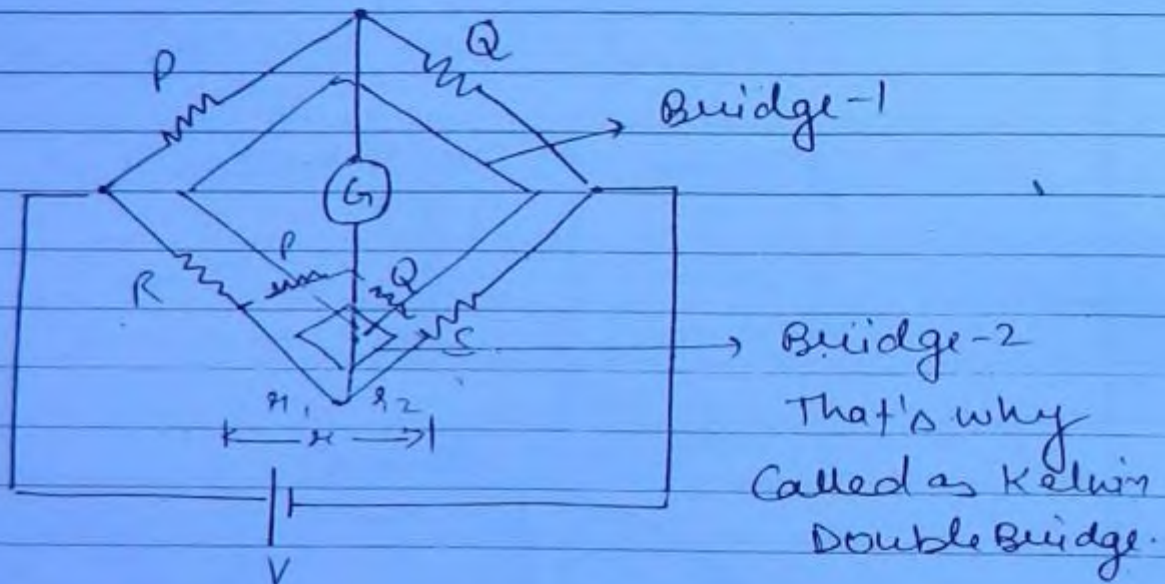

Lead resistance $x = (x_1 + x_2)$

Bridge ~~at~~ balanced at A :-

$$\frac{P}{Q} = \frac{R + x_1}{S + x_2}$$

$$(R + x_1) = \frac{P}{Q} (S + x_2) \quad \text{--- (1)}$$

Including lead Required \rightarrow $R = \frac{P \cdot S}{Q}$

Select) $\frac{P}{Q} = \frac{p}{q} = \frac{r_1}{r_2}$

$$\frac{p}{q} = \frac{r_1}{r_2}$$

(43)

$$\frac{p}{q} + 1 = \frac{r_1}{r_2} + 1$$

$$\frac{p+q}{q} = \frac{r_1+r_2}{r_2} = \frac{r}{r_2}$$

$$r_2 = \frac{qr}{(p+q)} \quad \text{--- (2)}$$

$$r_1 = r - r_2 = r - \frac{qr}{p+q}$$

$$\boxed{r_1 = \frac{pr}{p+q}} \quad \text{--- (3)}$$

Substitute (2), (3) in (1)


$$R + \frac{pr}{p+q} = \frac{P}{Q} S + \frac{P}{Q} \cdot \frac{qr}{(p+q)}$$

Put $P/Q = p/q$

$$R + \frac{pr}{p+q} = \frac{p}{q} S + \frac{p}{q} \cdot \frac{qr}{(p+q)}$$


$$\boxed{R = \frac{P}{Q} S} \rightarrow \text{NO Load Resistance}$$

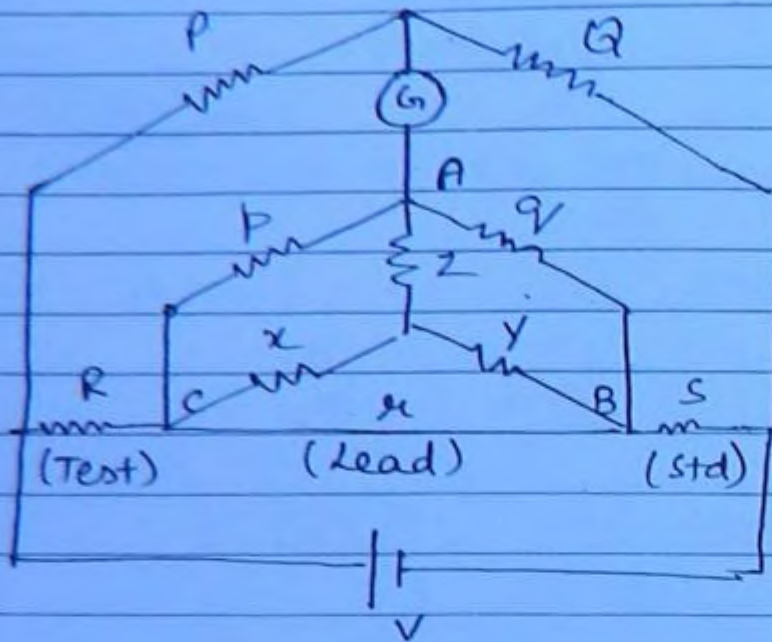Practical Circuit of Kelvin Double bridge \rightarrow




144

Convert Δ into λ

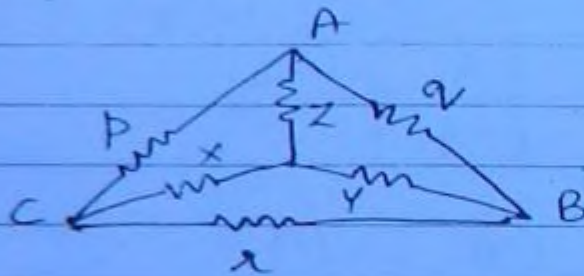

$$x = \frac{p r}{(p + q + r)} \quad \text{--- (1)}$$
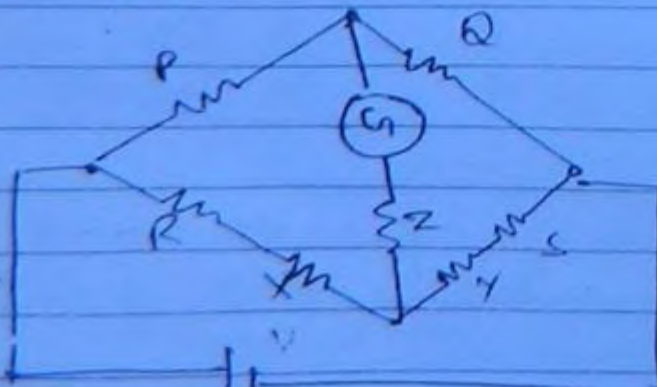
$$y = \frac{q r}{(p + q + r)} \quad \text{--- (2)}$$



Bridge under balance (Ignore r_1)

$$\frac{P}{Q} = \frac{R+X}{S+Y}$$

(145)

$$R+X = \frac{P}{Q} (S+Y) \quad \text{--- (3)}$$

Substitute (1) & (2) in (3) and solve.

$$R = \frac{P}{Q} S + \frac{qR}{p+q+r} \left[\frac{P}{Q} - \frac{p}{q} \right]$$

↑ Including lead resistance effect.

→ If $P/Q = p/q$

$$R = \frac{P}{Q} \cdot S$$

↑ No lead resistance effect.

P/Q = outer ratio arms.

p/q = inner ratio arms.

→ The effect of lead resistance is eliminated if $P/Q = p/q$. And hence, this is suitable for measurement of low resistance. And the accuracy of instrument is more.


Application →

Used for measurement of winding resistance of electrical motor, generator's and transformer's and also used for

measurement of earth conductor resistance

Potentiometer Method :-

(146)

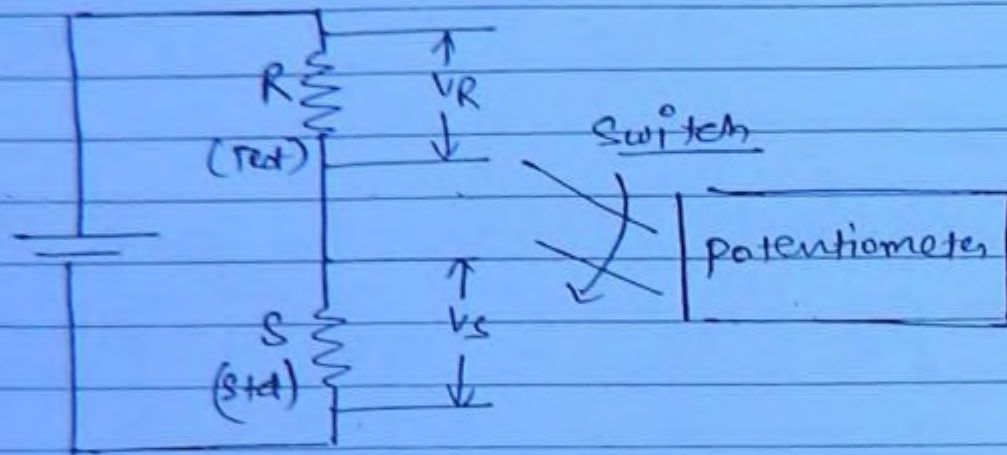

Switch across R

$$\begin{aligned} V_R &= I R \\ I &= V_R / R \end{aligned}$$

Switch across S

$$\begin{aligned} V_S &= I \cdot S \\ I &= V_S / S \end{aligned}$$


$$V_R / R = V_S / S$$

$$R = S \cdot V_R / V_S$$

High Resistance Measurement Methods →

- ① Meggar → Most practical
- ② Loss of charge method
- ③ Direct Deflection method
- ④ Mega ohm bridge.

Loss of charge Method :-

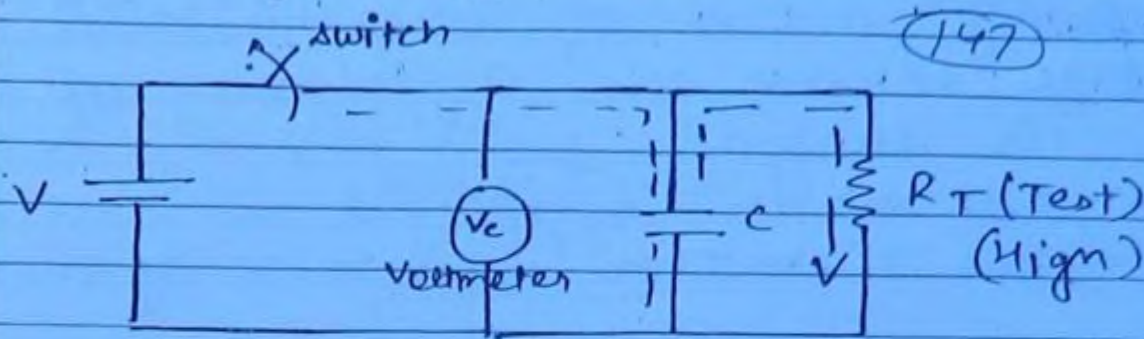

Switch opened at $t=0$


$$V_c = V \cdot e^{-t/RC}$$

$$\frac{V}{V_c} = e^{t/RC}$$

$$\frac{t}{RC} = \ln e (V/V_c)$$

$$R = \frac{t}{C \ln e (V/V_c)}$$
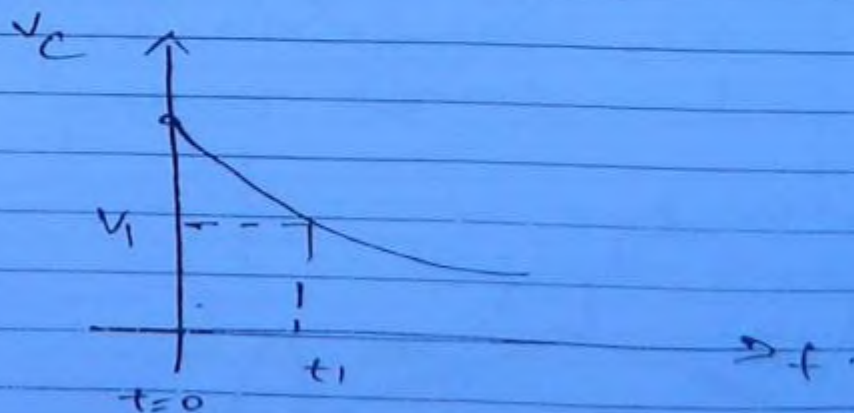
$$R = \frac{0.4343 t}{C \log_{10} (V/V_c)} \quad \text{where } t = \text{seconds}$$



Q Cable insulation resistance is measured by using a loss of charge method the voltage across the capacitance of $0.4343 \mu\text{F}$ is dropped from 10V to 1V in 2min 's when the switch is opened at time $t=0$ then the unknown resistance of the cable is

a) $1\text{M}\Omega$

c) $120\text{M}\Omega$

(148)

b) $2\text{M}\Omega$


d) $180\text{M}\Omega$

Ans

$$R = \frac{0.4343 \times 2 \times 60}{0.4343 \times 10^{-6} \log(19)} \quad (148)$$


$$\Rightarrow 120\text{M}\Omega$$


Direct Deflection Method :-

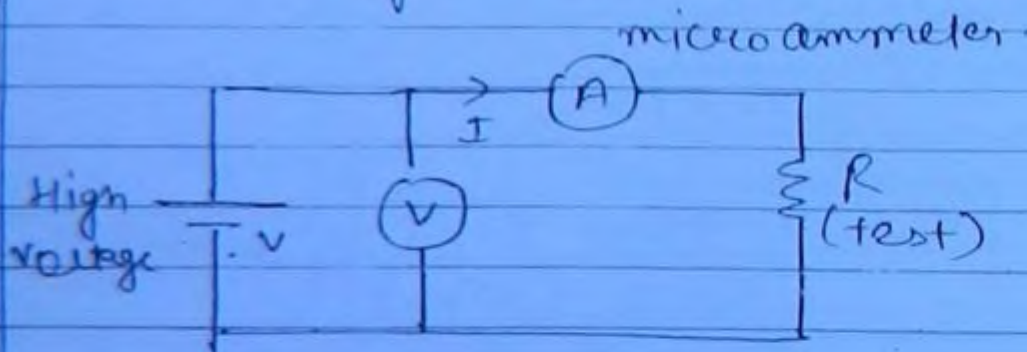

$$R = \frac{V}{I} = \frac{\text{Voltmeter Reading}}{\text{Ammeter Reading}}$$


Mega ohm Bridge :-

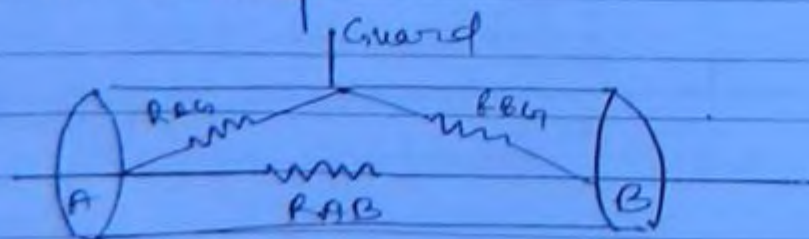

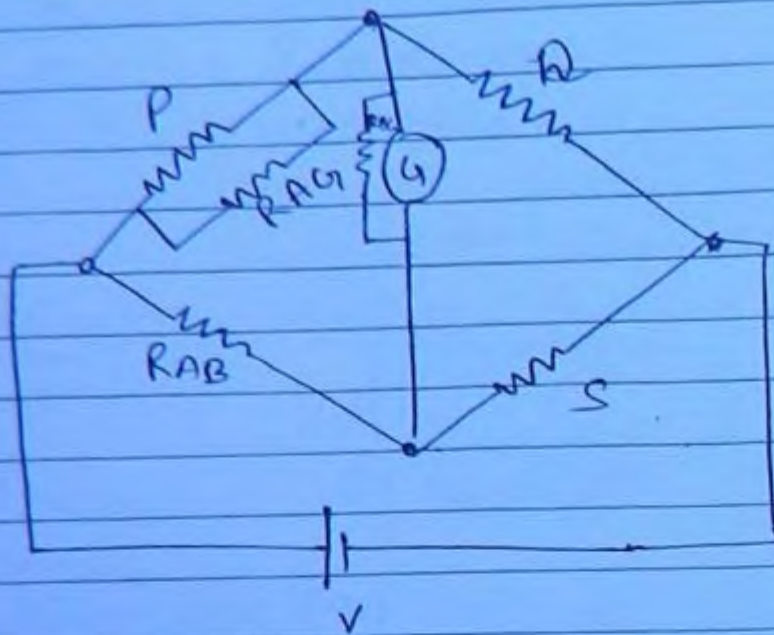

Megohm bridge is working on a principle of wheatstone bridge used to measure high value of resistance's by connecting guard terminal to the supply potential so that the effect of leakage terminals current are eliminated.

pg 45
Q8

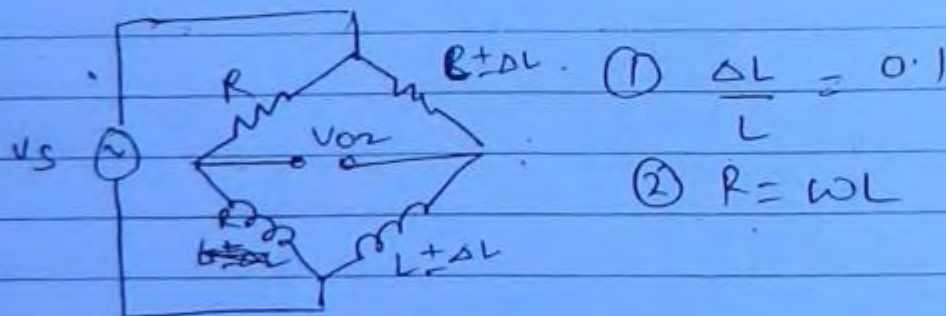

$$V_{th} = V_{O1} = V_B - V_D$$

$$= V_S \left[\frac{R}{R+R} - \frac{j\omega(L+\Delta L)}{j\omega(L+\cancel{\Delta L} + \cancel{R_0})} \right]$$

$$\Rightarrow V_S \left[\frac{1}{2} - \frac{(L+\Delta L)}{2L} \right]$$

$$V_{O1} = \frac{V_S}{2} \left[1 - \left(\frac{L}{L} + \frac{\Delta L}{L} \right) \right] \text{ or } \frac{V_S}{2} \left[1 - \left(\frac{L}{L} - \frac{\Delta L}{L} \right) \right]$$

$$\frac{V_S}{2} [-0.1] \quad \text{or} \quad \frac{V_S}{2} [0.1]$$

$$|V_{01}| = 0.05 V_S \quad (15)$$


Similarly

$$|V_{02}| = 0.05 V_S$$

Q Meter or Voltage Magnifier \rightarrow

Q Meter is working on a principle of series resonance.

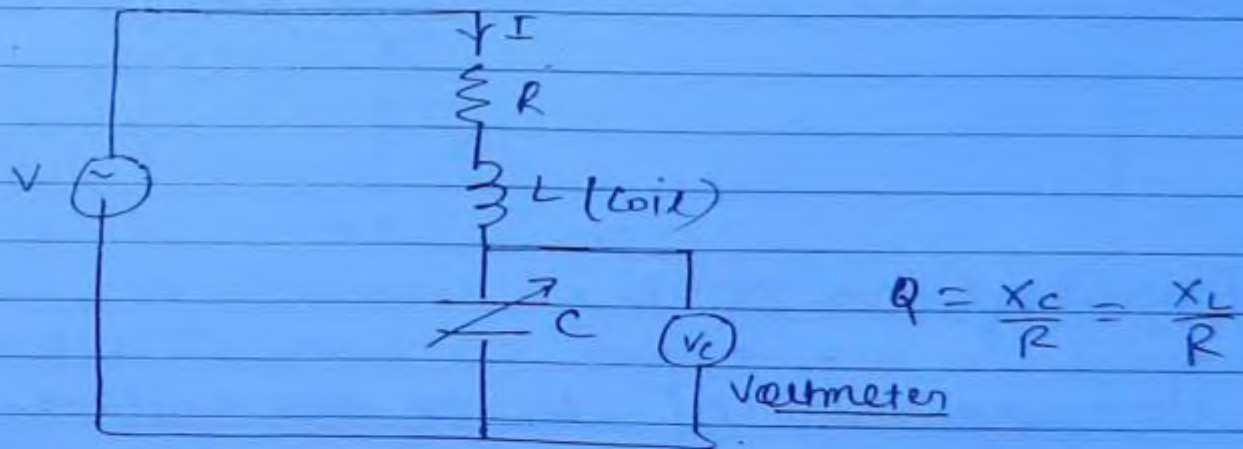Used for measurement of quality factor of the coil, unknown capacitance, inductance self or distributed capacitance of the coil etc.



Series resonance. $X_L = X_C$


$$I = \frac{V}{R}$$

$$V_C = I X_C$$

$$\Rightarrow V \cdot X_C / R$$

$$V_C = V \cdot Q$$
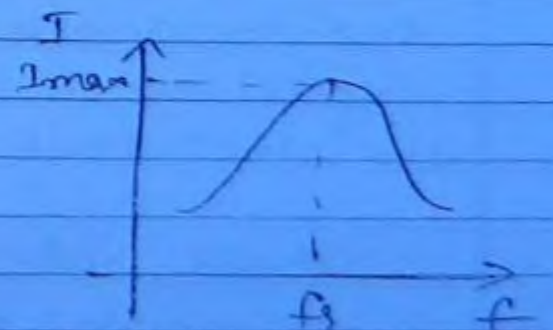
$$V_C \propto Q \quad V = \text{constant}$$




Theoretical Q Meter

A voltmeter is connected across the variable capacitor. This meter is calibrated to measure the quality ^{factor} of the coil under test.

Practical Q Meter →

(152)

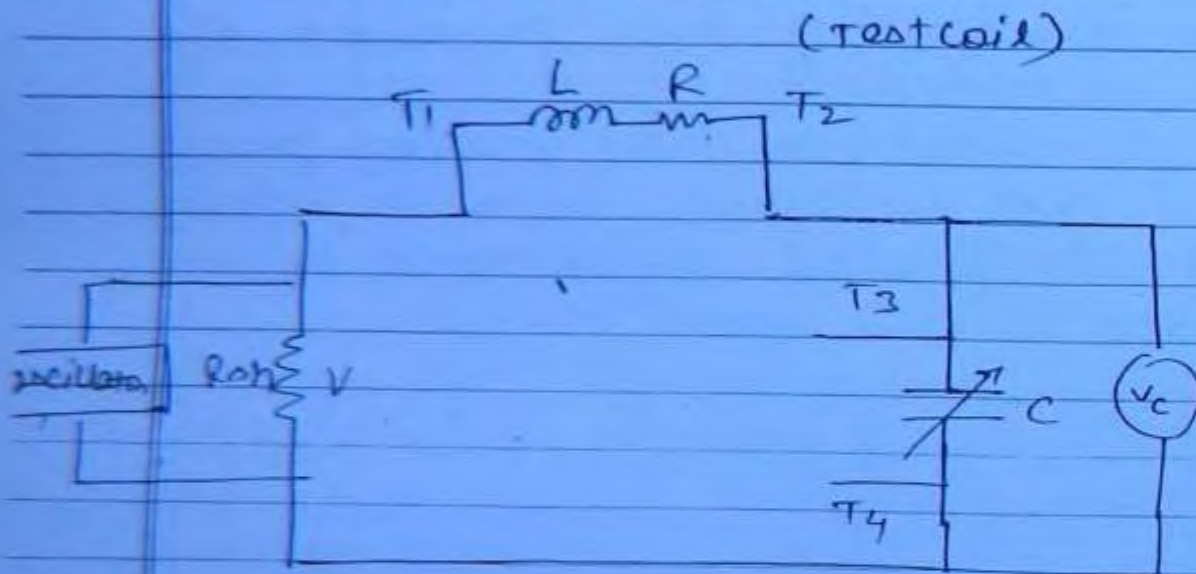

Applications →

- (1) Measurement of Q of the coil → The test coil is connected between terminals T1 & T2 & circuit is resonated by varying the capacitor C. The voltmeter across the capacitor is calibrated to measure Q of the test coil.

$$\text{True value of } Q(Q_T) = \frac{\omega L}{R}$$

$$\text{Measured of } Q = Q_m = \frac{\omega L}{(R + R_{sh})}$$

$$= \frac{\omega L}{R (1 + R_{sh}/R)}$$

(53)

$$Q_m = \frac{Q_T}{(1 + R_{sh}/R)}$$

$$Q_T = Q_m \left[1 + \frac{R_{sh}}{R} \right]$$

R_{sh} is to be low, so that $Q_T = Q_m$
 R_{sh} is in the range of m.Ω.

(ii) Measurement of unknown Capacitance →

The test capacitance is connected between T_3 & T_4 and the circuit is resonated to a frequency f_1

$C \rightarrow C_1$

$$f_1 = \frac{1}{2\pi \sqrt{L(C_1 + C_T)}}$$

Remove C_T b/w T_3 & T_4 change the capacitor to the f_2 value C_2 to get the same value of f_1 . From the known values of C_1 & C_2 C_T is measured.


$C \rightarrow C_2$

$$f_2 = \frac{1}{2\pi \sqrt{LC_2}} \Rightarrow f_1 = \frac{1}{2\pi \sqrt{L(C_1 + C_T)}}$$

$$C_T + C_1 = C_2$$

$$\boxed{C_T = C_2 - C_1}$$

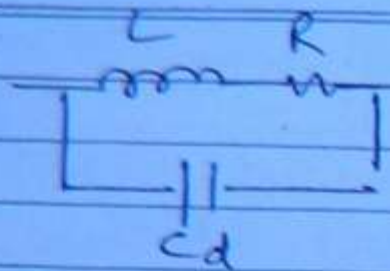(ii) Measurement of distributed or self capacitance → (C_D).



$$C \rightarrow C_2$$

$$f_2 = \frac{1}{2\pi \sqrt{L(C_2 + C_d)}} = n f_1$$

$$C \rightarrow C_1$$

(154)

$$\frac{1}{2\pi \sqrt{L(C_2 + C_d)}} = \frac{n}{2\pi \sqrt{L(C_1 + C_d)}}$$

$$f_1 = \frac{1}{2\pi \sqrt{L(C + C_d)}}$$

$$C_d = \frac{C_1 - n^2 C_2}{(n^2 - 1)}$$

$$\text{for } n=2, f_2 = 2f_1$$

$$C_d = \frac{C_1 - 4C_2}{3}$$

Q In a Q meter an inductor is tuned to 2 MHz, 450 pF and 4 MHz with 90 pF. Then the distributed capacitance of the inductor is


- a) 45
b) 90
c) 30
d) 360.

Ans

$$\begin{aligned} f_2 &= 2f_1 \\ &\Rightarrow 2(2) \\ &\Rightarrow 4 \end{aligned}$$

$$C_d = \frac{450 - 4 \times 90}{3} \Rightarrow 30 \text{ pF}$$

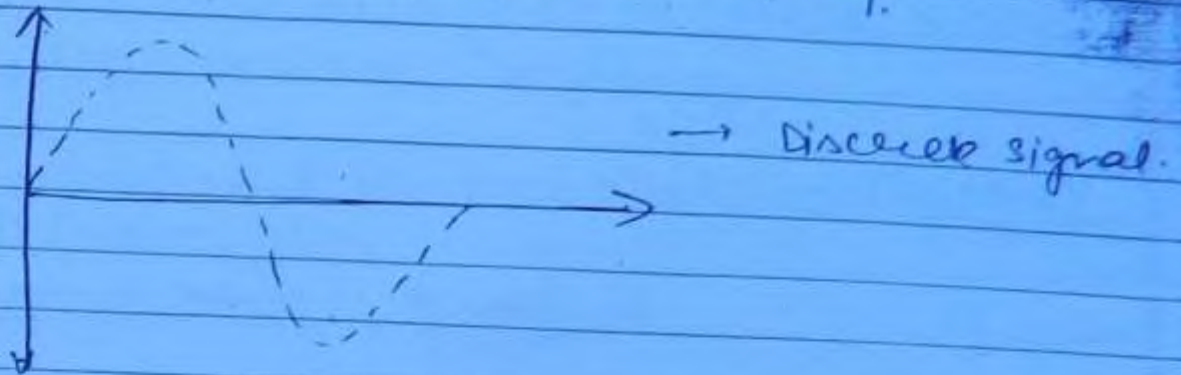
CRO \rightarrow Cathode Ray Oscilloscope.



Advantages.

- (i) X-Y plotter (wave form)
- (ii) V_{pp} , V_m , V_{RMS}
- (iii) f , ϕ , T
- (iv) Compare the signal.
- (v) Storage of data.
- (vi) Scale is adjustable.
- (vii) High Resolution
- (viii) High Accuracy
- (ix) High Sensitivity
- (x) High Speed
- (xi) No external effects.
- (xii) Linear Device.

Screen of CRO :-

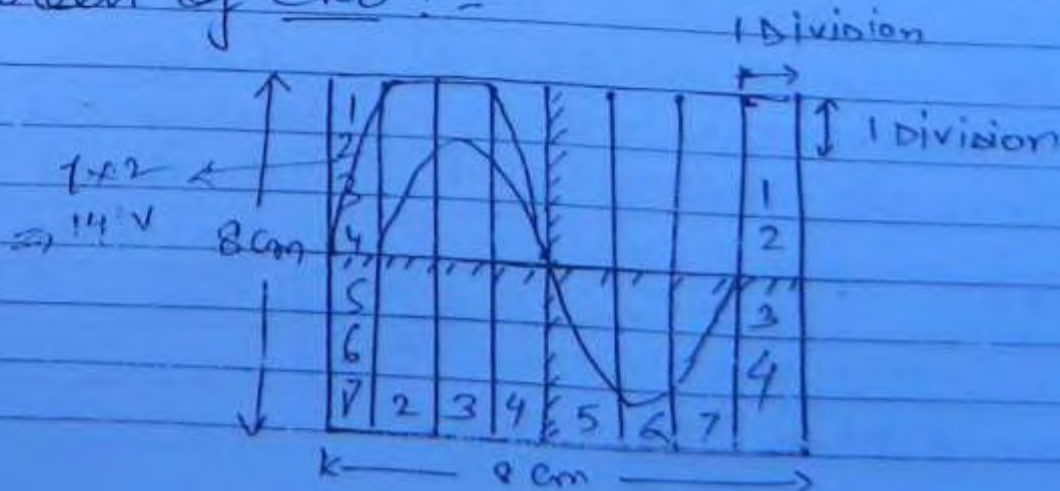

Measurement of Time period (T) :-

$$T = (X\text{-scale}) \times (\text{No of Division's occupied by signal over one cycle})$$

X-scale or Line base or Time base \rightarrow sec or msec/division or sec or msec/cm.

(156)

Ex: X scale :- 2 msec/division

$$X = 7 \times 2 = 14 \text{ msec}$$

$$f = \frac{1}{T} \text{ Hz}$$

No of cycles of waveform
or
Signal visible on screen = $\frac{\text{Total time period of screen}}{\text{Time period of waveform}}$

Measurement of V_{pp} :-

$$V_{pp} = (Y\text{-scale}) \times [\text{No of division occupied by signal from +ve peak to -ve peak}]$$

Y scale \rightarrow volt division or cm/division.
Volts/cm

$$Y\text{ scale} :- 2 \text{ V/cm}$$

$$V_{pp} = 4 \times 2 = 8 \text{ V}$$

$$\text{Peak} :- V_m = \frac{V_{pp}}{2} = \frac{8}{2} \rightarrow 4 \text{ V}$$

$$\text{Sinusoidal} :- V_{RMS} = \frac{V_m}{\sqrt{2}}$$

If I/P signal applied having peak to peak more than max^m allowable peak to peak signal then signal will be clipped on the screen.

Q14

(52)

X scale = 0.5 mV/cm - Time period of screen

Y scale = 100 mV/cm.

Time period of signal = $\frac{1}{200}$ Hz = 5 msec.

$$n = \frac{5}{5} \Rightarrow 1 \text{ cycle.}$$

$\rightarrow 8 \times 100 \Rightarrow 800 \text{ mV (max on screen)}$

Signal : - $V_{RMS} = 300 \text{ mV}$

$$V_m = \sqrt{2} V_{RMS} \Rightarrow 2$$

$$V_{pp} = 2 \sqrt{2} \times 300$$

$$\Rightarrow 848 \text{ mV} > 800 \text{ mV}$$

Calibration of CRO \rightarrow

CRO is calibrated by applying a square wave pulse signal having a frequency of 1 kHz and an amplitude of 1 volt.

Bandwidth of CRO - The max^m frequency of the signal that can be visible on the screen without any distortion is called bandwidth. Bandwidth and rise-time of the signal are related as

$$[Bw \times t_r = 0.35]$$



Bw = Bandwidth in Hz

t_r = Rise time in sec.

Input Impedance of CRO →

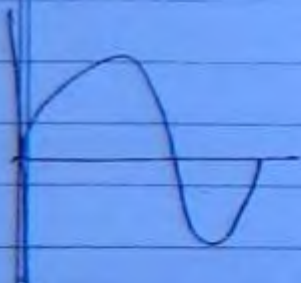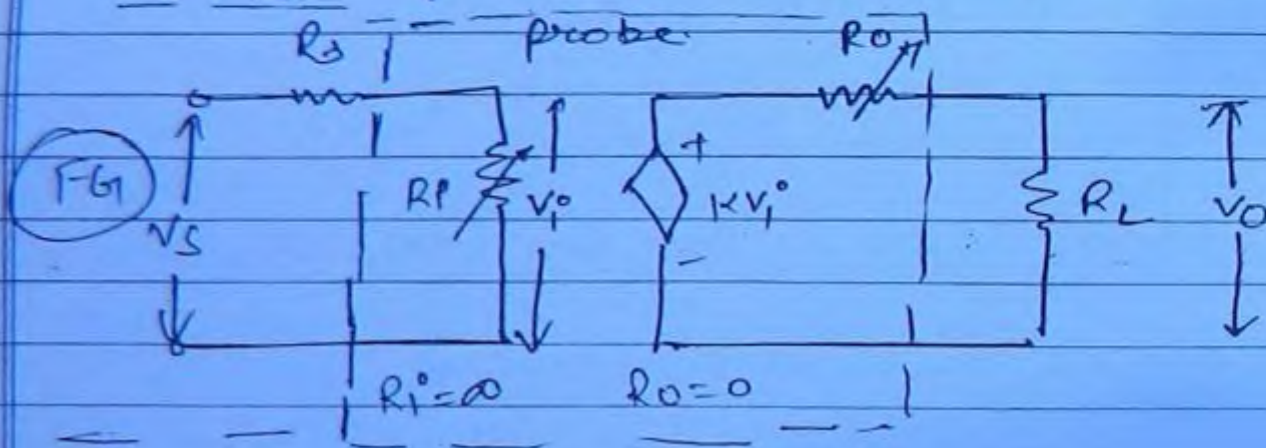(158)

The input resistance of CRO should be very high of order of $M\Omega$ and the input capacitance should be low of the order of pF so that the input voltage signal will not be attenuated.




$$V_i^* = V_s$$

$$V_o = K V_i^*$$


$$V_o = K V_s$$

$$\text{If } K = 1 \\ V_o = V_s$$

Transfer + Resistor = Transistor ✓

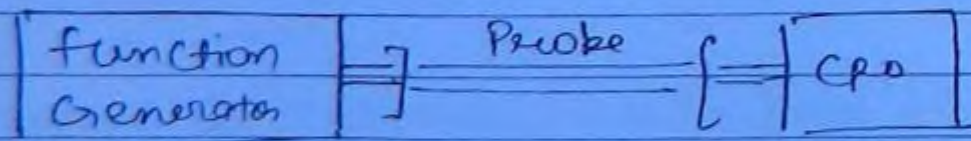

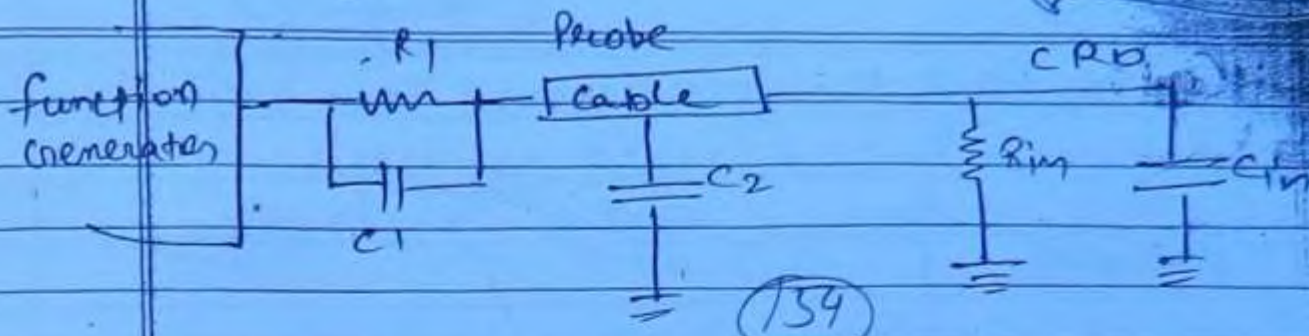10X or high impedance probe
Electrical Equivalent ckt.



$$\frac{R_1 + R_{in}}{R_{in}} = 10$$


Independent of frequency
 $R_1 C_1 = R_{in} C_{in}$

$$R_1 = 9 R_{in}$$


R_1, C_1 → Resistance & Capacitance of probe

R_{in}, C_{in} → Resistance & Capacitance of CRO.

C_2 → Capacitance to ground $\ll C_{in}$

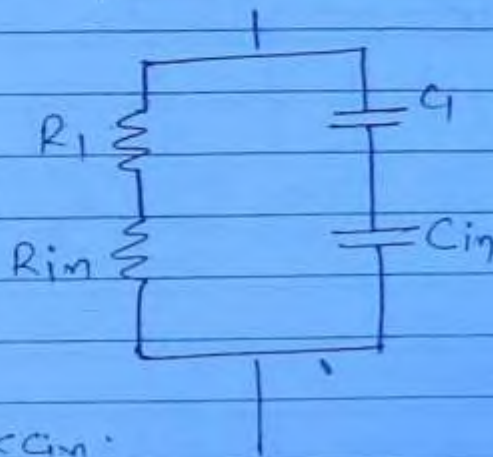

Pg 49
 Q3

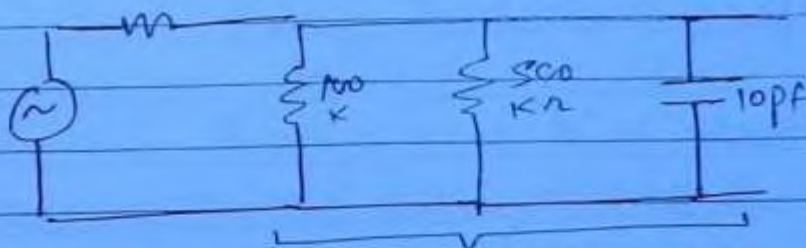

$$X_C = \frac{1}{2\pi fC}$$

$$\Rightarrow \frac{1}{2\pi \times 100 \times 10^3 \times 10^{-12}}$$

$$Z = 100 \parallel 500 \parallel (-j159 \text{ K})$$



$$X_C = j159 \Omega$$

$$Z = \frac{500 \times 100}{600} \parallel j159$$

$$\frac{500 \times 100}{600} + \frac{1}{j159}$$


$$\frac{500 \times 100}{600(j159) + 500 \times 100}$$
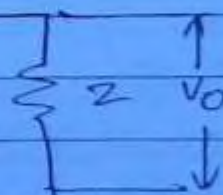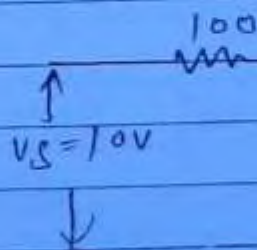
$$\frac{500 \times 100}{(500 - j159)(1 + j159)}$$



$$\Rightarrow \frac{V_S \cdot Z}{100 + Z}$$

Cathode Ray Tube: -

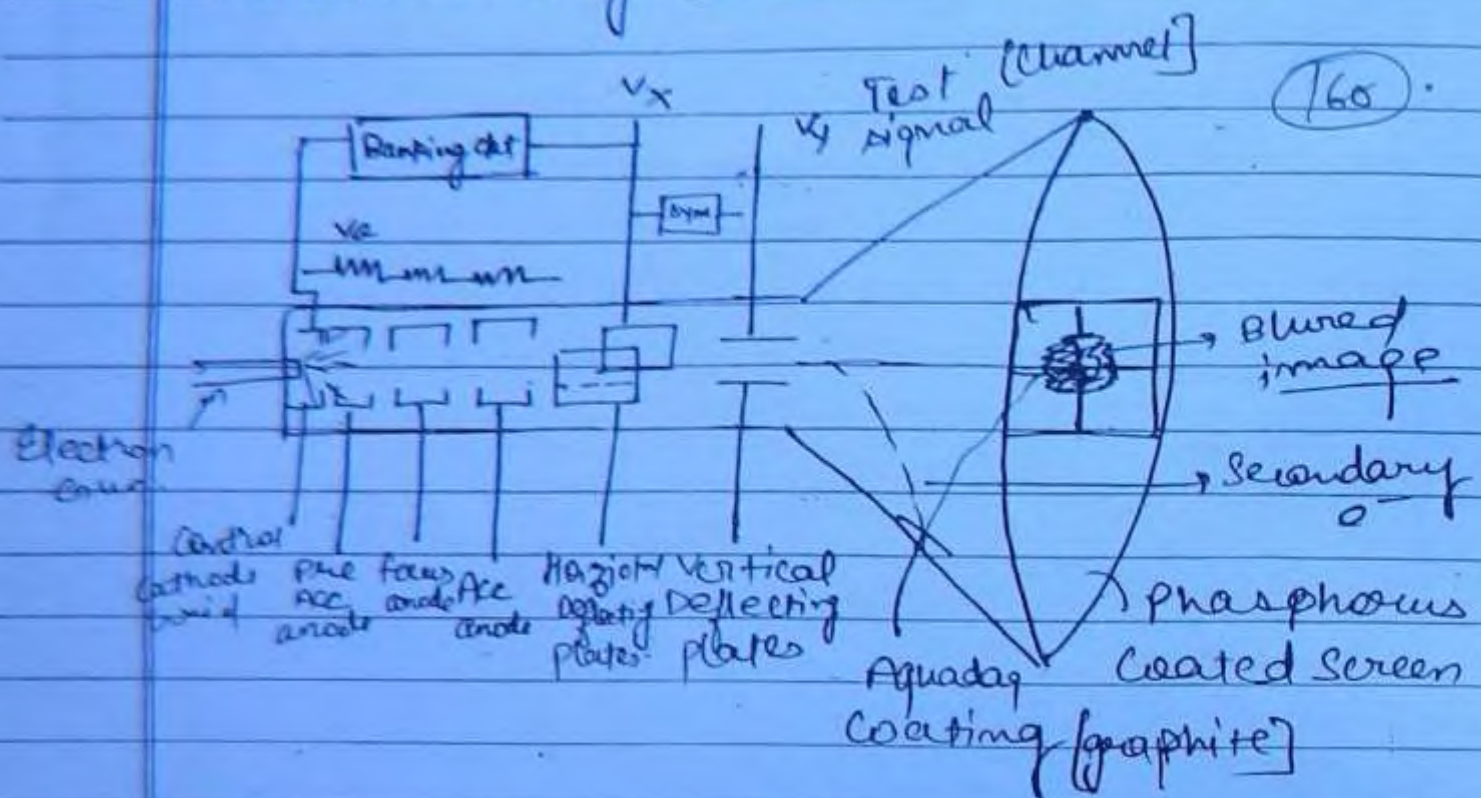

CRO or CRT working on the principle of Thermionic emission. i.e. emission of electron's from a heated surface. (electron gun)

Control Cathode Grid is applied with negative potential which is used to control no. of electron's entering into other region of CRT.

$$KE = PE$$

$$\frac{1}{2}mv^2 = qVa$$

$$v = \sqrt{\frac{2qVa}{m}}$$


$$v \propto \sqrt{Va}$$

v = velocity of electron
 Va = anode voltage.

The pre accelerating and accelerating potentials are used for controlling the speed of the electron shown above.

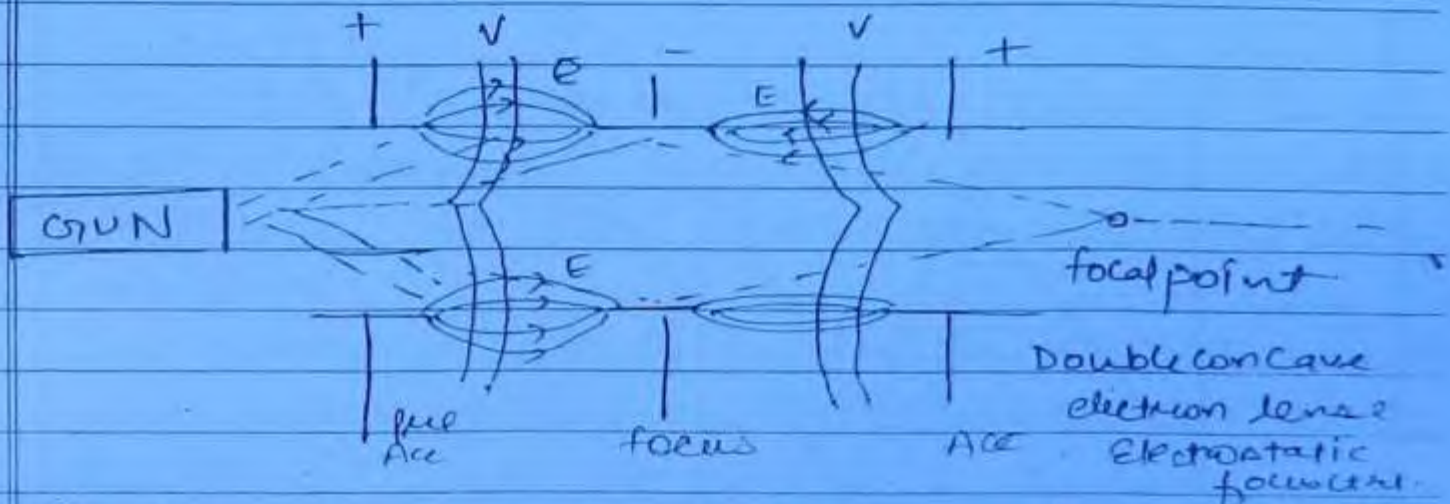(161)

In case of high frequency CRO post accelerating anode is used for controlling the brightness of electron beam on the screen for the frequency above 10 MHz.





Electrostatic focus control is used in laboratory CRO's.

Electromagnetic focus control is used in television picture tube.

Both electrostatic & magnetic focusing's are used in case of computer CRO's.

Electrostatic focusing working on a principle of double Concave electron lens adjustment for controlling of focal point.

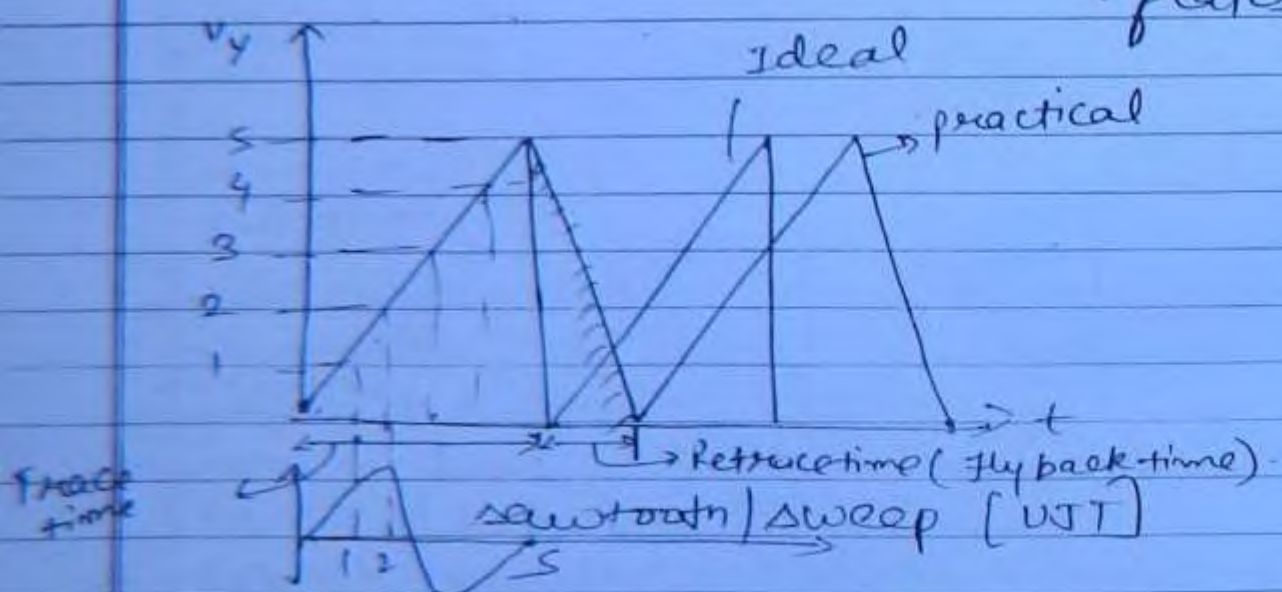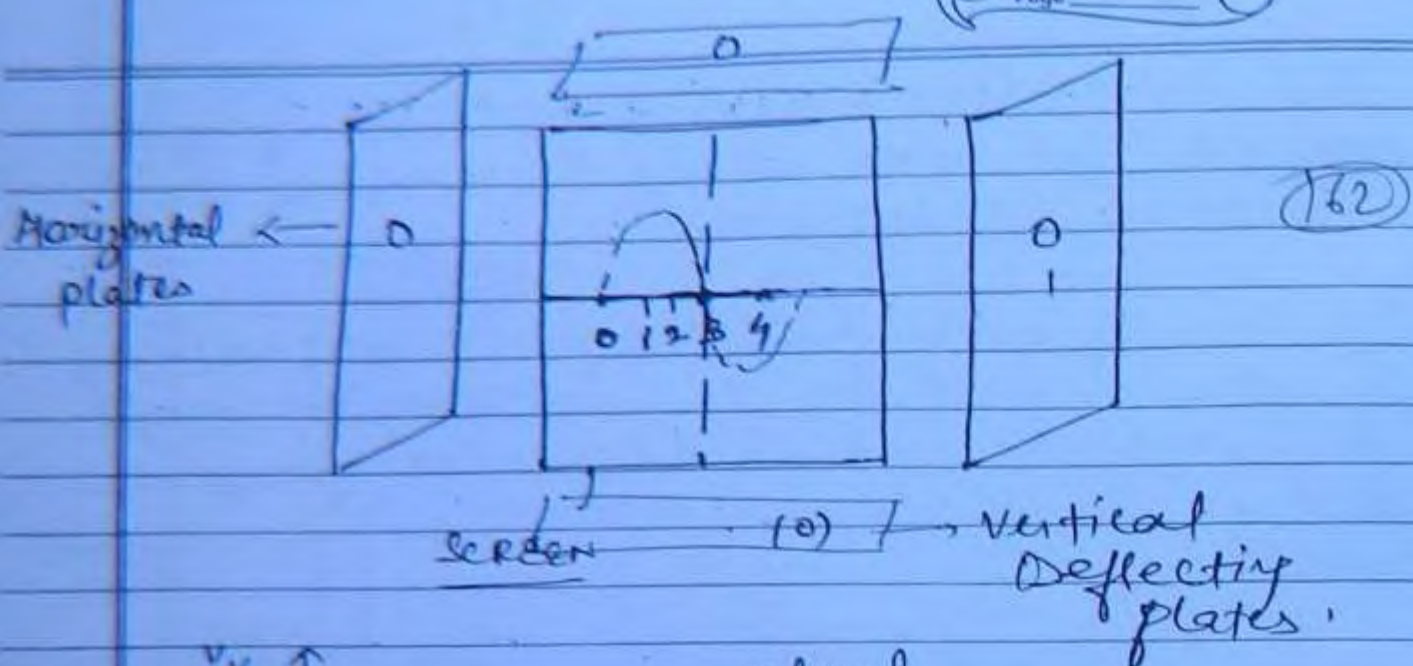Astigmatism is a method used for fine focus control by applying a small dc potential and by removing voltage sources of horizontal and vertical deflecting plate potentials.



The horizontal deflecting plates are in vertical position and is applied with sawtooth or sweep voltage which is produced by the V/T relaxation oscillator.

During Retrace period of this waveform blanking ckt is initiated which gives a command to the Cathode grid to produce high negative potential so that electrons are blanked out entering inside of CRT.

The time period of sawtooth waveform is adjusted by using synchronizing ckt

So that the time period of external signal and horizontal signal are to be Synchronizing.

(163)


Vertical deflecting plates are kept in horizontal position. A test signal is applied to the vertical deflecting plates so that the electron beam path is in synchronism with the test signal and this is achieved by controlling synchronizing circuit.

Aquadag Coating \rightarrow Aquadag coated with graphite is used for collection of secondary electron's so that keep the CRT electrically neutral.

The screen is coated with phosphorus depending on phosphorus coating the colour of the beam on the CRO is changed.

- \rightarrow P11 \rightarrow General purpose CRO
- \rightarrow P4 \rightarrow Black & white CRO
- \rightarrow P6 \rightarrow Colour display
- \rightarrow P15 \rightarrow Sampling CRO (High freq CRO)
- \rightarrow P31 \rightarrow Storage CRO.

Deflection Sensitivity \rightarrow

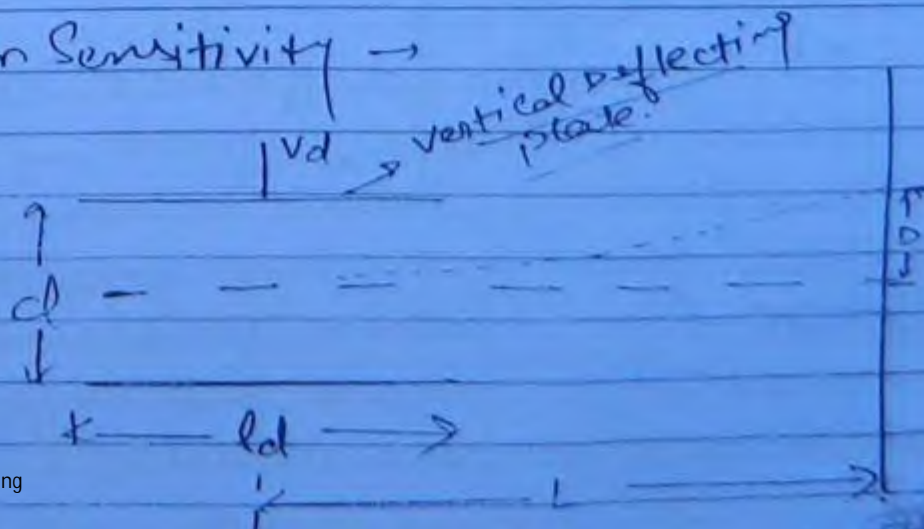

$$D = \frac{L l d V_d}{2 d v_a}$$

(T64)

Deflection sensitivity $S = \frac{D}{V_d} = \frac{L l d}{2 d v_a} \text{ mm/v}$

Deflection factor $G = 1/S$.

D = Deflection height on the screen.

d = distance b/w plates.

l = length of plates.

L = distance b/w center of plate to screen.

v_a = Anode voltage.

V_d = Deflecting plate voltage.

Lissajous pattern \rightarrow If both horizontal & vertical deflecting plates are applied with sinusoidal signals the waveform pattern appearing on the screen is called Lissajous pattern.

Application's \rightarrow

- It is used for finding
 - (i) phase angle difference b/w horizontal, vertical voltages applied.
 - (ii) the frequency ratio b/w the horizontal & vertical. ~~from a known frequency~~
 From the known frequency of one of the signal other signal frequency can be calculated by using Lissajous pattern.

Note:-

At any point of time the electron beam on the screen is the vector sum of the voltages applied to the horizontal & vertical deflection plates.

The vector sum consisting of both magnitude and phase angle.

(65)

$$V_x = V_m \sin \omega_x t$$


$$V_y = V_m \sin (\omega_y t + \phi)$$

Case I:-

Both V_x & V_y have same frequency ($\omega_x = \omega_y = \omega$) but phase difference (ϕ):- $V_x = V_m \sin \omega t$, $V_y = V_m \sin (\omega t + \phi)$

a) $\phi = 0^\circ$ ($V_x = V_m \sin \omega t$, $V_y = V_m \sin \omega t$).

Point	V_x	V_y	$\sqrt{V_x^2 + V_y^2}$	$\theta = \tan^{-1}(V_y/V_x)$
O	0	0	0	0
A	V_m	$V_m(45^\circ)$	$\sqrt{2} V_m [5m]$	$45^\circ [65^\circ]$
B	0	0	0	0
C	$-V_m$	$-V_m(135^\circ)$	$\sqrt{2} V_m [5m]$	$225^\circ [184.63^\circ]$
D	0	0	0	0




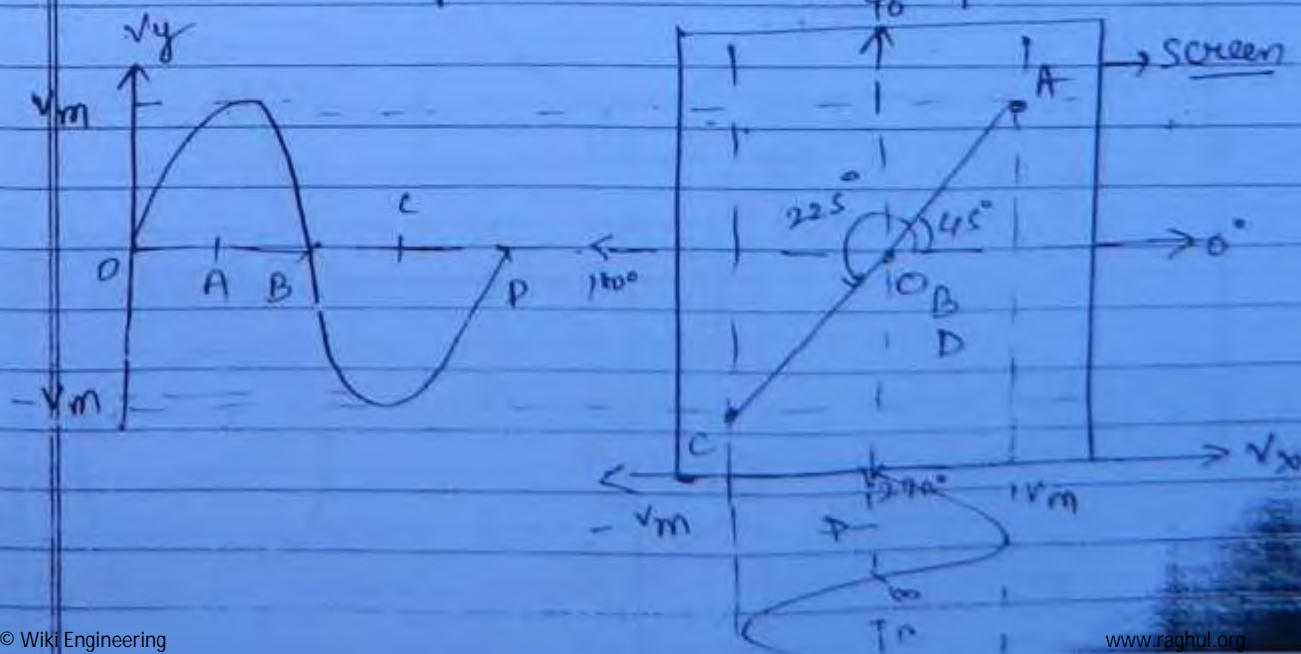


b) $\phi = 90^\circ$

(166)

$|v_x| = |v_y|$


point	v_x	v_y	$\sqrt{v_x^2 + v_y^2}$	$\theta = \tan^{-1}(v_y/v_x)$
O	0	V_m	V_m	90°
A	V_m	0	V_m	0°
B	0	$-V_m$	V_m	270°
C	$-V_m$	0	V_m	180°
D	0	V_m	V_m	90°

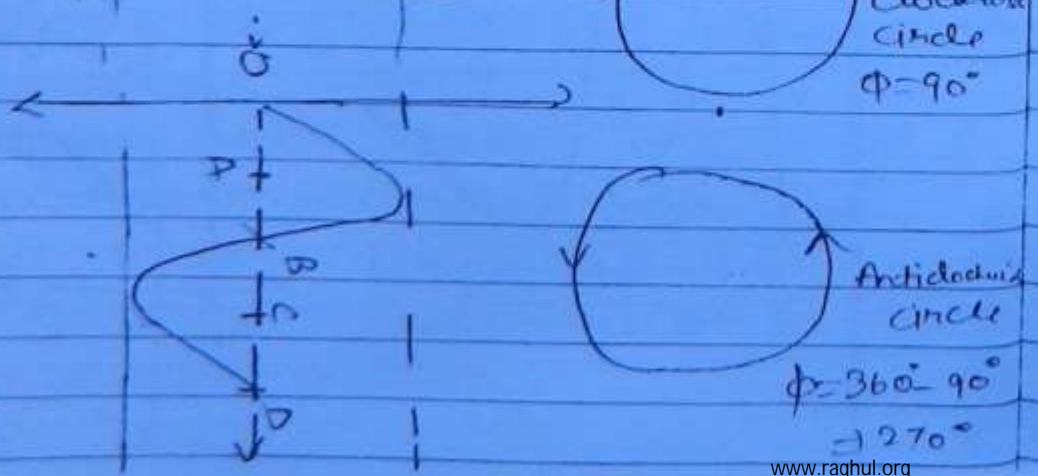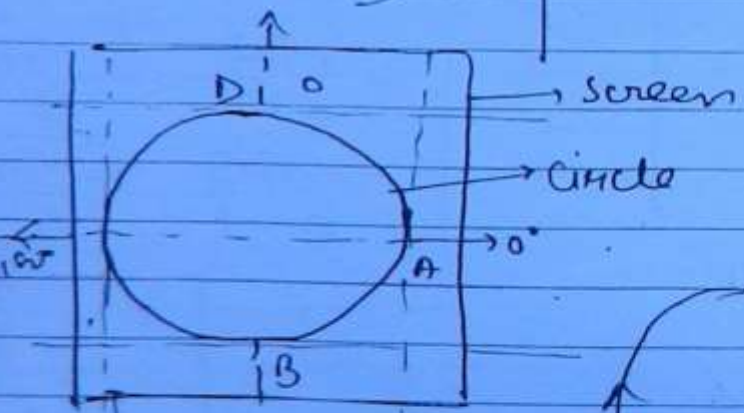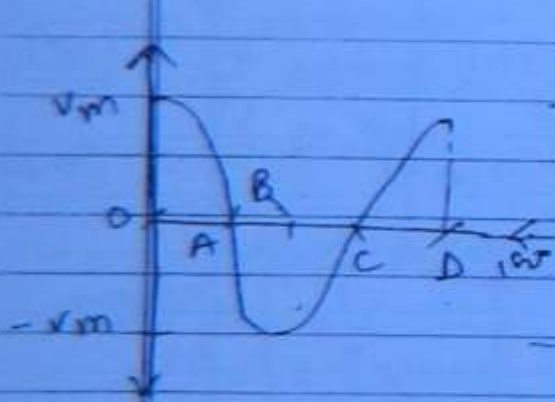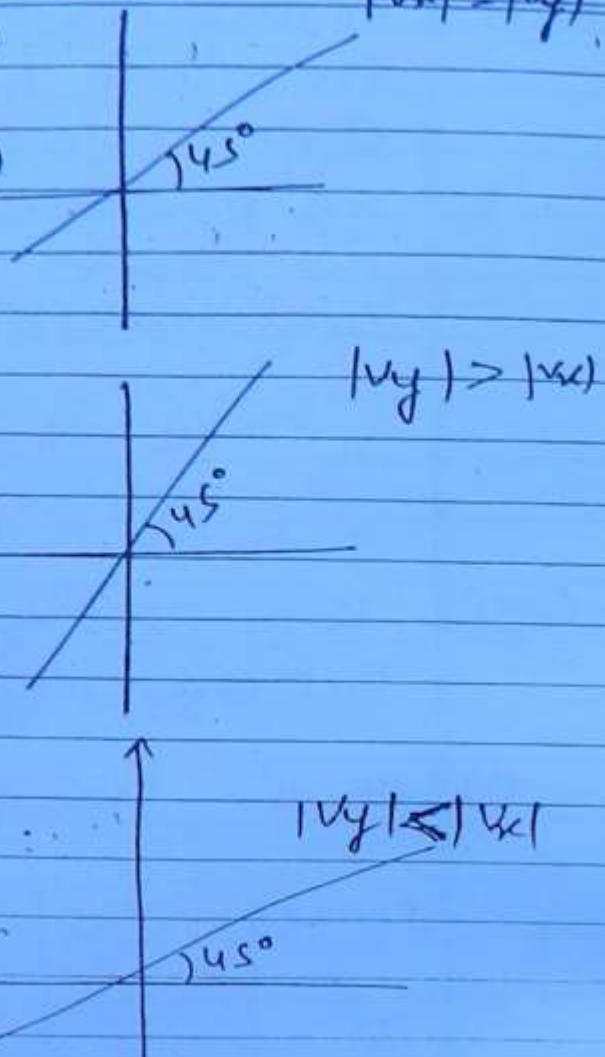

LP for different $\phi \rightarrow$

$$\phi = 0^\circ \text{ or } 360^\circ$$


(167)

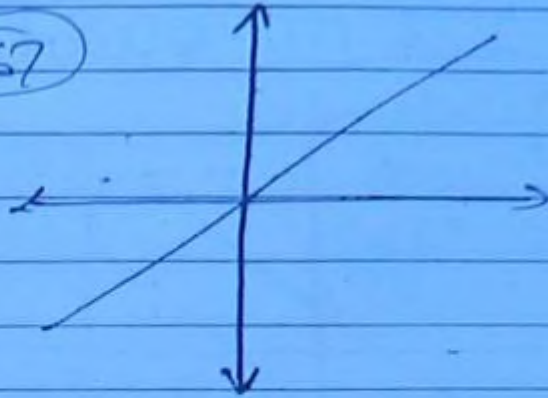


$$0 < \phi < 90^\circ$$

or

$$270^\circ < \phi < 360^\circ$$

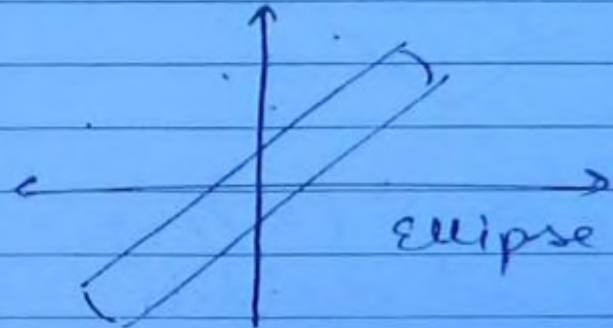

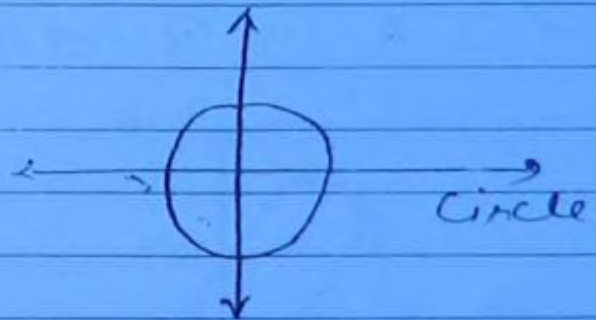
$$\phi = 90^\circ \text{ or } 270^\circ$$



$$90^\circ < \phi < 180^\circ$$

or

$$180^\circ < \phi < 270^\circ$$

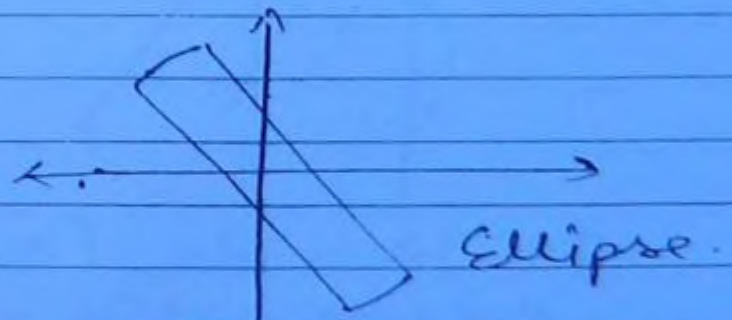


$$\phi = 180^\circ$$



Calculation of ϕ from LP \rightarrow

① LP in I & III Quadrant's \rightarrow


(168)

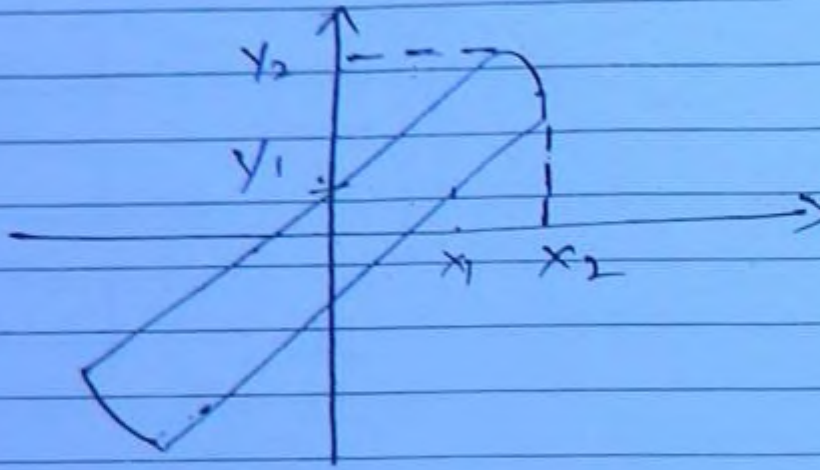

$$\phi = \sin^{-1}(x_1/x_2) \quad \text{or} \quad \sin^{-1}(y_1/y_2)$$

$$\text{Second possibility} = (360 - \phi) \quad (360 - \phi)$$

② LP in II & IV Quadrant's \rightarrow

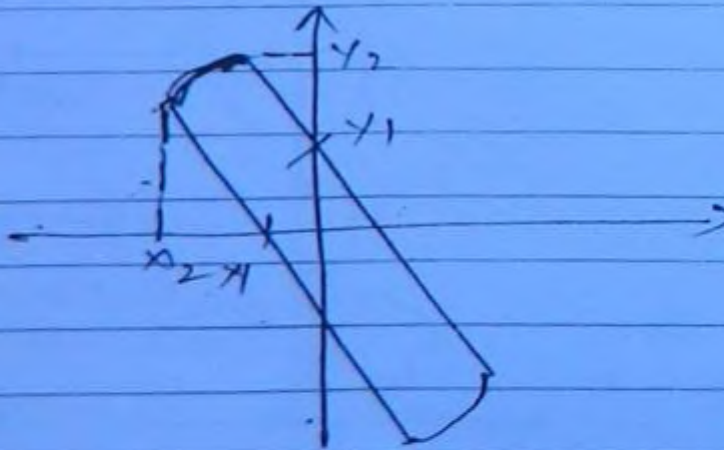


$$\phi = 180 - \sin^{-1}(x_1/x_2) \quad (\text{or})$$

$$\phi = 180 - \sin^{-1}(y_1/y_2)$$

$$\text{Second possibility} = (180 - \phi) \quad (360 - \phi)$$

Q For the following Lissajous pattern find ϕ

(i)

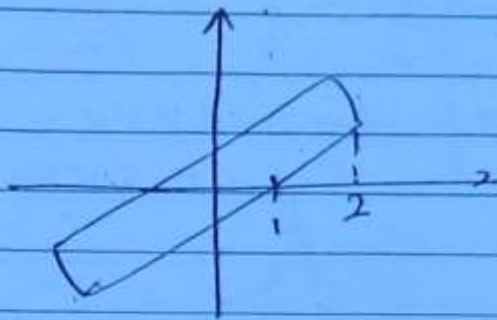


(169)

$$\phi = \sin^{-1} \left(\frac{1}{2} \right) = 30^\circ$$

or

$$360^\circ - 30^\circ = 330^\circ$$

(ii)

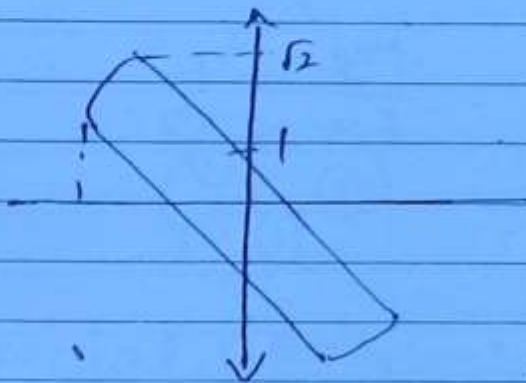


$$\phi = 180^\circ - \sin^{-1} \left(\frac{1}{\sqrt{2}} \right)$$

$$\Rightarrow 135^\circ \text{ or}$$

$$\Rightarrow 360 - 135$$

$$\Rightarrow 225^\circ$$

(iii)

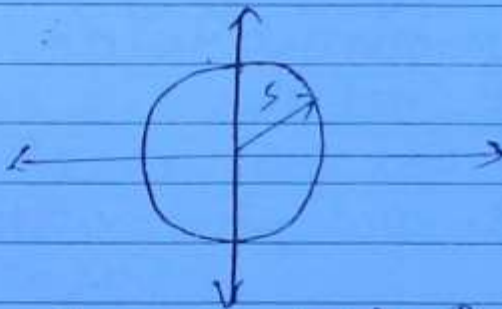


$$\phi = \sin^{-1} \left(\frac{5}{5} \right) = 90^\circ \text{ or } 270^\circ$$

(iv)

$$\phi = \sin^{-1} (0/0) = 0^\circ$$

or

$$360^\circ$$

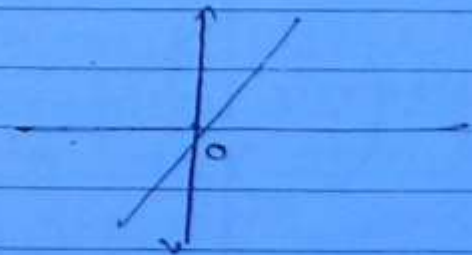


Case 2

V_x, V_y has different frequency.

$$V_x = V_m \sin \omega_x t = V_m \sin(2\pi f_x)t$$

$$V_y = V_m \sin \omega_y t = V_m \sin(2\pi f_y)t$$
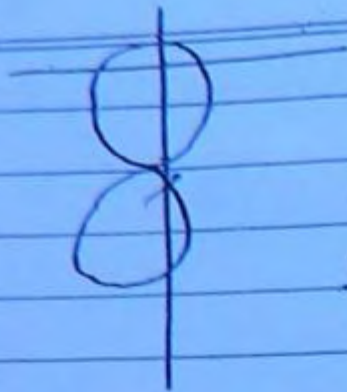
$$\frac{\omega_y}{\omega_x} = \frac{f_y}{f_x} = \frac{\text{No of horizontal Tangencies}}{\text{No of vertical Tangencies}}$$




$$\frac{f_y}{f_x} = \frac{2}{4} \Rightarrow \frac{1}{2}$$


(120)

$$1/ f_x = 1 \text{ kHz}$$


$$f_y = 0.5 \text{ kHz}$$

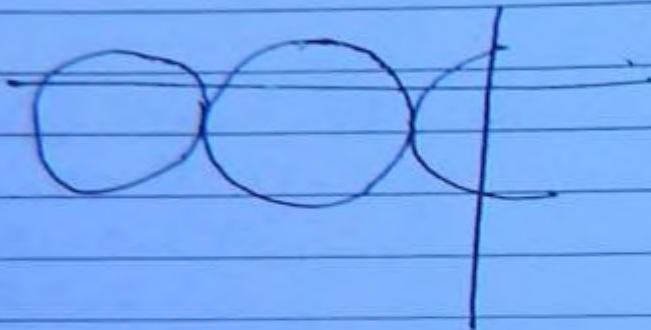


$$\frac{f_y}{f_x} = \frac{5}{2}$$

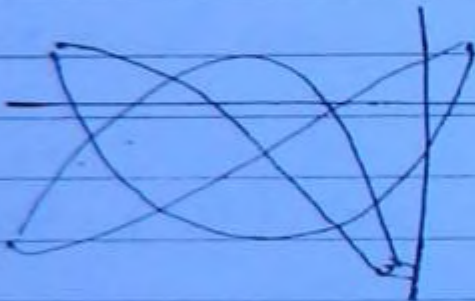
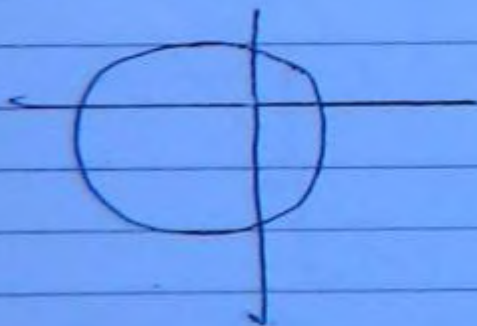
$$\frac{f_y}{f_x} = \frac{6}{4} \Rightarrow \frac{3}{2}$$



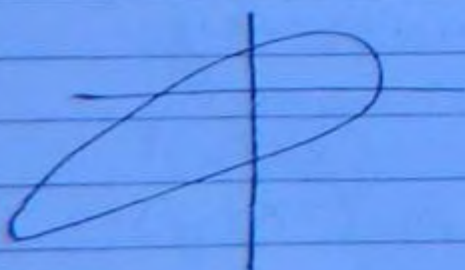
$$\frac{f_y}{f_x} = \frac{2}{2} \Rightarrow 1$$



$$\frac{f_y}{f_x} = \frac{2}{2} \Rightarrow 1$$


$$\frac{f_y}{f_x} \Rightarrow 1 \Rightarrow 1$$

Special cases \rightarrow

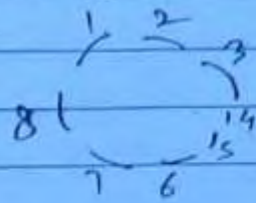


$$\frac{f_y}{f_x} \Rightarrow \frac{1}{8}$$

(171)

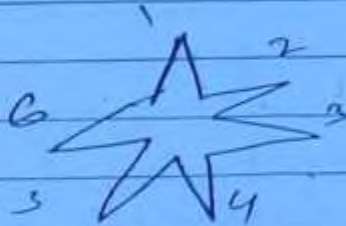
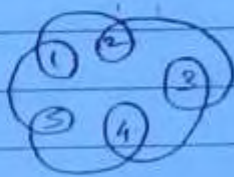
$$\frac{f_y}{f_x} \Rightarrow \frac{1}{6}$$




$$\frac{f_y}{f_x} = \frac{1}{5}$$


Special CRO's: -

- ① Dual trace CRO: - It contains two vertical deflecting plates and one e-gun. The selection switch is used for the selection of one of the input signals so that alternatively signals can be absorbed on the CRO screen.

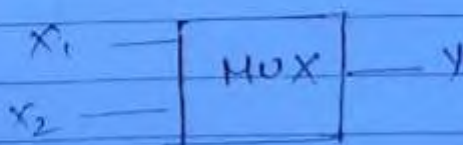A Dual trace CRO with multiplexer is used to display 2 input waveform simultaneously on the screen by keeping the time period of selection switch half the time period of saw tooth signal applied to horizontal plate.



S	Y
0	X ₁
1	X ₂

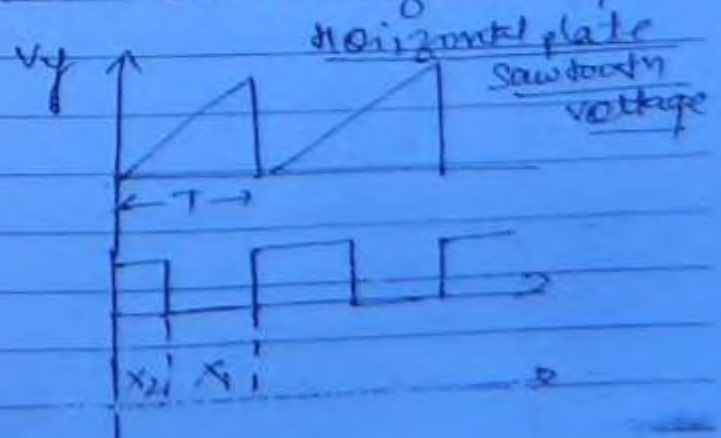

- ② Dual Beam CRO:- It contains two vertical deflecting plates and two electron gun's so that the two signal applied to the vertical plates can be simultaneously visible on the screen. Cost of the dual beam is higher.
- ③ High frequency CRO:- post accelerating anode is provided for rising the brightness of electron beam.
- It has low input capacitance
 - short persistent (P₁₅) phosphorus is used on the screen.
- ④ Storage CRO:- Memory storing element are provided for storage of signal's
- If the more storage data is required than it is converted into digital and stored in digital format.

01/2012

(172)

Digital Meters:- [Digital voltmeter]

Advantages:-

- ① No parallel error.
- ② Multiple application.
- ③ High speed
- ④ Store the data
- ⑤ Interfacing is possible
- ⑥ High Resolution.
- ⑦ High sensitivity
- ⑧ High accuracy
- ⑨ power consumption is low
- ⑩ Compact in size
- ⑪ No external effects.


(12)

Maintenance free.

(13)

Disadvantage

(i) External battery source is required.

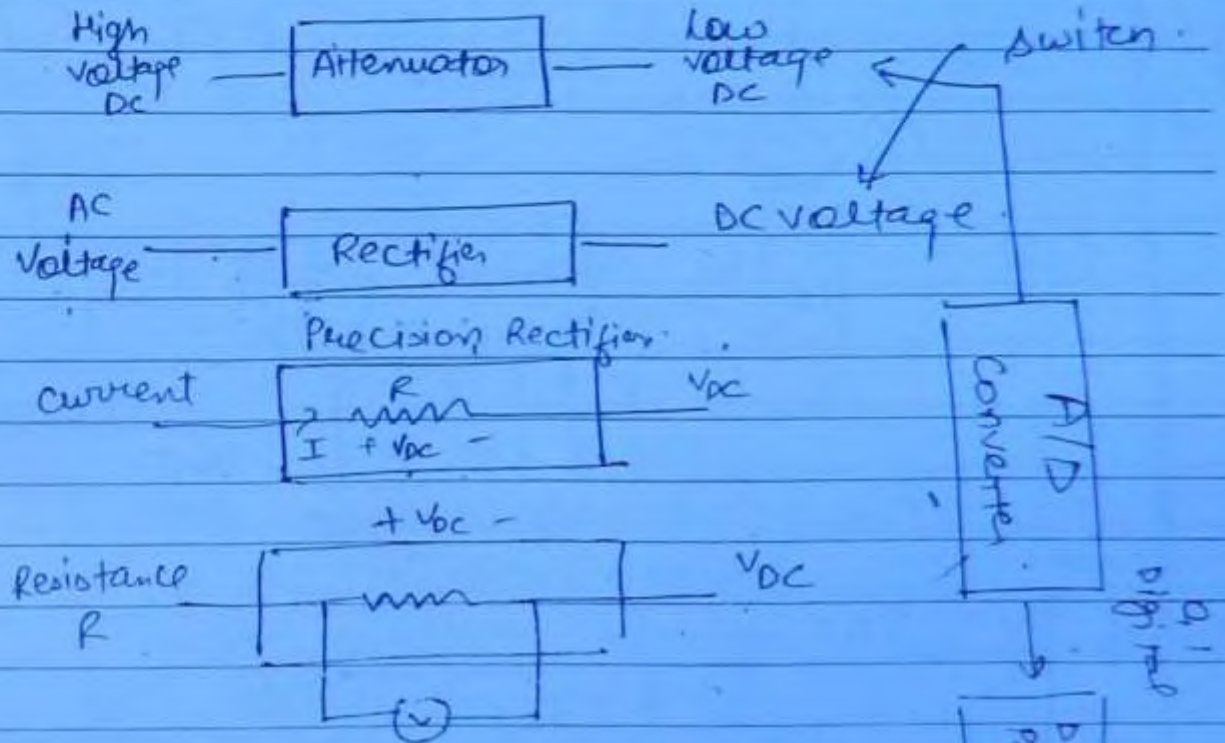

A/D converter

Conversion Time [cycles]

(1) flash	1
(2) S.A.R	n clocks
(3) Ramp or Counter	2^n clocks
(4) Dual Scope	$2^{(n+1)}$ clocks.

where, n = NO of digital output bits.



The basic measurable quantity of an A/D converter is dc voltage.

Dual slope A/D Converter :-

(174)

DC analog output

of type

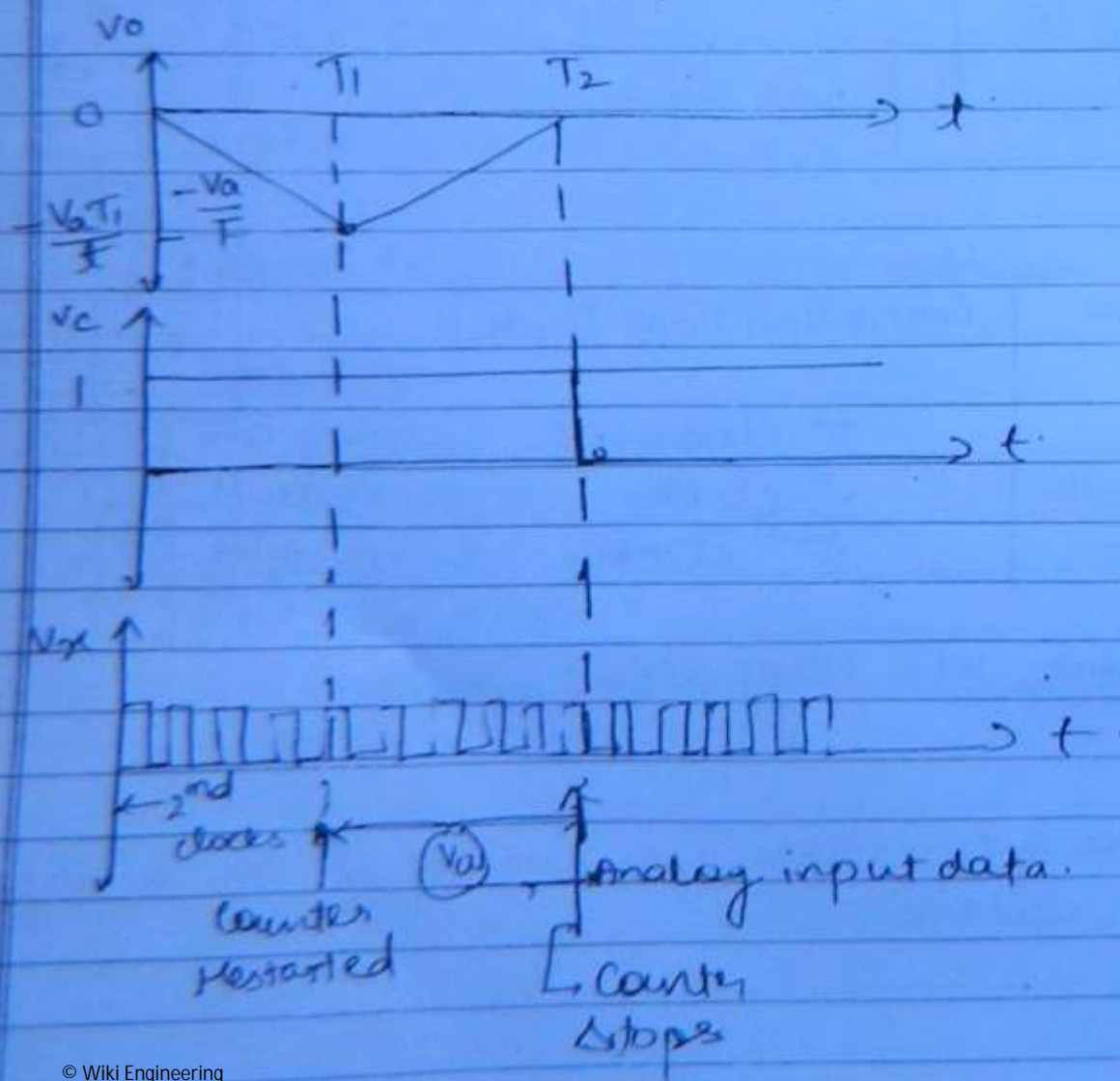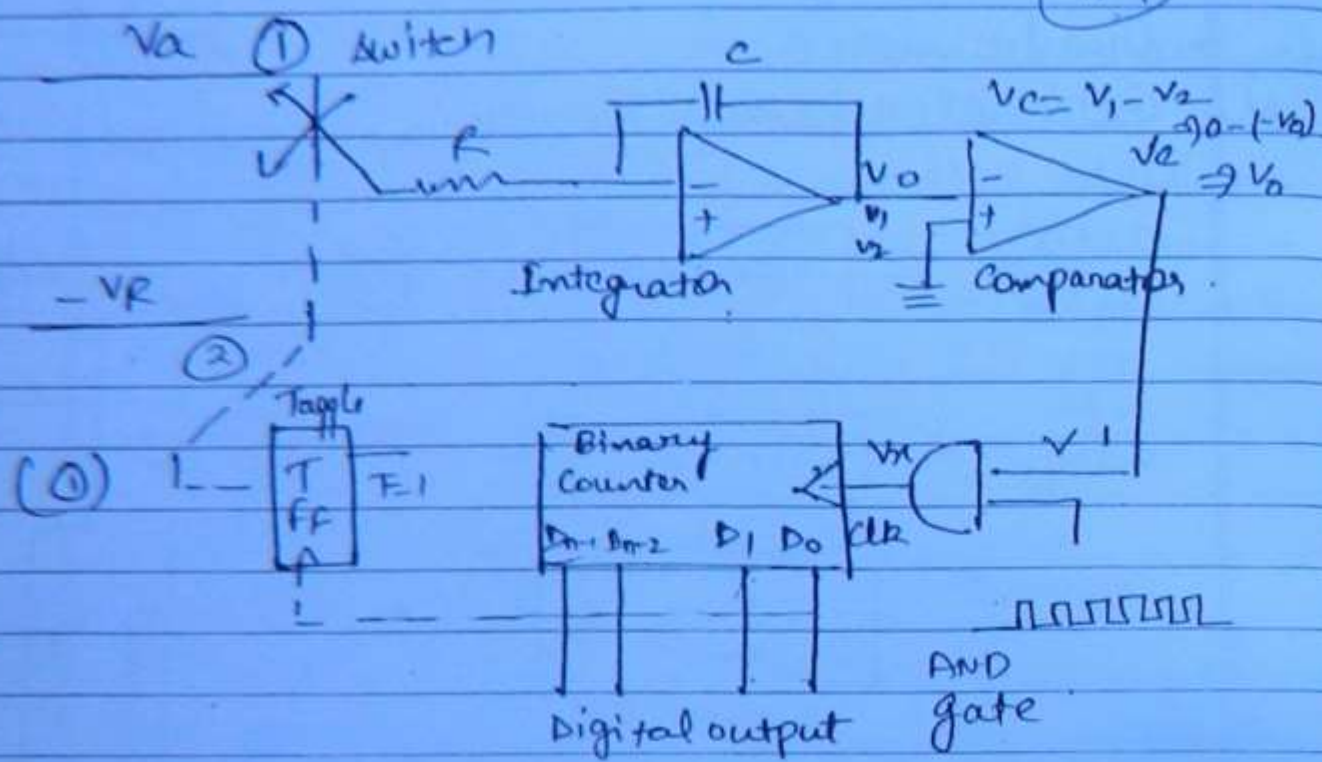

Switch is at posⁿ assume all output's of the device's integrator and gate binary counter T flip flop are initially zero. (175)

at time $t=0$; Switch is at ①

$$V_0 = -\frac{1}{RC} \int V_a \cdot dt$$

$$\Rightarrow -\frac{V_a \cdot t}{T} \quad T=RC$$

$$V_0 = m \cdot t, \quad m = \frac{V_0}{T}$$

$$V_0 = -V_R \Rightarrow V_C = +V_R = 1$$

$$V_C = 1 \Rightarrow V_X = \text{clocks.}$$

Binary counter incremented upto $t=T_1$.

At $t=T_1 = (2)^n$ clocks applied.

Counter resets to '0' value and T FF, output

$Q=1$, switch changes to ②.

$$\text{At } t=T_1, \quad \boxed{V_0 = -\frac{V_a T_1}{T}}$$

$0 < t < T_1 \rightarrow$ first integration or integration.

At $t=T_1$, switch at ②

$T_1 < t < T_2 \rightarrow$ second integration

$$V_0 = -\frac{V_a T_1}{T} + \left[-\frac{1}{T} \int_{T_1}^t (-V_R) dt \right] \text{ or Deintegration}$$

$$\boxed{V_0 = -\frac{V_a T_1}{T} + \frac{V_R}{T} (t - T_1)}$$

$$\boxed{\text{at } t=T_2, \quad V_0 = 0.}$$

$$\boxed{V_0 = -\frac{V_a T_1}{T} + \frac{V_R}{T} (T_2 - T_1)}$$


$$\boxed{V_R (T_2 - T_1) = V_a T_1}$$

$$(T_2 - T_1) = \frac{V_a T_1}{V_R} = \frac{V_a \cdot 2^n}{(2)^n} = V_a$$

$$\therefore \boxed{V_R = 2^n}$$

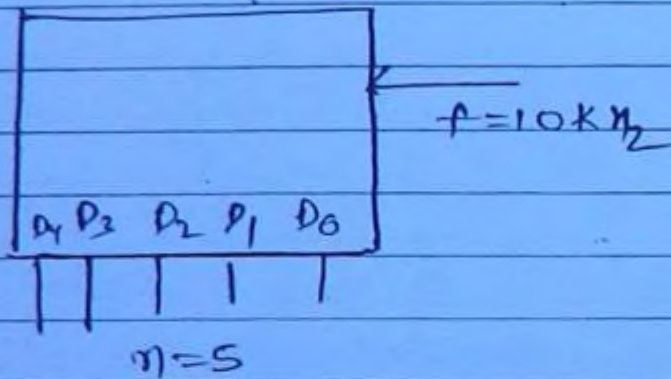(176)

Max^m Conversion Time $\rightarrow 2^n + 2^n = (2)^{n+1}$ clock's



$$T_1 = 2^n \times T_{clk}$$

$$\Rightarrow (2)^5$$

$$\Rightarrow 10 \times 10^{-3}$$

$$\boxed{T_1 = 3.2 \text{ ms}}$$

$$T_1 = 10/50 \text{ sec}$$

$$V_R = 2V$$

$$V_a = 1V$$

$$T_2 = ?$$

$$V_a T_1 = V_R (T_2 - T_1)$$

$$(1) \frac{10}{50} = 2 (T_2 - 10/50)$$

$$\frac{10}{50} = 2 (T_2 - 10/50)$$

$$\frac{1}{5} = T_2 - 10/50$$

$$T_2 = \frac{1}{5} + \frac{10}{50} = \frac{5 + 10}{50} = \frac{15}{50} = \frac{3}{10} \text{ sec}$$

Q20

$$V_R = 100 \text{ mV}$$

$$T_1 = 300 \text{ msec}$$


$$T_2 - T_1 = 370.2 \text{ msec}$$

$$V_a = ?$$

$$V_a = \frac{V_R(T_2 - T_1)}{T_1} \rightarrow 123.4 \text{ mV}$$

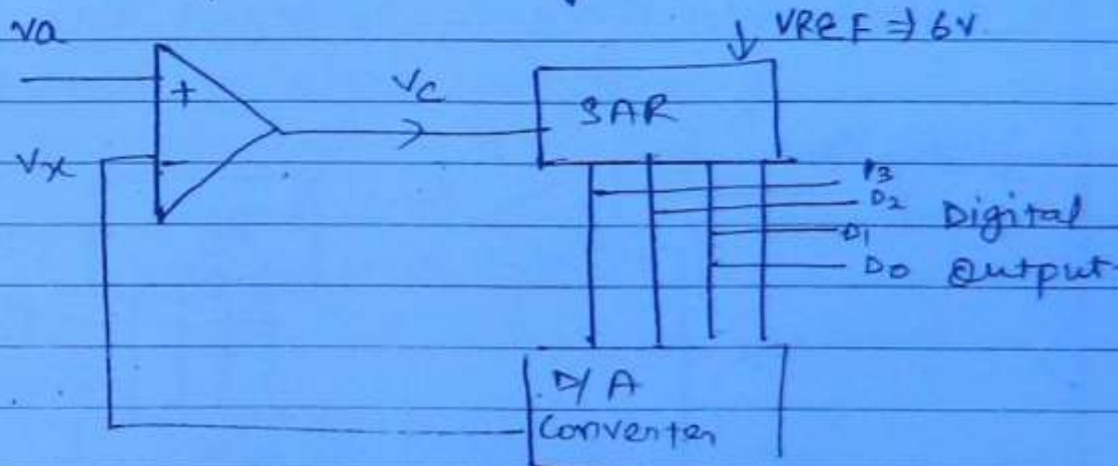
(177)

(Successive Approximation Register) SAR :-




$(2)^3$	$(2)^2$	$(2)^1$	$(2)^0$	
D ₃	D ₂	D ₁	D ₀	
1	0	0	0	
6	3	1.5	.75	$\Rightarrow 11.25 \text{ V}_a$
1	0	1	0	$\rightarrow 7.5 \text{ V}$

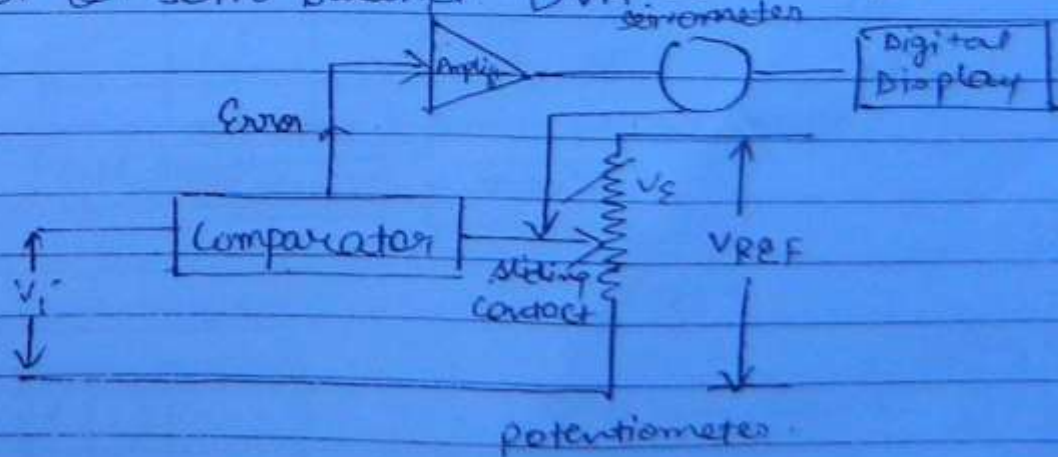
Comparator or Self balance type
Counter or Servo balance DVH:-
DUH:-





Voltage to frequency counter \rightarrow

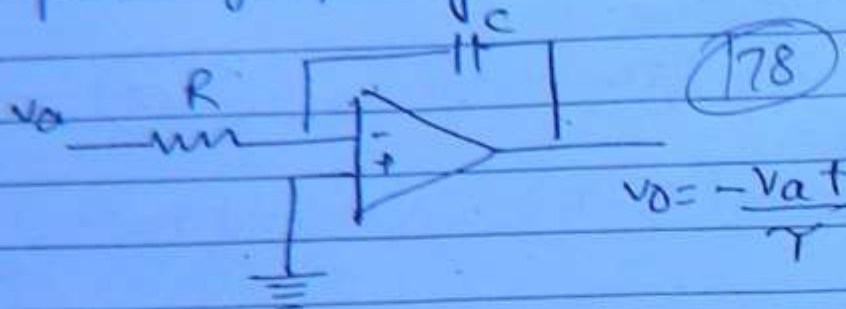

$$V_o = -\frac{V_a t}{T}$$

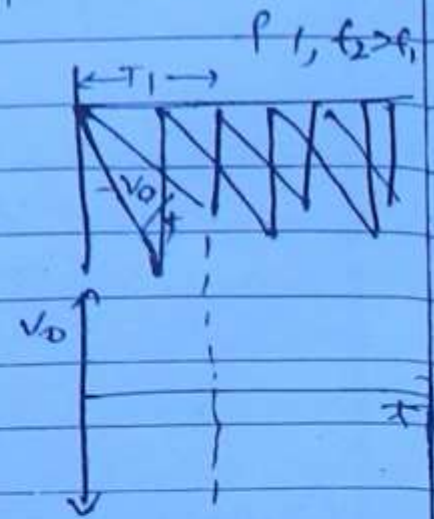

Ramp Type DVH :-

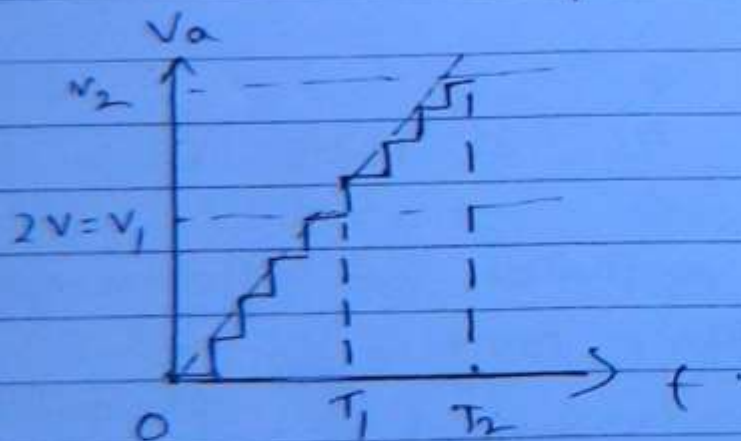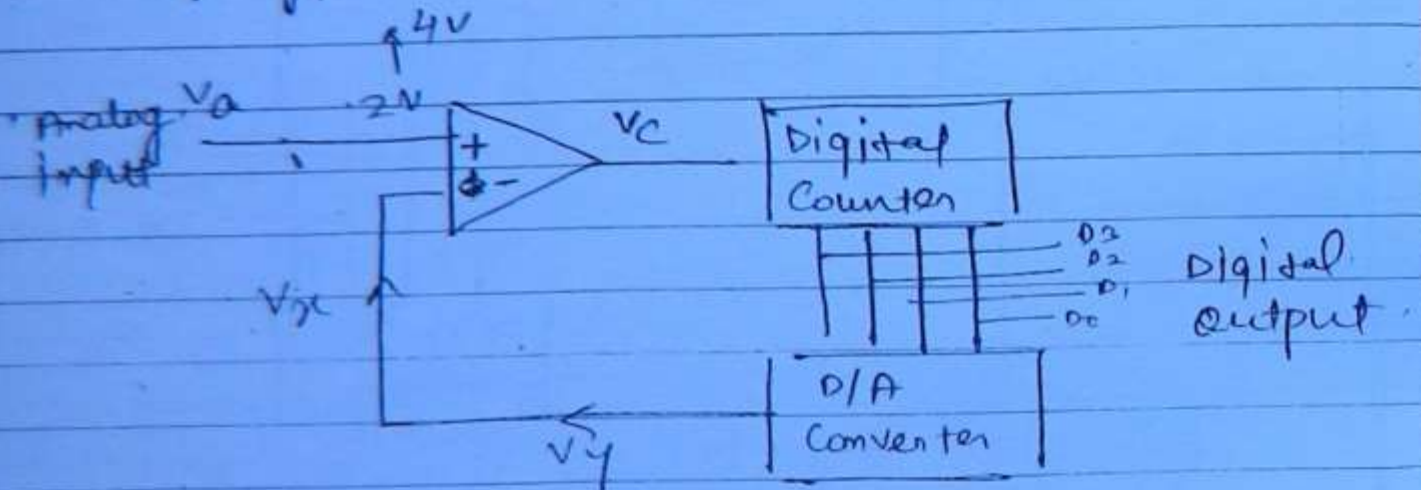

Voltage to time Converter.

$$V \propto T \quad T \propto V$$

Parameter of Digital Meter →

(179)

- (i) Resolution → Smallest value of I/P that can be measured by digital meter is called resolution.

$$R = \frac{1}{(10)^n}$$

n = No of full digit's.

- (ii) Sensitivity (S) → Smallest value of input that can be able to measure by digital meter at a given range is called sensitivity.

$$S = \text{Resolution} \times \text{min}^{\text{m}} \text{ full scale value}$$

$$S = R \times (FS)_{\text{min}}$$

$$S = R \times \text{Range of meter}$$


- (iii) Total Error →

$$\Rightarrow \left[\begin{array}{c} \% \text{ of Reading} \\ \text{value} \end{array} \right] + \begin{array}{c} \text{Error at counter} \\ \text{value} \end{array}$$

$\% \rightarrow$ Error.

- (iv) Over Ranging → The extra $\frac{1}{2}$ digit is switched ON is called $\frac{1}{2}$ digit.
↳ Over Ranging.

$n = 3$

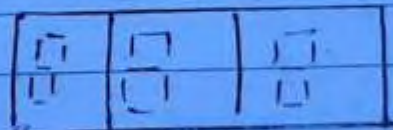

Full Digit's


(Resolution)

$$\frac{1}{10^3} = 0.001$$

000 - 999

0-1V Range

000 - 999

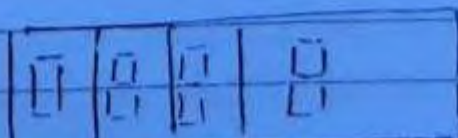

$$\frac{1}{10^4} = 0.0001$$

0-1V range
0000 - 1999
0000 - 1.999


Q How a no 0.457 can be displayed in $3\frac{1}{2}$ digital meter in the ranges of (i) 0-1 volt
(ii) 0-10 volt, (iii) 0-100 volt's.

(180)

Range	Resolution	Sensitivity	Display
0-1 V	$\frac{1}{10^3} = .001$	<u>.001</u>	0.457
0-10 V	$\frac{1}{10^3} = .001$	<u>.01</u>	00.45
0-100 V	$\frac{1}{10^3} = .001$	<u>0.1</u>	000.4

Error Analysis →

Types of Error

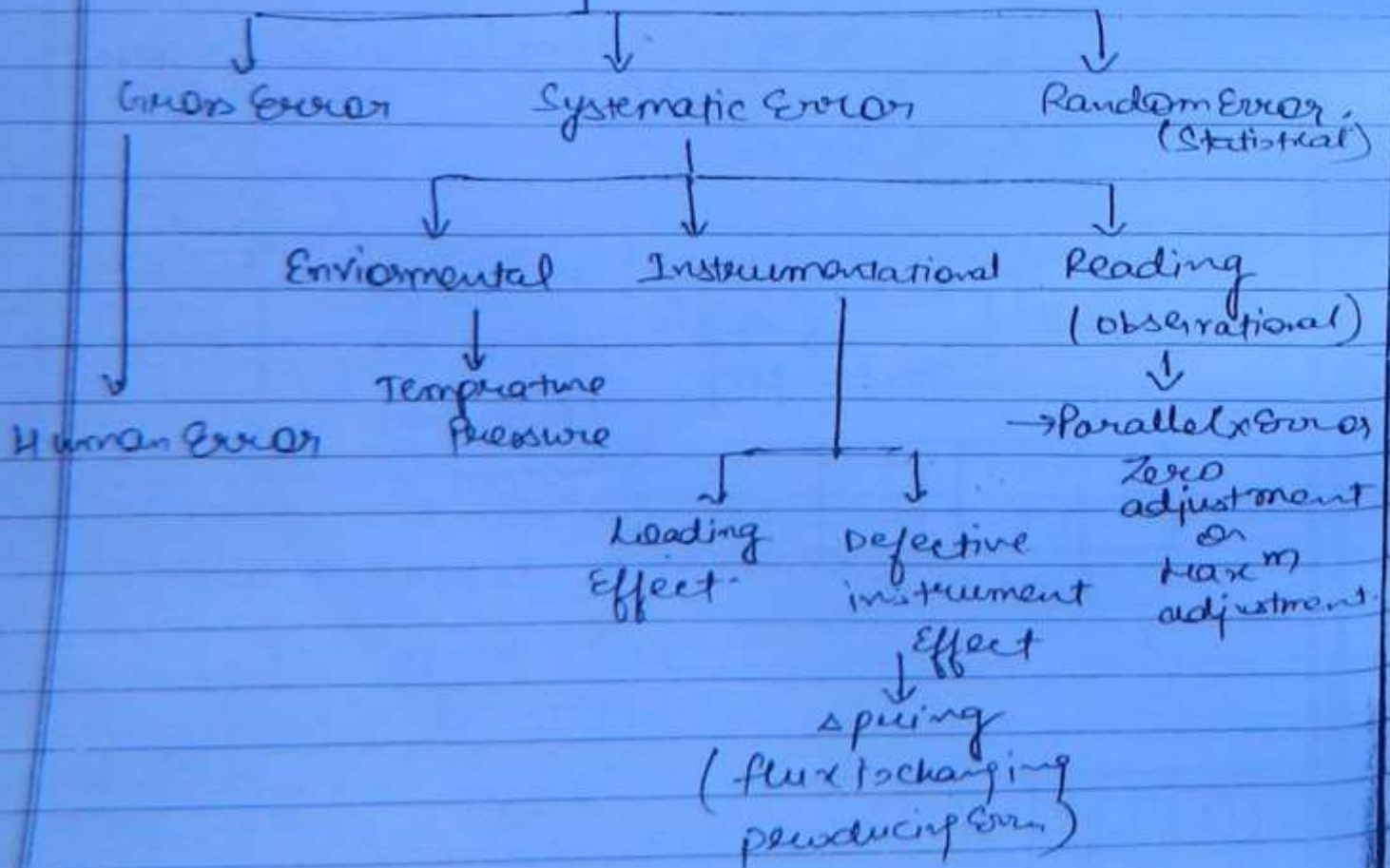

$$\% E_r = \frac{A_m - A_T}{A_T} \times 100$$

(181)

% Error measured value = $\frac{\text{Full Scale Value} \times \% \text{ Full Scale Error}}{\text{Measured Value}}$

Q An ammeter has a full scale value of 100 amps and a full scale error of 2% then what is the error in the measurement of current of

- (i) 50 amp.
- (ii) 20 amp
- (iii) 10 amp.

Ans (i) $\frac{100 \times 2}{50} \Rightarrow 4 \%$

(ii) $\frac{100 \times 2}{20} \Rightarrow 10 \%$

(iii) $\frac{100 \times 2}{10} \Rightarrow 20 \%$

The error increases at the lower value of the readings if the error is specified as full scale.

Composite Error →

$$x_1 = a \pm E_{r1}$$

$$x_2 = b \pm E_{r2}$$

$$x_3 = c \pm E_{r3}$$

a) Sum or Difference Term :-

$$x = x_1 + x_2 + x_3$$

$$= -x_1 + x_2 - x_3$$

$$\% \varepsilon_x = \pm \left[\frac{a}{(a+b+c)} \varepsilon_{q1} + \frac{b}{(a+b+c)} \varepsilon_{q2} + \frac{c}{(a+b+c)} \varepsilon_{q3} \right]$$

② Product or division terms \rightarrow

(182)

$$x = \frac{x_1 x_2}{x_3}, \quad \frac{x_1}{x_2 x_3}$$

$$\% \varepsilon_x = \pm [\varepsilon_{q1} + \varepsilon_{q2} + \varepsilon_{q3}]$$

③ Power terms \rightarrow

$$x = x_1^m x_2^n x_3^p, \quad \frac{x_1^m x_2^n}{x_3^p}$$

$$\% \varepsilon_x = \pm [m \varepsilon_{q1} + n \varepsilon_{q2} + p \varepsilon_{q3}]$$

Uncertainty Error \rightarrow

$$Y = f[x_1, x_2, \dots, x_n]$$

$w_{x1}, w_{x2}, \dots, w_{xn}$ are uncertainties of x_1, x_2, \dots, x_n .

Uncertainty of y .

$$w_y = \sqrt{\left(\frac{\partial y}{\partial x_1}\right)^2 w_{x1}^2 + \left(\frac{\partial y}{\partial x_2}\right)^2 w_{x2}^2 + \dots}$$

Standard deviation Error (s)

$$Z = f[x_1, x_2, \dots, x_n]$$

$\sigma_{x1}, \sigma_{x2}, \dots, \sigma_{xn}$ are standard deviations of x_1, x_2, \dots, x_n .

Standard deviation of Z.

(183)

$$\sigma_Z = \sqrt{\left(\frac{\partial Z}{\partial x_1}\right)^2 \sigma_{x_1}^2 + \left(\frac{\partial Z}{\partial x_2}\right)^2 \sigma_{x_2}^2 + \dots}$$

Q

$R_1 = 10 \pm 2\%$ Three resistance's are
 $R_2 = 20 \pm 3\%$ Connected in series. find
 $R_3 = 70 \pm 5\%$ Error in the measurement of
error of total series resistance.

As

$$\% E_1 = \frac{10 \times 2}{100} + \frac{20 \times 3}{100} + \frac{70 \times 5}{100}$$

$$\Rightarrow \pm 4.3\%$$

$$R_{eq} = (10 + 20 + 70) \pm 4.3\%$$

$$\Rightarrow 100 \pm 4.3\%$$

Q

Unknown resistance R is measured by using wheat stone bridge where $R = \frac{P}{Q} \cdot S$. The values of P, Q, S are $P = 10 \pm 2\%$, $Q = 20 \pm 3\%$, $S = 70 \pm 5\%$. Find the error and limiting value.

As

$$\% E_1 = [2 + 3 + 5] \Rightarrow 10\%$$

$$R \Rightarrow \frac{10 \times 70}{20} = \pm 10\%$$

$$\Rightarrow 35 \pm 10\%$$

Q

The power consumed by the resistor of $(10 \pm 2)\% \Omega$ is measured by passing a current through the resistance and the current is measured by using an ammeter that reads $(5 \pm 3)\% \text{ amps}$. Find the power

and its limiting error? $[250 \pm 8\%]$

$$P = I^2 R$$

(184)

$$\epsilon_P = \pm [2\epsilon_I + \epsilon_R]$$

$$\Rightarrow \pm [2 \times 3.5\%]$$

$$\epsilon_P = \pm 8\%$$

$$P = I^2 R \pm 8\% \Rightarrow \underline{250 \pm 8\% \text{ W}}$$

Q Find the uncertainty in the measurement of power dissipated by a resistor if the current flowing by resistor is 5 amp and the voltage across resistor is 200 volts. The uncertainty of ammeter is 0.2 amp and that of voltmeter uncertainty is 1.5 volt. Find the uncertainty of power.

Ans $V = 200, I = 5 \text{ A}$

$$W_V = 1.5 \text{ V}, W_I = 0.2 \text{ A}$$

$$P = VI$$

$$\frac{\partial P}{\partial V} = I = 5$$

$$\frac{\partial P}{\partial I} = V = 200$$

$$W_P \Rightarrow \sqrt{\left(\frac{\partial P}{\partial V}\right)^2 W_V^2 + \left(\frac{\partial P}{\partial I}\right)^2 W_I^2}$$

$$\Rightarrow \sqrt{(5)^2 \times (1.5)^2 + (200)^2 \times (0.2)^2}$$


$$\Rightarrow 40.5 \text{ W}$$

Accuracy \rightarrow It is a closeness of instrument reading approaches to the true value of the quantity being measured

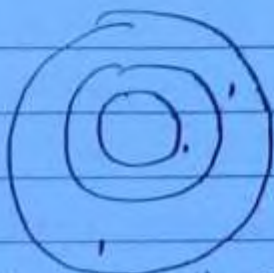
(185)

Precision \rightarrow It is a measure of reproducibility and repeating of measurement. Precision is not guaranteed for accuracy.


If the no of significant figure's \uparrow then the precision is higher



Not precise.
Not accurate

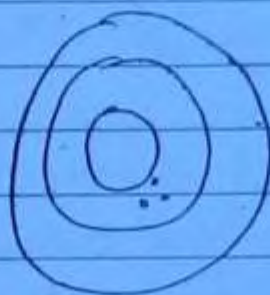

precise
Not Accurate

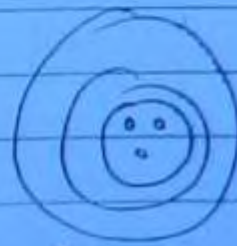

Precise
Accurate


①

25 kV	24 - 26 V - 1	} same precision
0.25 kV	0.024 - 0.026 V - 1	
250V	24.9 - 25.1 - 0.1	\rightarrow More precise.
25.00 V	24.99 - 25.01 - 0.01	Most precise

Linearity \rightarrow If the output is proportional to input then it is called linear.


Sensitivity \rightarrow It is the ratio of output to the input.

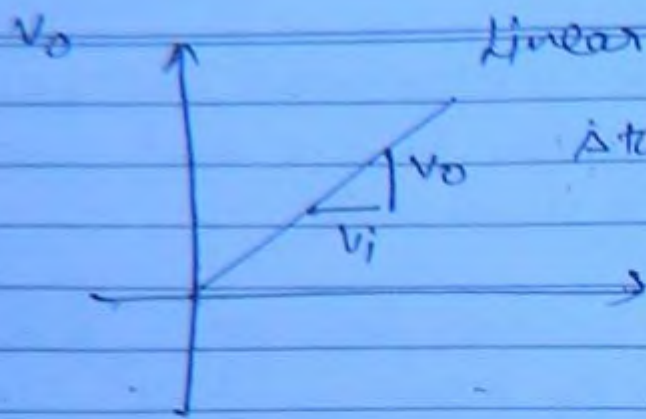For linear devices the sensitivity is same value and hence it is called static sensitivity.



$$\text{Static Sensitivity} = \frac{V_o}{V_i}$$

(186)

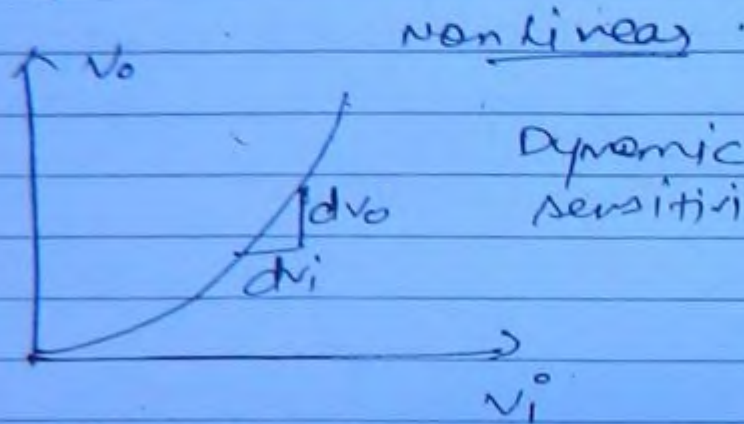


$$\text{Dynamic Sensitivity} = \frac{dV_o}{dV_i}$$



Resolution → The smallest measurable qty of the input is called resolution

Dead Time & Dead Zone → The time req for the measurement to begin to respond to changes of the input quantity is called dead time.

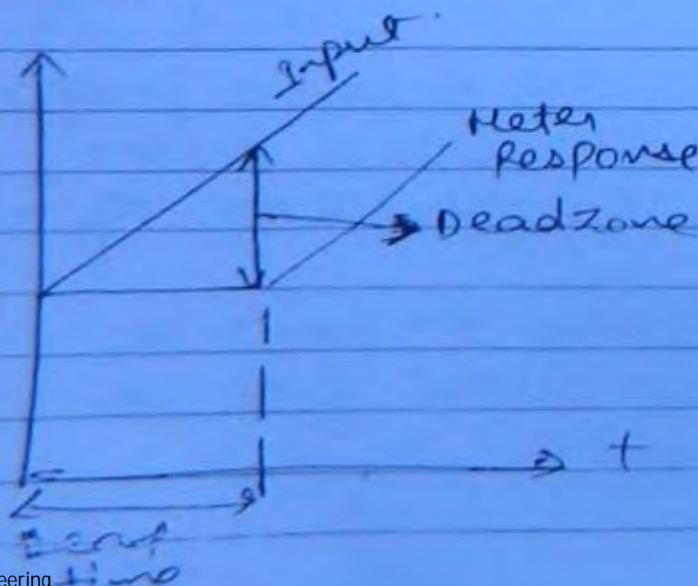Dead zone is the largest change of i/p qty for which there is no output of instrument.




187

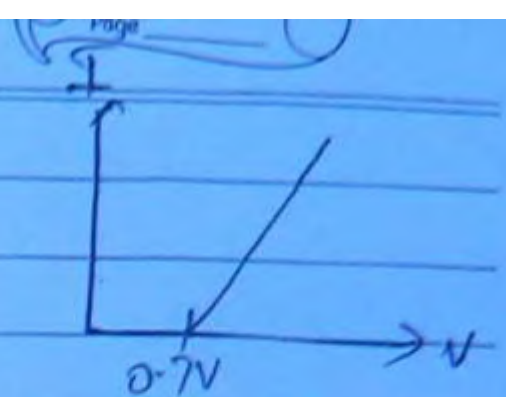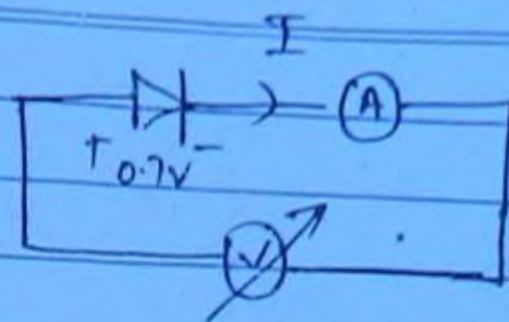

Properties of Resistance

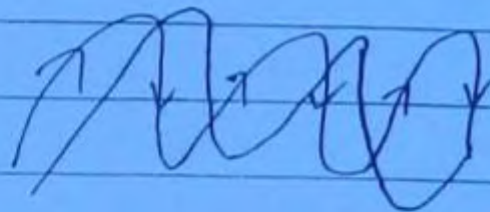- (i) Resistance should not change with time.
- (ii) The Resistivity should be higher and the tempⁿ coefficient α should be lower.
- (iii) It is independent of frequency.
- (iv) Bifilar winding is used to eliminate the effect of inductance in the resistor.



188

The End Book